#### Power Device

# Method for Monitoring Switching Waveform

To monitor a location where switching is performed by a power device element, for example, in a switching power supply or a motor drive circuit, an oscilloscope and a voltage probe are commonly used. The switching waveform is a rectangular wave, and contains high frequencies with high power in the case of power circuits. The correct waveform cannot be monitored unless the probe, which is the entrance of the waveforms, is appropriately used. This application note explains how to correctly monitor the switching waveforms.

#### Switching location

For example, even if a switching power supply circuit is created and produces a correct value of the output voltage, it is still necessary to confirm that the switching operation does not malfunction and the switching waveform does not exceed the rated voltage of the element. Since the switching waveform is a rectangular wave and contains high order harmonic components, the frequency may reach several GHz. In addition, since the power processed by power circuits is large, high voltage is generated with minimal influence from the parasitic elements (the inductance component, especially).

#### Waveform monitoring with voltage probe

Ideally, a differential probe should be used to monitor switching locations. However, since differential probes are expensive, a passive voltage probe is frequently used for low voltage circuits with a voltage of 300 V or less in general. The photograph in Figure 1 shows monitoring of a switching location with a voltage probe. The end of the probe is connected to the switching location, and the ground side is connected with the attached ground lead with alligator clip. Figure 2 shows the waveforms monitored. The top shows the switching waveform and the bottom shows the output waveform of the DC/DC converter. Ringing is observed when the switching signal changes abruptly.



Figure 1. Monitoring of switching location with voltage probe; the ground side connected with the ground lead with attached alligator clip.



Figure 2. Waveforms monitored using the probe connected with the ground lead with alligator clip

Since the ground lead of the probe is added as inductance, this ringing is caused by a series resonance with the input capacitance of the probe. Therefore, the correct waveforms cannot be monitored with this method.

Figure 3 shows an example of an equivalent circuit to the probe. In addition, the resonance equation is expressed as Equation (1). When the ground lead is 160 mm in length and the inductance per 1 mm is estimated at 1 nH, the inductance is 160 nH. From Equation (1), the resonance frequency is approximately 200 MHz.



Figure 3. Example of an equivalent circuit to the probe

$$f_r = \frac{1}{2\pi\sqrt{L_{GROUND} \times C_{PROBE}}} \quad [Hz] \tag{1}$$

To prevent the resonance and obtain the correct waveforms, the inductance added by the ground lead should be reduced. By shortening the ground lead and reducing the inductance, the resonance frequency can be increased beyond the frequency band of the measuring equipment.

Figures 4 and 5 show examples of a short ground lead. Figure 4 shows a type to be mounted on the PCB, and Figure 5 shows a type to be contacted with the PCB. Especially probe tip adapters have a ground lead of a few mm in length, reducing the inductance to a few nH. These accessories are sold together with voltage probes.



Figure 4. Probe tip adapter (Tektronix)



Figure 5. Ground spring (Tektronix)

The state where the switching location is monitored using the probe tip adapter is shown in Figure 6. The measurement result is shown in Figure 7. Compared with the above waveforms that are monitored using the probe connected with the ground lead with alligator clip (Figure 2), the ringing caused by the probe almost disappears and the obtained waveform is faithful to the original waveform.

The above method is effective if the operating voltage of the circuit is low. However, correct waveforms cannot be obtained if the operating voltage is high. In such cases, use a high voltage differential probe or an optically isolated differential probe.



Figure 6. State where the switching location is monitored using the probe tip adapter



Figure 7. Waveforms monitored with the probe using the probe tip adapter

## Simplified probe tip adapter

As mentioned above, the probe tip adapters are highly effective. However, when they are not available at hand, a simplified device may be used as a substitute. The procedure to self-build the simplified device is described below.

- Wind a leaded resistor or 0.5 mm tinned wire around the ground part of a probe to create the ground support part of the adapter (Figure 8).
- Wind a leaded resistor or 0.5 mm tinned wire around the tip of a tweezer to create the tip (end) support part of the adapter (Figure 9).
- 3. Figure 10 shows the created adapter and the probe to be used.
- Mount the adapter on the board with soldering before using (Figure 11).



Figure 8. Creating the ground support part of the adapter



Figure 9. Creating the tip (end) support part of the adapter



Figure 10. Created simplified probe tip adapter



Figure 11. State where the adapter is mounted on the board

#### Influence of probe in simulations

There may be cases where the simulation results do not match the waveforms that are actually measured. One of the causes is difference in the measurement system. Since the measurement probe in simulations is an ideal probe, its input impedance is infinite. On the other hand, since the measuring equipment is connected to the monitoring point in actual measurements, various parasitic impedances are added. Since the ground lead of the probe mentioned above is one of such parasitic components, if a simulated waveform does not match the waveform that is actually measured, it is also necessary to add the equivalent circuit of the measuring equipment to the simulation circuit and perform verification.

Figure 12 shows a circuit diagram to simulate the switching by MOSFETs and Figure 13 shows the result. In this result, a waveform with almost no ringing is monitored.

Next, on the assumption that a probe is used for monitoring, Figure 14 shows a circuit diagram where the simulation is performed with the addition of the equivalent circuit in Figure 3. The result is shown in Figure 15. The ground lead is assumed to be 160 mm in length, having 160 nH of inductance. A large ringing occurs in the waveform, showing a major difference from the original waveform.

Although the above is one example, it can be seen that the equivalent circuit added by the measurement system affects the monitored waveform.



Figure 12. Circuit to simulate the switching by MOSFETs



Figure 13. Waveform resulting from the simulation in Figure 12



PULSE(0 18 0 1n 1n 1u 2u 0)

Figure 14. Simulation circuit with the addition of an equivalent circuit to the probe



Figure 15. Waveform resulting from the simulation in Figure 14

N	o t	i c	е
---	-----	-----	---

- The information contained in this document is intended to introduce ROHM Group (hereafter referred to asROHM) products. When using ROHM products, please verify the latest specifications or datasheets before use.
- 2) ROHM products are designed and manufactured for use in general electronic equipment and applications (such as Audio Visual equipment, Office Automation equipment, telecommunication equipment, home appliances, amusement devices, etc.) or specified in the datasheets. Therefore, please contact the ROHM sales representative before using ROHM products in equipment or devices requiring extremely high reliability and whose failure or malfunction may cause danger or injury to human life or body or other serious damage (such as medical equipment, transportation, traffic, aircraft, spacecraft, nuclear power controllers, fuel control, automotive equipment including car accessories, etc. hereafter referred to as Specific Applications). Unless otherwise agreed in writing by ROHM in advance, ROHM shall not be in any way responsible or liable for any damages, expenses, or losses incurred by you or third parties arising from the use of ROHM Products for Specific Applications.
- 3) Electronic components, including semiconductors, can fail or malfunction at a certain rate. Please be sure to implement, at your own responsibilities, adequate safety measures including but not limited to fail-safe design against physical injury, and damage to any property, which a failure or malfunction of products may cause.
- 4) The information contained in this document, including application circuit examples and their constants, is intended to explain the standard operation and usage of ROHM products, and is not intended to guarantee, either explicitly or implicitly, the operation of the product in the actual equipment it will be used. As a result, you are solely responsible for it, and you must exercise your own independent verification and judgment in the use of such information contained in this document. ROHM shall not be in any way responsible or liable for any damages, expenses, or losses incurred by you or third parties arising from the use of such information.
- 5) When exporting ROHM products or technologies described in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, such as the Foreign Exchange and Foreign Trade Act and the US Export Administration Regulations, and follow the necessary procedures in accordance with these provisions.
- 6) The technical information and data described in this document, including typical application circuits, are examples only and are not intended to guarantee to be free from infringement of third parties intellectual property or other rights. ROHM does not grant any license, express or implied, to implement, use, or exploit any intellectual property or other rights owned or controlled by ROHM or any third parties with respect to the information contained herein.
- 7) No part of this document may be reprinted or reproduced in any form by any means without the prior written consent of ROHM.
- 8) All information contained in this document is current as of the date of publication and subject to change without notice. Before purchasing or using ROHM products, please confirm the latest information with the ROHM sales representative.
- 9) ROHM does not warrant that the information contained herein is error-free. ROHM shall not be in any way responsible or liable for any damages, expenses, or losses incurred by you or third parties resulting from errors contained in this document.



Thank you for your accessing to ROHM product informations. More detail product informations and catalogs are available, please contact us.

### **ROHM** Customer Support System

https://www.rohm.com/contactus