

Power Device

# Calculating Power Loss from Measured Waveforms

This application note describes how to calculate the power loss of a SiC MOSFET from measured switching waveforms in a switching circuit with a SiC MOSFET.

## Measurement of switching waveforms

Figure 1 shows a switching circuit and probes for monitoring waveforms. The voltage between the drain and source of the MOSFET is measured using a differential voltage probe. In addition, a current probe is used for the drain current.

Figure 2 shows the waveform of each component and the power loss is shown (shaded area).  $t_{on}$  and  $t_{off}$  represent the turn on and turn off times, respectively. The switching loss occurs where  $V_{DS}$  and  $I_D$  overlap in these sections. During the turn ON, since this circuit has an inductance load,  $I_D$  starts changing first and then  $V_{DS}$  starts changing after the current change is completed. During the turn OFF, on the other hand,  $V_{DS}$  starts changing first and then  $I_D$  starts changing after the voltage change is completed. Next,  $T_{ON}$  is the section where the MOSFET is in an ON state, and conduction loss occurs due to  $I_D$  and the on-resistance of the MOSFET.

The latest oscilloscopes may automatically compute the shaded area and display the power loss. However, you need to calculate the power loss from the measured waveforms when using oscilloscopes without this function.

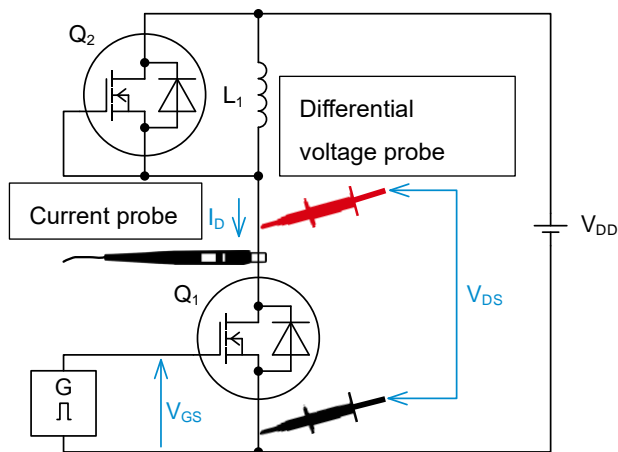


Figure 1. Switching circuit and probes for monitoring waveforms

waveforms cannot be captured with an insufficient sampling number, causing an error in the measurement result. It is necessary to display the sampling points and check whether the waveforms are traced accurately. The second point is that, since the characteristics of the delay time are different between the voltage and current probes, the measured waveforms include an error due to this difference in delay. Without correction, deviation is produced along the direction of the time axis between voltage and current, resulting in an incorrect shaded area in Figure 2. This leads to a larger or smaller loss than the actual value, giving erroneous results. To eliminate the difference in delay from the measurement system, it is necessary to perform a skew correction (de-skew). For the method, refer to the instruction manuals of the measuring instruments or the technical materials of the manufacturers of the measuring instruments.

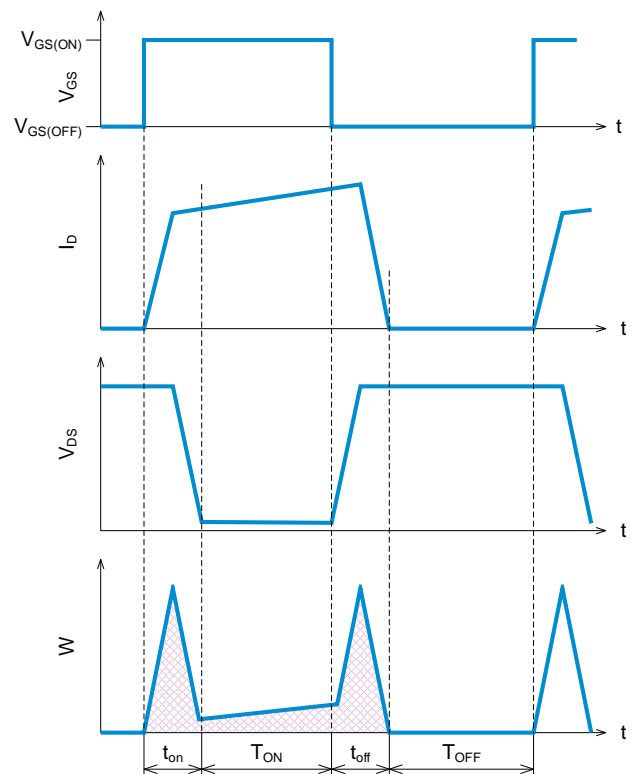


Figure 2. Waveform of each component and power loss (shaded area)

The following are cautions for the measurement. The first point is the sampling number of the oscilloscope. The detail of the

### Approximate calculation for waveforms

From the measured waveforms, calculate the power loss by dividing them into sections where a linear approximation can be performed. First, calculate power losses  $P_{ton}$  and  $P_{toff}$  to be consumed during the turn on and turn off times, respectively. The power loss is calculated with the approximate equations in Table 1. Since the calculation formula depends on waveform shapes, select one that is close to the shape of the measured waveform.

In the example of the waveforms shown in Figure 3, divide the waveforms during the turn ON into two sections, and use case 2 in Table 1 for the former section ( $t_{on1}$ ). In addition, use the equation under  $I_{D1} := 0$  as the condition. For the latter section ( $t_{on2}$ ), use the equation under  $V_{DS2} := 0$  in case 3. Although voltage is produced by the on-resistance of the MOSFET and  $I_D$  in Figure 3,  $V_{DS2(on)}$  is treated as 0 if it is sufficiently small relative to the High voltage of  $V_{DS}$ . As a result, the power loss during the turn ON can be approximated with the following equation.

$$P_{ton} \approx \frac{1}{2} V_{DS1(on)} I_{D2(on)} t_{on1} f + \frac{1}{6} V_{DS1(on)} (2 I_{D2(on)} + I_{D3(on)}) t_{on2} f \quad (1)$$

Similarly, divide the waveform during the turn OFF into two sections, and use the equation under  $V_{DS1} := 0$  in case 1 for the former section ( $t_{off1}$ ). For the latter section ( $t_{off2}$ ), use the equation under  $I_{D2} := 0$  in case 8. Although voltage is produced in Figure 3 for the same reason as mentioned above,  $V_{DS1(off)}$  is treated as 0 if it is sufficiently small relative to the High voltage of  $V_{DS}$ . As a result, the power loss during the turn OFF can be approximated with the following equation.

$$P_{toff} \approx \frac{1}{6} V_{DS2(off)} (I_{D1(off)} + 2 I_{D2(off)}) t_{off1} f + \frac{1}{2} V_{DS2(off)} I_{D2(off)} t_{off2} f \quad (2)$$

Next, calculate the power loss to be consumed during conduction. Figure 4 shows an example of the waveforms to determine the conduction loss. Since the MOSFET is energized in the  $T_{ON}$  section,  $V_{DS}$  is the product of the on-resistance of the MOSFET and  $I_D$ . Refer to the data sheet for the value of the on-resistance. To calculate the power loss, select one of the cases in Table 2 where the shape is close to the waveform and use the approximate equation.

For this example, case 1 in Table 2 is used. The conduction loss can be calculated with the following equation.

$$P_{ON} \approx \frac{1}{3} R_{ON} (I_{D1(ON)}^2 + I_{D1(ON)} I_{D2(ON)} + I_{D2(ON)}^2) T_{ON} f \quad (3)$$

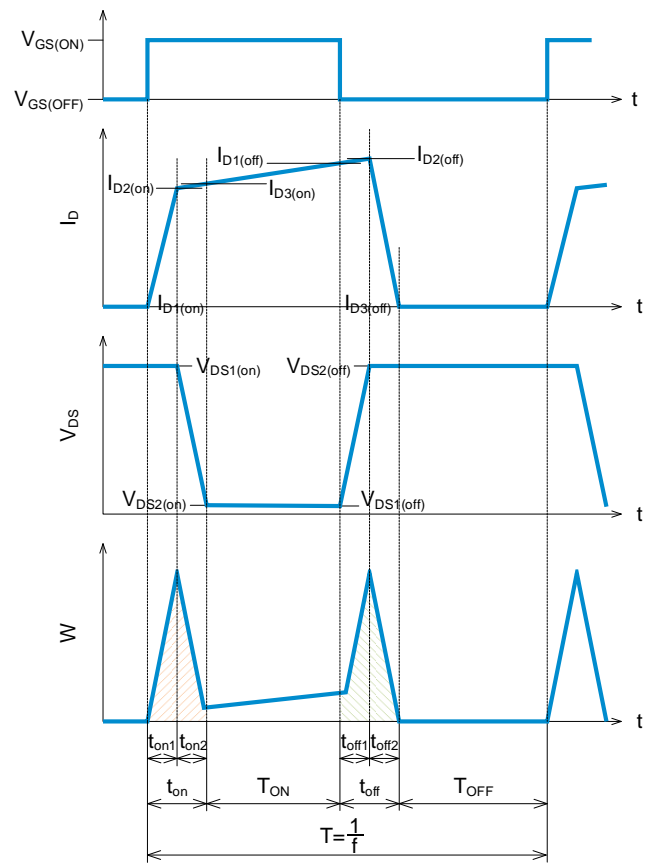


Figure 3. Example of switching loss waveforms

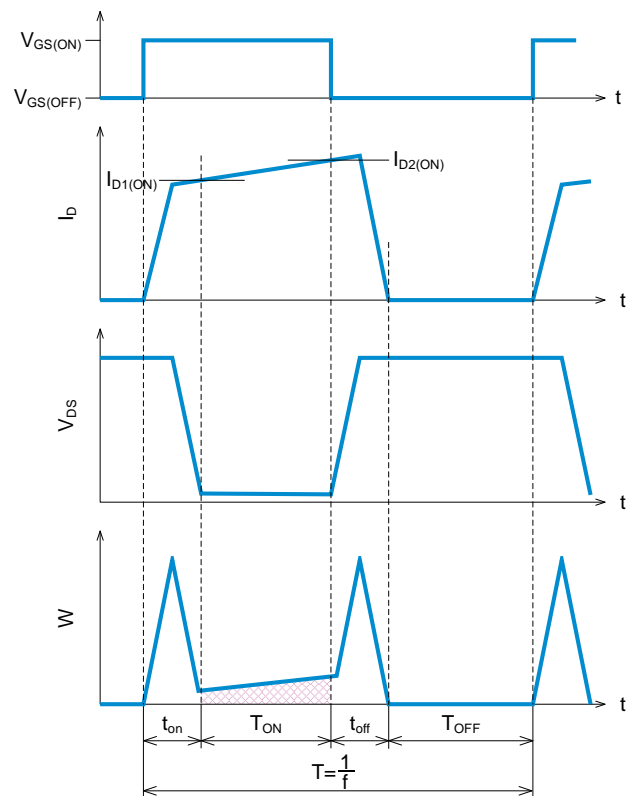







Figure 4. Example of conduction loss waveforms

Next, calculate the power loss when the MOSFET is turned OFF. In Figure 4, the MOSFET is turned OFF in the  $T_{OFF}$  section. Since  $I_D$  is sufficiently small, the power loss is considered to be 0.

The power loss of the MOSFET is the sum of the power losses calculated so far.

$$P_D = P_{ton} + P_{toff} + P_{ON} \quad [W] \quad (4)$$




Table 1. Calculation formulas of switching loss using linear approximation for each waveform shape

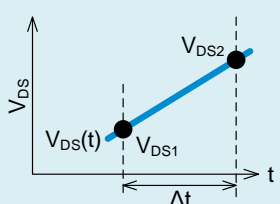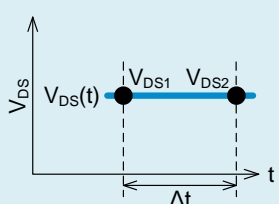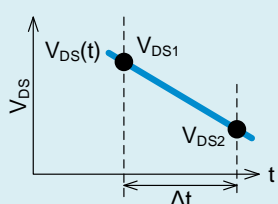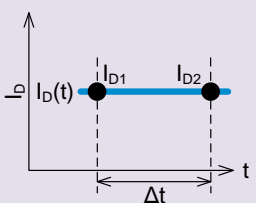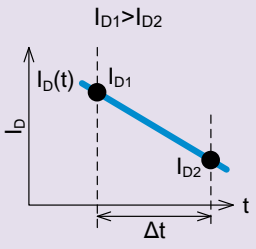		Variation in $V_{DS}$ with time		
Variation in $I_D$ with time		$V_{DS1} < V_{DS2}$	$V_{DS1} = V_{DS2}$	$V_{DS1} > V_{DS2}$
				
		Case 1 (see Appendix A)	Case 2 (see Appendix B)	Case 3 (see Appendix C)
		$P \approx$ See Equation (A) below $V_{DS1} := 0,$ $P \approx \frac{1}{6} V_{DS2} (I_{D1} + 2 I_{D2}) \Delta t f$ $I_{D1} := 0,$ $P \approx \frac{1}{6} (V_{DS1} + 2 V_{DS2}) I_{D2} \Delta t f$	$P \approx \frac{1}{2} V_{DS1} (I_{D1} + I_{D2}) \Delta t f \quad (C)$ $I_{D1} := 0,$ $P \approx \frac{1}{2} V_{DS1} I_{D2} \Delta t f$	$P \approx$ Equation (A) below $I_{D1} := 0,$ $P \approx \frac{1}{6} (V_{DS1} + 2 V_{DS2}) I_{D2} \Delta t f$ $V_{DS2} := 0,$ $P \approx \frac{1}{6} V_{DS1} (2 I_{D1} + I_{D2}) \Delta t f$ $I_{D1} := 0, V_{DS2} := 0,$ $P \approx \frac{1}{6} V_{DS1} I_{D2} \Delta t f$
		Case 4 (see Appendix D)	Case 5 (see Appendix E)	Case 6 (see Appendix F)
				
		$P \approx \frac{1}{2} (V_{DS1} + V_{DS2}) I_{D1} \Delta t f \quad (B)$ $V_{DS1} := 0,$ $P \approx \frac{1}{2} V_{DS2} I_{D1} \Delta t f$	$P = V_{DS1} I_{D1} \Delta t f \quad (D)$	$P \approx \frac{1}{2} (V_{DS1} + V_{DS2}) I_{D1} \Delta t f \quad (B)$ $V_{DS2} := 0,$ $P \approx \frac{1}{2} V_{DS1} I_{D1} \Delta t f$
		Case 7 (see Appendix G)	Case 8 (see Appendix H)	Case 9 (see Appendix I)
				
		$P \approx$ Equation (A) below $I_{D2} := 0,$ $P \approx \frac{1}{6} (2 V_{DS1} + V_{DS2}) I_{D1} \Delta t f$ $V_{DS1} := 0,$ $P \approx \frac{1}{6} V_{DS2} (I_{D1} + 2 I_{D2}) \Delta t f$ $I_{D2} := 0, V_{DS1} := 0,$ $P \approx \frac{1}{6} V_{DS2} I_{D1} \Delta t f$	$P \approx \frac{1}{2} V_{DS1} (I_{D1} + I_{D2}) \Delta t f \quad (C)$ $I_{D2} := 0,$ $P \approx \frac{1}{2} V_{DS1} I_{D1} \Delta t f$	$P \approx$ Equation (A) below $V_{DS2} := 0,$ $P \approx \frac{1}{6} V_{DS1} (2 I_{D1} + I_{D2}) \Delta t f$ $I_{D2} := 0,$ $P \approx \frac{1}{6} (2 V_{DS1} + V_{DS2}) I_{D1} \Delta t f$

$$P \approx \left[ \frac{1}{3} (V_{DS1} - V_{DS2}) (I_{D1} - I_{D2}) - \frac{1}{2} I_{D1} (V_{DS1} - V_{DS2}) - \frac{1}{2} V_{DS1} (I_{D1} - I_{D2}) + V_{DS1} I_{D1} \right] \Delta t f \quad (A)$$

where,  $f$ . Switching frequency [Hz]

Table 2. Calculation formulas of conduction loss using linear approximation for each waveform shape

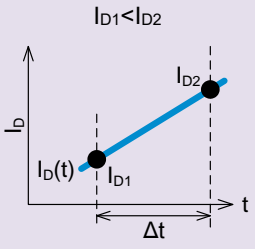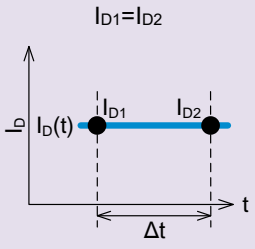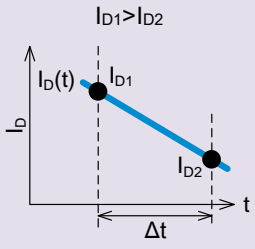Variation in $I_D$ with time		
 <p style="text-align: center;"><math>I_{D1} &lt; I_{D2}</math></p>	 <p style="text-align: center;"><math>I_{D1} = I_{D2}</math></p>	 <p style="text-align: center;"><math>I_{D1} &gt; I_{D2}</math></p>
Case 1 (see Appendix J)	Case 2 (see Appendix K)	Case 3 (see Appendix L)
$P \approx \frac{1}{3} R_{ON} (I_{D1}^2 + I_{D1} I_{D2} + I_{D2}^2) \Delta t f \quad (E)$	$P = R_{ON} I_{D1}^2 \Delta t f \quad (F)$	$P \approx \frac{1}{3} R_{ON} (I_{D1}^2 + I_{D1} I_{D2} + I_{D2}^2) \Delta t f \quad (E)$

where,  $R_{ON}$ : On-resistance of MOSFET [ $\Omega$ ]  
 $f$ : Switching frequency [Hz]

**Calculation example**

Calculate the power loss from the measured switching waveforms (Figure 5). Enlarged waveforms during turn ON, conduction, and turn OFF are shown in Figures 6, 7, and 8, respectively.

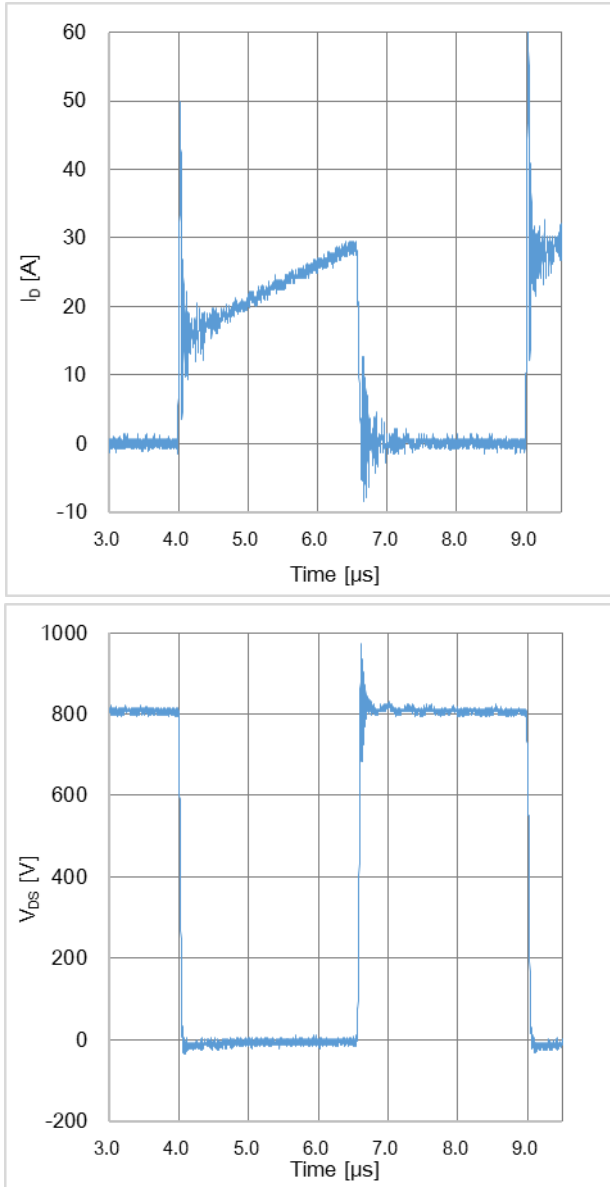


Figure 5. Switching waveforms to be used for power loss calculation

SiC MOSFET SCT3040KR manufactured by ROHM  
Switching frequency 200 kHz

Figure 6 shows the enlarged waveforms during the turn ON. Since the slope changes in the middle of the waveforms, divide them into sections with the same slope. However, this division is subjective due to complexity of the waveforms. For each section, read the start voltage and current, the end voltage and current, and the time. Substitute the values into Equation (A) in Table 1 to calculate the power loss.

An example of calculating the power loss during the turn ON is shown below. Here, the waveforms are divided into sections t1 to t5.

$$P_{t1} = \left[ \frac{1}{3}(V_{DS1} - V_{DS2})(I_{D1} - I_{D2}) - \frac{1}{2} I_{D1}(V_{DS1} - V_{DS2}) - \frac{1}{2} V_{DS1}(I_{D1} - I_{D2}) + V_{DS1} I_{D1} \right] \Delta t f$$

$$= \left[ \frac{1}{3}(800 - 800)(0 - 6.8) - \frac{1}{2} \times 0(800 - 800) - \frac{1}{2} \times 800(0 - 6.8) + 800 \times 0 \right] 7.8n \times 200k = 4.2 [W]$$

$$P_{t2} = \left[ \frac{1}{3}(800 - 710)(6.8 - 10.7) - \frac{1}{2} \times 6.8(800 - 710) - \frac{1}{2} \times 800(6.8 - 10.7) + 800 \times 6.8 \right] 4.2n \times 200k = 5.5 [W]$$

$$P_{t3} = \left[ \frac{1}{3}(710 - 389)(10.7 - 49.5) - \frac{1}{2} \times 10.7(710 - 389) - \frac{1}{2} \times 710(10.7 - 49.5) + 710 \times 10.7 \right] 24.9 \times 200k = 77.2 [W]$$

$$P_{t4} = \left[ \frac{1}{3}(389 - 83)(49.5 - 31.6) - \frac{1}{2} \times 49.5(389 - 83) - \frac{1}{2} \times 389(49.5 - 31.6) + 389 \times 49.5 \right] 13n \times 200k = 26.1 [W]$$

$$P_{t5} = \left[ \frac{1}{3}(83 - 18)(31.6 - 8.7) - \frac{1}{2} \times 31.6(83 - 18) - \frac{1}{2} \times 83(31.6 - 8.7) + 83 \times 31.6 \right] 7.9n \times 200k = 1.8 [W]$$

$$P_{ton} = P_{t1} + P_{t2} + P_{t3} + P_{t4} + P_{t5}$$

$$= 4.2 + 5.5 + 77.2 + 26.1 + 1.8$$

$$= 114.8 [W]$$

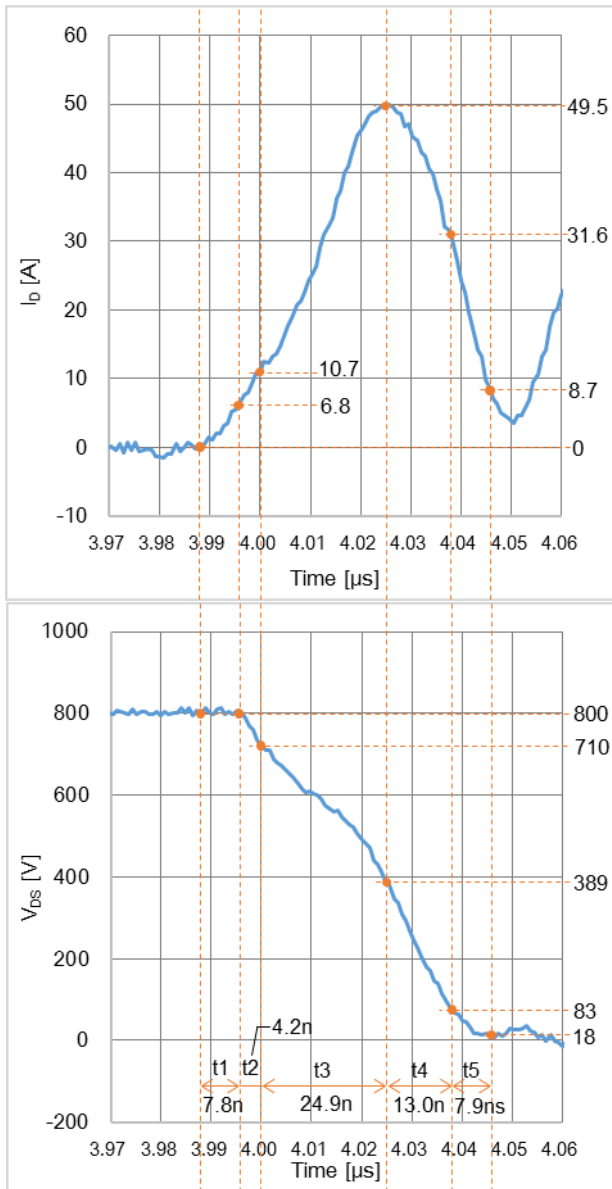


Figure 6. Enlarged waveforms and measured values in each section during turn ON

Figure 7 shows the enlarged waveforms during conduction. Here, substitute the values into Equation (E) in Table 2 to calculate the power loss. For the on-resistance of the MOSFET, use the maximum value from the data sheet.

$$\begin{aligned}
 P_{ON} &= \frac{1}{3} R_{ON} (I_{D1}^2 + I_{D1} I_{D2} + I_{D2}^2) \Delta t f \\
 &= \frac{1}{3} \times 68 \text{ m} (15^2 + 15 \times 28.7 + 28.7^2) 2.49 \mu \times 200 \text{ k} \\
 &= 16.7 \text{ [W]}
 \end{aligned}$$

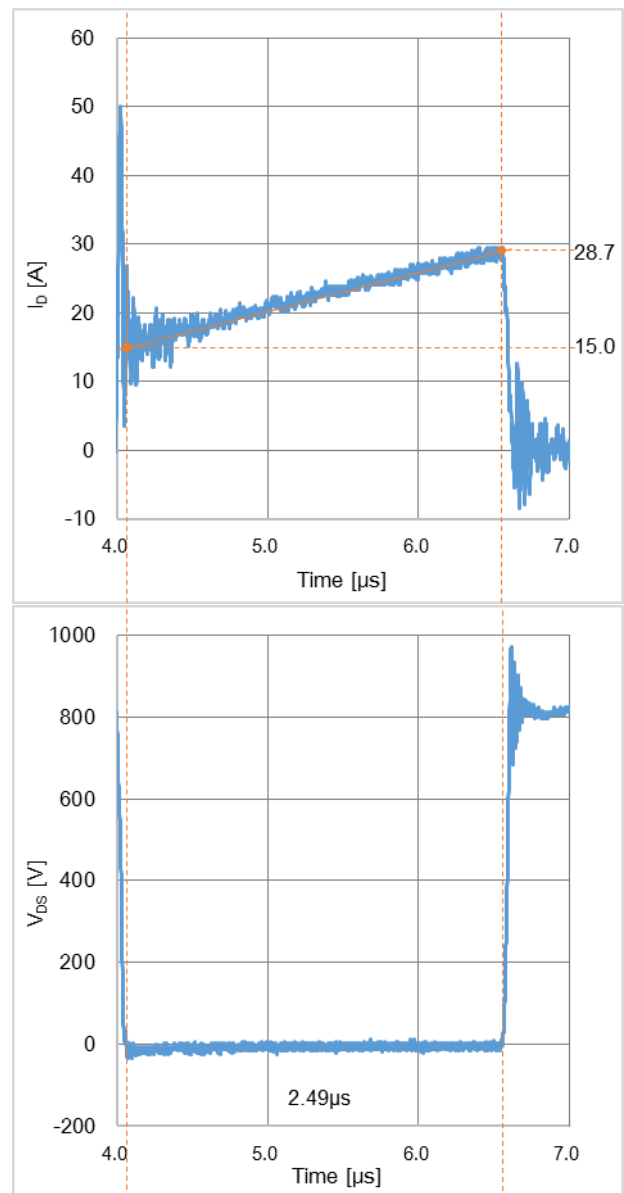


Figure 7. Enlarged waveforms and measured values during conduction

Figure 8 shows the enlarged waveforms during the turn OFF. The power loss is calculated with the same procedure as during the turn ON.

The total power loss can be calculated with the following equation.

An example of calculating the power loss during the turn OFF is shown below. Here, the waveforms are divided into sections t1 to t8.

$$\begin{aligned}
 P &= P_{ton} + P_{ON} + P_{toff} \\
 &= 114.8 + 16.7 + 63.8 \\
 &= 195.3 [W]
 \end{aligned}$$

$$\begin{aligned}
 P_{t1} &= 1.5 [W] & P_{t2} &= 9.3 [W] \\
 P_{t3} &= 9.9 [W] & P_{t4} &= 14.6 [W] \\
 P_{t5} &= 7.8 [W] & P_{t6} &= 7.0 [W] \\
 P_{t7} &= 8.0 [W] & P_{t8} &= 5.7 [W]
 \end{aligned}$$

$$P_{toff} = 1.5 + 9.3 + 9.9 + 14.6 + 7.8 + 7 + 8 + 5.7 = 63.8 [W]$$

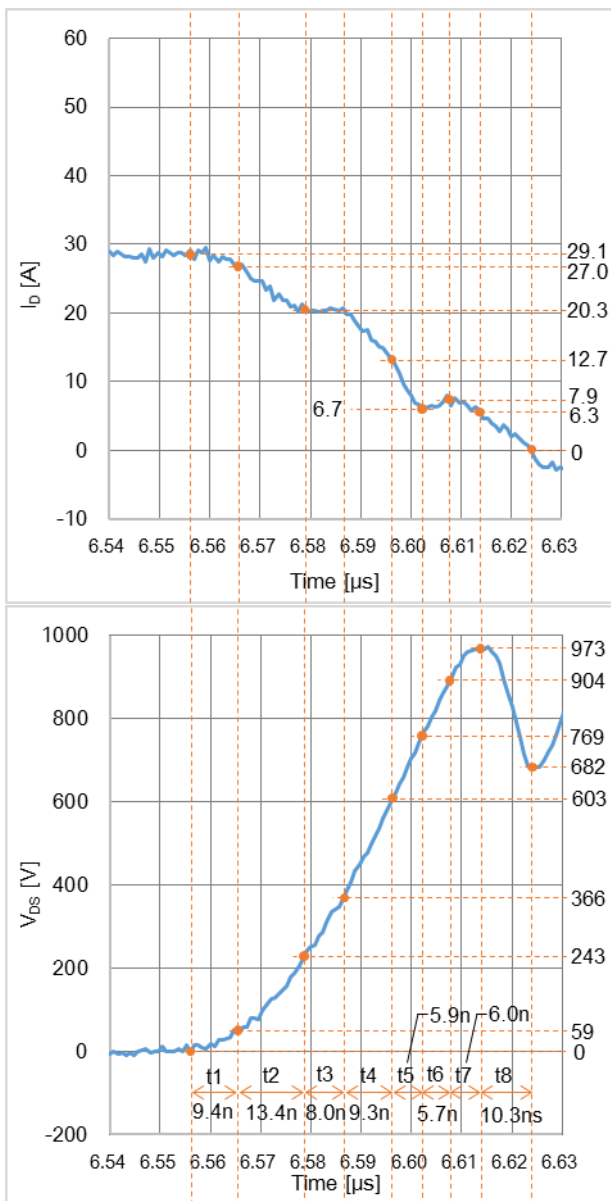


Figure 8. Enlarged waveforms and measured values in each section during turn OFF

Appendix A

Calculation of switching loss (when the waveforms of  $I_D$  and  $V_{DS}$  are increasing)

From voltage  $V_{DS}$  between the drain and source and drain current  $I_D$ , calculate the power loss (switching loss) during turn ON and turn OFF using linear approximation. The waveforms to be used for the loss calculation are shown in Figure A-1.

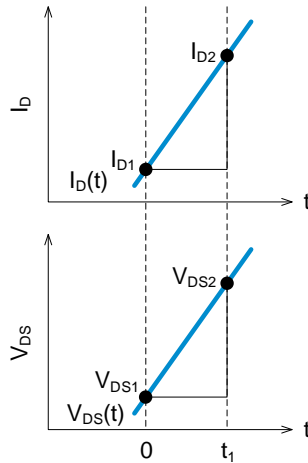


Figure A-1.  $I_D(t)$  and  $V_{DS}(t)$  in period 0- $t_1$

Power loss  $P$  in period 0- $t_1$  shown in Figure A-1 can be generally calculated with the integration of the product of the current and the voltage as shown in Equation (A-1).

$$P = f \int_0^{t_1} I_D(t) V_{DS}(t) dt \tag{A-1}$$

where,  $f$ , Switching frequency [Hz]

In addition,  $I_D(t)$  and  $V_{DS}(t)$  can be represented with Equations (A-2) and (A-3) from the slopes in Figure A-1.

$$I_D(t) = I_{D1} + \frac{I_{D2} - I_{D1}}{t_1} t = I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \tag{A-2}$$

$$V_{DS}(t) = V_{DS1} + \frac{V_{DS2} - V_{DS1}}{t_1} t = V_{DS1} - \frac{V_{DS1} - V_{DS2}}{t_1} t \tag{A-3}$$

Substitute (A-2) and (A-3) into (A-1).

$$P = f \int_0^{t_1} \left( I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \right) \left( V_{DS1} - \frac{V_{DS1} - V_{DS2}}{t_1} t \right) dt \tag{A-4}$$

$$= f \int_0^{t_1} \left( V_{DS1} I_{D1} - \frac{I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})}{t_1} t + \frac{(V_{DS1} - V_{DS2})(I_{D1} - I_{D2})}{t_1^2} t^2 \right) dt \tag{A-5}$$

Appendix A (continued)

Perform the integration according to the formula.

$$P = f \left[ V_{DS1} I_{D1} t - \frac{1}{2} \frac{I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})}{t_1} t^2 + \frac{1}{3} \frac{(V_{DS1} - V_{DS2})(I_{D1} - I_{D2})}{t_1^2} t^3 \right]_0^{t_1} \quad (A-6)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} \frac{I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})}{t_1} t_1^2 + \frac{1}{3} \frac{(V_{DS1} - V_{DS2})(I_{D1} - I_{D2})}{t_1^2} t_1^3 \right] \quad (A-7)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} (I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})) t_1 + \frac{1}{3} (V_{DS1} - V_{DS2})(I_{D1} - I_{D2}) t_1 \right] \quad (A-8)$$

$$= \left[ \frac{1}{3} (V_{DS1} - V_{DS2})(I_{D1} - I_{D2}) - \frac{1}{2} I_{D1}(V_{DS1} - V_{DS2}) - \frac{1}{2} V_{DS1}(I_{D1} - I_{D2}) + V_{DS1} I_{D1} \right] t_1 f \quad [W] \quad (A-9)$$

where,  $f$ , Switching frequency [Hz]

Next, calculate the power loss under the conditions below.

$$\underline{V_{DS1} := 0} \quad (A-10)$$

Substitute (A-10) into (A-9).

$$P = \left[ \frac{1}{3} (0 - V_{DS2})(I_{D1} - I_{D2}) - \frac{1}{2} I_{D1}(0 - V_{DS2}) - \frac{1}{2} \times 0(I_{D1} - I_{D2}) + 0 \times I_{D1} \right] t_1 f \quad (A-11)$$

$$= \left[ -\frac{1}{3} V_{DS2}(I_{D1} - I_{D2}) + \frac{1}{2} I_{D1} V_{DS2} \right] t_1 f \quad (A-12)$$

$$= \frac{1}{6} V_{DS2}(I_{D1} + 2 I_{D2}) t_1 f \quad [W] \quad (A-13)$$

$$\underline{I_{D1} := 0} \quad (A-14)$$

Substitute (A-14) into (A-9).

$$P = \left[ \frac{1}{3} (V_{DS1} - V_{DS2})(0 - I_{D2}) - \frac{1}{2} \times 0(V_{DS1} - V_{DS2}) - \frac{1}{2} V_{DS1}(0 - I_{D2}) + V_{DS1} \times 0 \right] t_1 f \quad (A-15)$$

$$= \left[ \frac{1}{3} (V_{DS1} - V_{DS2})(-I_{D2}) + \frac{1}{2} V_{DS1} I_{D2} \right] t_1 f \quad (A-16)$$

$$= \frac{1}{6} (V_{DS1} + 2 V_{DS2}) I_{D2} t_1 f \quad [W] \quad (A-17)$$

**Appendix B**

Calculation of switching loss (when the waveform of  $I_D$  is increasing and  $V_{DS}$  constant)

From voltage  $V_{DS}$  between the drain and source and drain current  $I_D$ , calculate the power loss (switching loss) during turn ON and turn OFF using linear approximation. The waveforms to be used for the loss calculation are shown in Figure B-1.

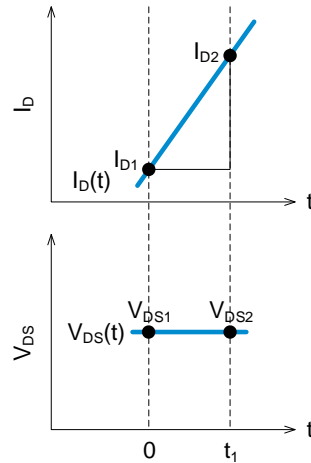


Figure B-1.  $I_D(t)$  and  $V_{DS}(t)$  in period 0- $t_1$

Power loss  $P$  in period 0- $t_1$  shown in Figure B-1 can be generally calculated with the integration of the product of the current and the voltage as shown in Equation (B-1).

$$P = f \int_0^{t_1} I_D(t) V_{DS}(t) dt \tag{B-1}$$

where,  $f$ . Switching frequency [Hz]

In addition,  $I_D(t)$  and  $V_{DS}(t)$  can be represented with Equations (B-2) and (B-3) from the slopes in Figure B-1.

$$I_D(t) = I_{D1} + \frac{I_{D2} - I_{D1}}{t_1} t = I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \tag{B-2}$$

$$V_{DS}(t) = V_{DS1} \tag{B-3}$$

Substitute (B-2) and (B-3) into (B-1).

$$P = f \int_0^{t_1} \left( I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \right) (V_{DS1}) dt \tag{B-4}$$

$$= f \int_0^{t_1} \left( V_{DS1} I_{D1} - \frac{V_{DS1} (I_{D1} - I_{D2})}{t_1} t \right) dt \tag{B-5}$$

Appendix B (continued)

Perform the integration according to the formula.

$$P = f \left[ V_{DS1} I_{D1} t - \frac{1}{2} \frac{V_{DS1}(I_{D1} - I_{D2})}{t_1} t^2 \right]_0^{t_1} \quad (B-6)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} \frac{V_{DS1}(I_{D1} - I_{D2})}{t_1} t_1^2 \right] \quad (B-7)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} (V_{DS1}(I_{D1} - I_{D2})) t_1 \right] \quad (B-8)$$

$$\underline{= \frac{1}{2} V_{DS1} (I_{D1} + I_{D2}) t_1 f} \quad [W] \quad (B-9)$$

Next, calculate the power loss under the conditions below.

$$\underline{I_{D1} := 0} \quad (B-10)$$

Substitute (B-10) into (B-9).

$$\underline{P = \frac{1}{2} V_{DS1} I_{D2} t_1 f} \quad [W] \quad (B-11)$$

Appendix C

Calculation of switching loss (when the waveform of  $I_D$  is increasing and  $V_{DS}$  decreasing)

From voltage  $V_{DS}$  between the drain and source and drain current  $I_D$ , calculate the power loss (switching loss) during turn ON and turn OFF using linear approximation. The waveforms to be used for the loss calculation are shown in Figure C-1.

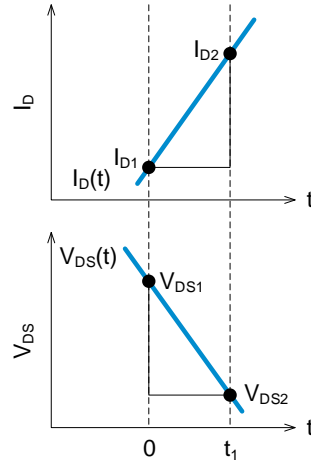


Figure C-1.  $I_D(t)$  and  $V_{DS}(t)$  in period 0- $t_1$

Power loss  $P$  in period 0- $t_1$  shown in Figure C-1 can be generally calculated with the integration of the product of the current and the voltage as shown in Equation (C-1).

$$P = f \int_0^{t_1} I_D(t) V_{DS}(t) dt \tag{C-1}$$

where,  $f$ , Switching frequency [Hz]

In addition,  $I_D(t)$  and  $V_{DS}(t)$  can be represented with Equations (C-2) and (C-3) from the slopes in Figure C-1.

$$I_D(t) = I_{D1} + \frac{I_{D2} - I_{D1}}{t_1} t = I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \tag{C-2}$$

$$V_{DS}(t) = V_{DS1} - \frac{V_{DS1} - V_{DS2}}{t_1} t \tag{C-3}$$

Substitute (C-2) and (C-3) into (C-1).

$$P = f \int_0^{t_1} \left( I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \right) \left( V_{DS1} - \frac{V_{DS1} - V_{DS2}}{t_1} t \right) dt \tag{C-4}$$

$$= f \int_0^{t_1} \left( V_{DS1} I_{D1} - \frac{I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})}{t_1} t + \frac{(V_{DS1} - V_{DS2})(I_{D1} - I_{D2})}{t_1^2} t^2 \right) dt \tag{C-5}$$

Appendix C (continued)

Perform the integration according to the formula.

$$P = f \left[ V_{DS1} I_{D1} t - \frac{1}{2} \frac{I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})}{t_1} t^2 + \frac{1}{3} \frac{(V_{DS1} - V_{DS2})(I_{D1} - I_{D2})}{t_1^2} t^3 \right]_0^{t_1} \quad (C-6)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} \frac{I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})}{t_1} t_1^2 + \frac{1}{3} \frac{(V_{DS1} - V_{DS2})(I_{D1} - I_{D2})}{t_1^2} t_1^3 \right] \quad (C-7)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} (I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})) t_1 + \frac{1}{3} (V_{DS1} - V_{DS2})(I_{D1} - I_{D2}) t_1 \right] \quad (C-8)$$

$$= \left[ \frac{1}{3} (V_{DS1} - V_{DS2})(I_{D1} - I_{D2}) - \frac{1}{2} I_{D1}(V_{DS1} - V_{DS2}) - \frac{1}{2} V_{DS1}(I_{D1} - I_{D2}) + V_{DS1} I_{D1} \right] t_1 f \quad [W] \quad (C-9)$$

Next, calculate the power loss under the conditions below.

$$\underline{I_{D1} := 0} \quad (C-10)$$

Substitute (C-10) into (C-9).

$$P = \left[ \frac{1}{3} (V_{DS1} - V_{DS2})(0 - I_{D2}) - \frac{1}{2} \times 0 (V_{DS1} - V_{DS2}) - \frac{1}{2} V_{DS1}(0 - I_{D2}) + V_{DS1} \times 0 \right] t_1 f \quad (C-11)$$

$$= \left[ \frac{1}{3} (V_{DS1} - V_{DS2})(-I_{D2}) + \frac{1}{2} V_{DS1} I_{D2} \right] t_1 f \quad (C-12)$$

$$= \frac{1}{6} (V_{DS1} + 2 V_{DS2}) I_{D2} t_1 f \quad [W] \quad (C-13)$$

$$\underline{V_{DS2} := 0} \quad (C-14)$$

Substitute (C-14) into (C-9).

$$P = \left[ \frac{1}{3} (V_{DS1} - 0)(I_{D1} - I_{D2}) - \frac{1}{2} I_{D1}(V_{DS1} - 0) - \frac{1}{2} V_{DS1}(I_{D1} - I_{D2}) + V_{DS1} I_{D1} \right] t_1 f \quad (C-15)$$

$$= \left[ \frac{1}{3} V_{DS1}(I_{D1} - I_{D2}) - \frac{1}{2} I_{D1} V_{DS1} - \frac{1}{2} V_{DS1}(I_{D1} - I_{D2}) + V_{DS1} I_{D1} \right] t_1 f \quad (C-16)$$

$$= \frac{1}{6} V_{DS1}(2 I_{D1} + I_{D2}) t_1 f \quad [W] \quad (C-17)$$

$$\underline{I_{D1} := 0, V_{DS2} := 0} \quad (C-18)$$

Substitute (C-18) into (C-9).

$$P = \left[ \frac{1}{3} (V_{DS1} - 0)(0 - I_{D2}) - \frac{1}{2} \times 0 (V_{DS1} - 0) - \frac{1}{2} V_{DS1}(0 - I_{D2}) + V_{DS1} \times 0 \right] t_1 f \quad (C-19)$$

$$= \left[ \frac{1}{3} V_{DS1}(-I_{D2}) - \frac{1}{2} V_{DS1}(-I_{D2}) \right] t_1 f \quad (C-20)$$

$$= \frac{1}{6} V_{DS1} I_{D2} t_1 f \quad [W] \quad (C-21)$$

Appendix D

Calculation of switching loss (when the waveform of  $I_D$  is constant and  $V_{DS}$  increasing)

From voltage  $V_{DS}$  between the drain and source and drain current  $I_D$ , calculate the power loss (switching loss) during turn ON and turn OFF using linear approximation. The waveforms to be used for the loss calculation are shown in Figure D-1.

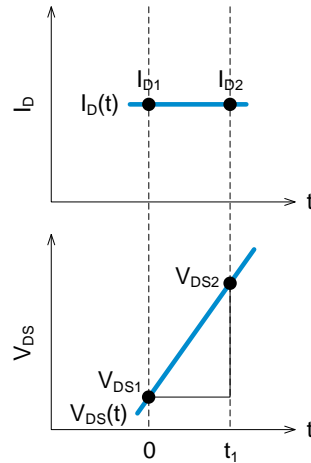


Figure D-1.  $I_D(t)$  and  $V_{DS}(t)$  in period 0- $t_1$

Power loss  $P$  in period 0- $t_1$  shown in Figure D-1 can be generally calculated with the integration of the product of the current and the voltage as shown in Equation (D-1).

$$P = f \int_0^{t_1} I_D(t) V_{DS}(t) dt \tag{D-1}$$

where,  $f$ , Switching frequency [Hz]

In addition,  $I_D(t)$  and  $V_{DS}(t)$  can be represented with Equations (D-2) and (D-3) from the slopes in Figure D-1.

$$I_D(t) = I_{D1} \tag{D-2}$$

$$V_{DS}(t) = V_{DS1} + \frac{V_{DS2} - V_{DS1}}{t_1} t = V_{DS1} - \frac{V_{DS1} - V_{DS2}}{t_1} t \tag{D-3}$$

Substitute (D-2) and (D-3) into (D-1).

$$P = f \int_0^{t_1} I_{D1} \left( V_{DS1} - \frac{V_{DS1} - V_{DS2}}{t_1} t \right) dt \tag{D-4}$$

$$= f \int_0^{t_1} \left( V_{DS1} I_{D1} - \frac{I_{D1}(V_{DS1} - V_{DS2})}{t_1} t \right) dt \tag{D-5}$$

Appendix D (continued)

Perform the integration according to the formula.

$$P = f \left[ V_{DS1} I_{D1} t - \frac{1}{2} \frac{I_{D1}(V_{DS1} - V_{DS2})}{t_1} t^2 \right]_0^{t_1} \quad (D-6)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} \frac{I_{D1}(V_{DS1} - V_{DS2})}{t_1} t_1^2 \right] \quad (D-7)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} (I_{D1}(V_{DS1} - V_{DS2})) t_1 \right] \quad (D-8)$$

$$= \frac{1}{2} (V_{DS1} + V_{DS2}) I_{D1} t_1 f \quad [W] \quad (D-9)$$

Next, calculate the power loss under the conditions below.

$$\underline{V_{DS1} := 0} \quad (D-10)$$

Substitute (D-10) into (D-9).

$$P = \frac{1}{2} (0 + V_{DS2}) I_{D1} t_1 f \quad (D-11)$$

$$= \frac{1}{2} V_{DS2} I_{D1} t_1 f \quad [W] \quad (D-12)$$

## Appendix E

Calculation of switching loss (when  $I_D$  and  $V_{DS}$  are constant)

From voltage  $V_{DS}$  between the drain and source and drain current  $I_D$ , calculate the power loss (switching loss) during turn ON and turn OFF using linear approximation. The waveforms to be used for the loss calculation are shown in Figure E-1.

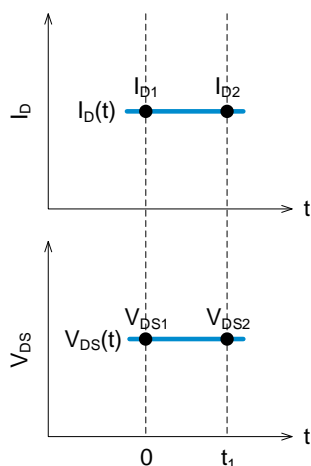


Figure E-1.  $I_D(t)$  and  $V_{DS}(t)$  in period 0- $t_1$

Power loss  $P$  in period 0- $t_1$  shown in Figure E-1 can be generally calculated with the integration of the product of the current and the voltage as shown in Equation (E-1).

$$P = f \int_0^{t_1} I_D(t) V_{DS}(t) dt \quad (E - 1)$$

where,  $f$ , Switching frequency [Hz]

In addition,  $I_D(t)$  and  $V_{DS}(t)$  can be represented with Equations (E-2) and (E-3) from the slopes in Figure E-1.

$$I_D(t) = I_{D1} \quad (E - 2)$$

$$V_{DS}(t) = V_{DS1} \quad (E - 3)$$

Substitute (E-2) and (E-3) into (E-1).

$$P = f \int_0^{t_1} I_{D1} V_{DS1} dt \quad (E - 4)$$

Perform the integration according to the formula.

$$P = f [V_{DS1} I_{D1} t]_0^{t_1} \quad (E - 5)$$

$$= \underline{V_{DS1} I_{D1} t_1 f} \quad [W] \quad (E - 6)$$

Appendix F

Calculation of switching loss (when the waveform of  $I_D$  is constant and  $V_{DS}$  decreasing)

From voltage  $V_{DS}$  between the drain and source and drain current  $I_D$ , calculate the power loss (switching loss) during turn ON and turn OFF using linear approximation. The waveforms to be used for the loss calculation are shown in Figure F-1.

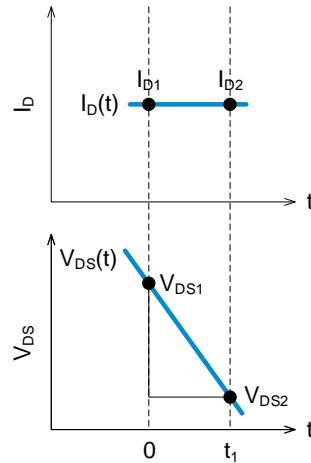


Figure F-1.  $I_D(t)$  and  $V_{DS}(t)$  in period 0- $t_1$

Power loss  $P$  in period 0- $t_1$  shown in Figure F-1 can be generally calculated with the integration of the product of the current and the voltage as shown in Equation (F-1).

$$P = f \int_0^{t_1} I_D(t) V_{DS}(t) dt \tag{F-1}$$

where,  $f$ , Switching frequency [Hz]

In addition,  $I_D(t)$  and  $V_{DS}(t)$  can be represented with Equations (F-2) and (F-3) from the slopes in Figure F-1.

$$I_D(t) = I_{D1} \tag{F-2}$$

$$V_{DS}(t) = V_{DS1} - \frac{V_{DS1} - V_{DS2}}{t_1} t \tag{F-3}$$

Substitute (F-2) and (F-3) into (F-1).

$$P = f \int_0^{t_1} I_{D1} \left( V_{DS1} - \frac{V_{DS1} - V_{DS2}}{t_1} t \right) dt \tag{F-4}$$

$$= f \int_0^{t_1} \left( V_{DS1} I_{D1} - \frac{I_{D1}(V_{DS1} - V_{DS2})}{t_1} t \right) dt \tag{F-5}$$

Appendix F (continued)

Perform the integration according to the formula.

$$P = f \left[ V_{DS1} I_{D1} t - \frac{1}{2} \frac{I_{D1}(V_{DS1} - V_{DS2})}{t_1} t^2 \right]_0^{t_1} \quad (F-6)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} \frac{I_{D1}(V_{DS1} - V_{DS2})}{t_1} t_1^2 \right] \quad (F-7)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} (I_{D1}(V_{DS1} - V_{DS2})) t_1 \right] \quad (F-8)$$

$$= \frac{1}{2} (V_{DS1} + V_{DS2}) I_{D1} t_1 f \quad [W] \quad (F-9)$$

Next, calculate the power loss under the conditions below.

$$\underline{V_{DS2} := 0} \quad (F-10)$$

Substitute (F-10) into (F-9).

$$P = \frac{1}{2} (V_{DS1} + 0) I_{D1} t_1 f \quad (F-11)$$

$$= \frac{1}{2} V_{DS1} I_{D1} t_1 f \quad [W] \quad (F-12)$$

## Appendix G

Calculation of switching loss (when the waveform of  $I_D$  is decreasing and  $V_{DS}$  increasing)

From voltage  $V_{DS}$  between the drain and source and drain current  $I_D$ , calculate the power loss (switching loss) during turn ON and turn OFF using linear approximation. The waveforms to be used for the loss calculation are shown in Figure G-1.

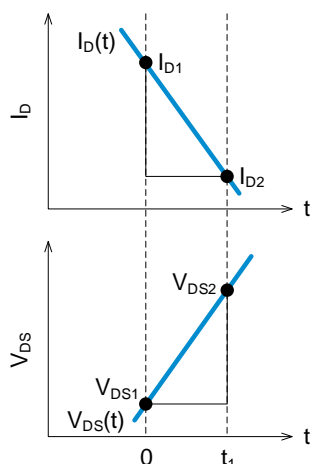


Figure G-1.  $I_D(t)$  and  $V_{DS}(t)$  in period 0- $t_1$

Power loss  $P$  in period 0- $t_1$  shown in Figure G-1 can be generally calculated with the integration of the product of the current and the voltage as shown in Equation (G-1).

$$P = f \int_0^{t_1} I_D(t) V_{DS}(t) dt \quad (G-1)$$

where,  $f$ , Switching frequency [Hz]

In addition,  $I_D(t)$  and  $V_{DS}(t)$  can be represented with Equations (G-2) and (G-3) from the slopes in Figure G-1.

$$I_D(t) = I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \quad (G-2)$$

$$V_{DS}(t) = V_{DS1} + \frac{V_{DS2} - V_{DS1}}{t_1} t = V_{DS1} - \frac{V_{DS1} - V_{DS2}}{t_1} t \quad (G-3)$$

Substitute (G-2) and (G-3) into (G-1).

$$P = f \int_0^{t_1} \left( I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \right) \left( V_{DS1} - \frac{V_{DS1} - V_{DS2}}{t_1} t \right) dt \quad (G-4)$$

$$= f \int_0^{t_1} \left( V_{DS1} I_{D1} - \frac{I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})}{t_1} t + \frac{(V_{DS1} - V_{DS2})(I_{D1} - I_{D2})}{t_1^2} t^2 \right) dt \quad (G-5)$$

Appendix G (continued)

Perform the integration according to the formula.

$$P = f \left[ V_{DS1} I_{D1} t - \frac{1}{2} \frac{I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})}{t_1} t^2 + \frac{1}{3} \frac{(V_{DS1} - V_{DS2})(I_{D1} - I_{D2})}{t_1^2} t^3 \right]_0^{t_1} \quad (G-6)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} \frac{I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})}{t_1} t_1^2 + \frac{1}{3} \frac{(V_{DS1} - V_{DS2})(I_{D1} - I_{D2})}{t_1^2} t_1^3 \right] \quad (G-7)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} (I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})) t_1 + \frac{1}{3} (V_{DS1} - V_{DS2})(I_{D1} - I_{D2}) t_1 \right] \quad (G-8)$$

$$= \left[ \frac{1}{3} (V_{DS1} - V_{DS2})(I_{D1} - I_{D2}) - \frac{1}{2} I_{D1}(V_{DS1} - V_{DS2}) - \frac{1}{2} V_{DS1}(I_{D1} - I_{D2}) + V_{DS1} I_{D1} \right] t_1 f \quad [W] \quad (G-9)$$

Next, calculate the power loss under the conditions below.

$$\underline{I_{D2} := 0} \quad (G-10)$$

Substitute (G-10) into (G-9).

$$P = \left[ \frac{1}{3} (V_{DS1} - V_{DS2})(I_{D1} - 0) - \frac{1}{2} I_{D1}(V_{DS1} - V_{DS2}) - \frac{1}{2} V_{DS1}(I_{D1} - 0) + V_{DS1} I_{D1} \right] t_1 f \quad (G-11)$$

$$= \left[ \frac{1}{3} (V_{DS1} - V_{DS2}) I_{D1} - \frac{1}{2} I_{D1}(V_{DS1} - V_{DS2}) - \frac{1}{2} V_{DS1} I_{D1} + V_{DS1} I_{D1} \right] t_1 f \quad (G-12)$$

$$= \frac{1}{6} (2 V_{DS1} + V_{DS2}) I_{D1} t_1 f \quad [W] \quad (G-13)$$

$$\underline{V_{DS1} := 0} \quad (G-14)$$

Substitute (G-14) into (G-9).

$$P = \left[ \frac{1}{3} (0 - V_{DS2})(I_{D1} - I_{D2}) - \frac{1}{2} I_{D1}(0 - V_{DS2}) - \frac{1}{2} \times 0(I_{D1} - I_{D2}) + 0 \times I_{D1} \right] t_1 f \quad (G-15)$$

$$= \left[ -\frac{1}{3} V_{DS2}(I_{D1} - I_{D2}) + \frac{1}{2} I_{D1} V_{DS2} \right] t_1 f \quad (G-16)$$

$$= \frac{1}{6} V_{DS2}(I_{D1} + 2 I_{D2}) t_1 f \quad [W] \quad (G-17)$$

$$\underline{I_{D2} := 0, V_{DS1} := 0} \quad (G-18)$$

Substitute (G-18) into (G-9).

$$P = \left[ \frac{1}{3} (0 - V_{DS2})(I_{D1} - 0) - \frac{1}{2} I_{D1}(0 - V_{DS2}) - \frac{1}{2} \times 0(I_{D1} - 0) + 0 \times I_{D1} \right] t_1 f \quad (G-19)$$

$$= \left( -\frac{1}{3} V_{DS2} I_{D1} + \frac{1}{2} I_{D1} V_{DS2} \right) t_1 f \quad (G-20)$$

$$= \frac{1}{6} V_{DS2} I_{D1} t_1 f \quad [W] \quad (G-21)$$

## Appendix H

Calculation of switching loss (when the waveform of  $I_D$  is decreasing and  $V_{DS}$  constant)

From voltage  $V_{DS}$  between the drain and source and drain current  $I_D$ , calculate the power loss (switching loss) during turn ON and turn OFF using linear approximation. The waveforms to be used for the loss calculation are shown in Figure H-1.

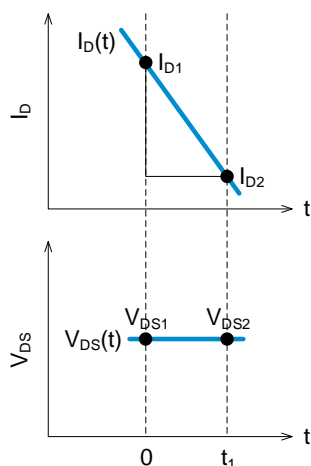


Figure H-1.  $I_D(t)$  and  $V_{DS}(t)$  in period 0- $t_1$

Power loss  $P$  in period 0- $t_1$  shown in Figure H-1 can be generally calculated with the integration of the product of the current and the voltage as shown in Equation (H-1).

$$P = f \int_0^{t_1} I_D(t) V_{DS}(t) dt \quad (H-1)$$

where,  $f$ . Switching frequency [Hz]

In addition,  $I_D(t)$  and  $V_{DS}(t)$  can be represented with Equations (H-2) and (H-3) from the slopes in Figure H-1.

$$I_D(t) = I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \quad (H-2)$$

$$V_{DS}(t) = V_{DS1} \quad (H-3)$$

Substitute (H-2) and (H-3) into (H-1).

$$P = f \int_0^{t_1} \left( I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \right) (V_{DS1}) dt \quad (H-4)$$

$$= f \int_0^{t_1} \left( V_{DS1} I_{D1} - \frac{V_{DS1} (I_{D1} - I_{D2})}{t_1} t \right) dt \quad (H-5)$$

Appendix H (continued)

Perform the integration according to the formula.

$$P = f \left[ V_{DS1} I_{D1} t - \frac{1}{2} \frac{V_{DS1}(I_{D1} - I_{D2})}{t_1} t^2 \right]_0^{t_1} \quad (H-6)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} \frac{V_{DS1}(I_{D1} - I_{D2})}{t_1} t_1^2 \right] \quad (H-7)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} (V_{DS1}(I_{D1} - I_{D2})) t_1 \right] \quad (H-8)$$

$$\underline{= \frac{1}{2} V_{DS1} (I_{D1} + I_{D2}) t_1 f} \quad [W] \quad (H-9)$$

Next, calculate the power loss under the conditions below.

$$\underline{I_{D2} := 0} \quad (H-10)$$

Substitute (H-10) into (H-9).

$$\underline{P = \frac{1}{2} V_{DS1} I_{D1} t_1 f} \quad [W] \quad (H-11)$$

## Appendix I

Calculation of switching loss (when the waveforms of  $I_D$  and  $V_{DS}$  are decreasing)

From voltage  $V_{DS}$  between the drain and source and drain current  $I_D$ , calculate the power loss (switching loss) during turn ON and turn OFF using linear approximation. The waveforms to be used for the loss calculation are shown in Figure I-1.

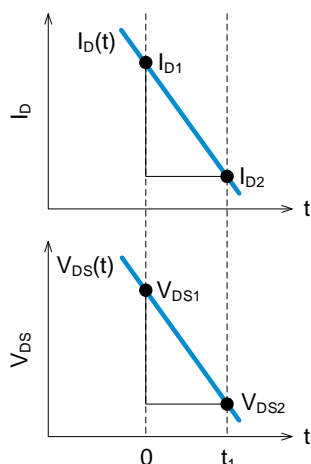


Figure I-1.  $I_D(t)$  and  $V_{DS}(t)$  in period 0- $t_1$

Power loss  $P$  in period 0- $t_1$  shown in Figure I-1 can be generally calculated with the integration of the product of the current and the voltage as shown in Equation (I-1).

$$P = f \int_0^{t_1} I_D(t) V_{DS}(t) dt \quad (I-1)$$

where,  $f$ , Switching frequency [Hz]

In addition,  $I_D(t)$  and  $V_{DS}(t)$  can be represented with Equations (I-2) and (I-3) from the slopes in Figure I-1.

$$I_D(t) = I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \quad (I-2)$$

$$V_{DS}(t) = V_{DS1} - \frac{V_{DS1} - V_{DS2}}{t_1} t \quad (I-3)$$

Substitute (I-2) and (I-3) into (I-1).

$$P = f \int_0^{t_1} \left( I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \right) \left( V_{DS1} - \frac{V_{DS1} - V_{DS2}}{t_1} t \right) dt \quad (I-4)$$

$$= f \int_0^{t_1} \left( V_{DS1} I_{D1} - \frac{I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})}{t_1} t + \frac{(V_{DS1} - V_{DS2})(I_{D1} - I_{D2})}{t_1^2} t^2 \right) dt \quad (I-5)$$

Appendix I (continued)

Perform the integration according to the formula.

$$P = f \left[ V_{DS1} I_{D1} t - \frac{1}{2} \frac{I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})}{t_1} t^2 + \frac{1}{3} \frac{(V_{DS1} - V_{DS2})(I_{D1} - I_{D2})}{t_1^2} t^3 \right]_0^{t_1} \quad (I-6)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} \frac{I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})}{t_1} t_1^2 + \frac{1}{3} \frac{(V_{DS1} - V_{DS2})(I_{D1} - I_{D2})}{t_1^2} t_1^3 \right] \quad (I-7)$$

$$= f \left[ V_{DS1} I_{D1} t_1 - \frac{1}{2} (I_{D1}(V_{DS1} - V_{DS2}) + V_{DS1}(I_{D1} - I_{D2})) t_1 + \frac{1}{3} (V_{DS1} - V_{DS2})(I_{D1} - I_{D2}) t_1 \right] \quad (I-8)$$

$$= \left[ \frac{1}{3} (V_{DS1} - V_{DS2})(I_{D1} - I_{D2}) - \frac{1}{2} I_{D1}(V_{DS1} - V_{DS2}) - \frac{1}{2} V_{DS1}(I_{D1} - I_{D2}) + V_{DS1} I_{D1} \right] t_1 f \quad [W] \quad (I-9)$$

Next, calculate the power loss under the conditions below.

$$\underline{V_{DS2} := 0} \quad (I-10)$$

Substitute (I-10) into (I-9).

$$P = \left[ \frac{1}{3} (V_{DS1} - 0)(I_{D1} - I_{D2}) - \frac{1}{2} I_{D1}(V_{DS1} - 0) - \frac{1}{2} V_{DS1}(I_{D1} - I_{D2}) + V_{DS1} I_{D1} \right] t_1 f \quad (I-11)$$

$$= \left[ \frac{1}{3} V_{DS1}(I_{D1} - I_{D2}) - \frac{1}{2} I_{D1} V_{DS1} - \frac{1}{2} V_{DS1}(I_{D1} - I_{D2}) + V_{DS1} I_{D1} \right] t_1 f \quad (I-12)$$

$$= \underline{\underline{\frac{1}{6} V_{DS1}(2 I_{D1} + I_{D2}) t_1 f}} \quad [W] \quad (I-13)$$

$$\underline{I_{D2} := 0} \quad (I-14)$$

Substitute (I-14) into (I-9).

$$P = \left[ \frac{1}{3} (V_{DS1} - V_{DS2})(I_{D1} - 0) - \frac{1}{2} I_{D1}(V_{DS1} - V_{DS2}) - \frac{1}{2} V_{DS1}(I_{D1} - 0) + V_{DS1} I_{D1} \right] t_1 f \quad (I-15)$$

$$= \left[ \frac{1}{3} (V_{DS1} - V_{DS2}) I_{D1} - \frac{1}{2} I_{D1}(V_{DS1} - V_{DS2}) - \frac{1}{2} V_{DS1} I_{D1} + V_{DS1} I_{D1} \right] t_1 f \quad (I-16)$$

$$= \underline{\underline{\frac{1}{6} (2 V_{DS1} + V_{DS2}) I_{D1} t_1 f}} \quad [W] \quad (I-17)$$

Appendix J

Calculation of power loss during conduction (when  $I_D$  is increasing)

From on-resistance  $R_{ON}$  of the MOSFET and drain current  $I_D$  of the switching waveform, calculate the power loss during conduction (0- $t_1$ ) using linear approximation. The waveforms to be used for the loss calculation are shown in Figure J-1.

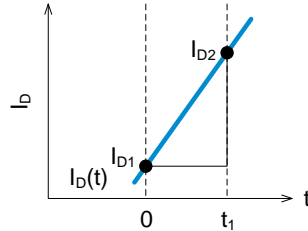


Figure J-1.  $I_D(t)$  in period 0- $t_1$

In Figure J-1, since the MOSFET is energized in period 0- $t_1$ ,  $V_{DS}$  is the product of on-resistance  $R_{ON}$  of the MOSFET and  $I_D$ .

Power loss  $P$  in period 0- $t_1$  can be generally calculated with the integration of the product of the resistance and the square of the current as shown in Equation (J-1).

$$P = f \int_0^{t_1} R_{ON} I_D(t)^2 dt \tag{J-1}$$

where,  $R_{ON}$ : On-resistance of MOSFET [ $\Omega$ ]

$f$ : Switching frequency [Hz]

In addition,  $I_D(t)$  can be represented with Equation (J-2) from the slope in Figure J-1.

$$I_D(t) = I_{D1} + \frac{I_{D2} - I_{D1}}{t_1} t = I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \tag{J-2}$$

Substitute (J-2) into (J-1).

$$P = f \int_0^{t_1} R_{ON} \left( I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \right)^2 dt \tag{J-3}$$

$$= f \int_0^{t_1} R_{ON} \left( I_{D1}^2 - 2 I_{D1} \frac{I_{D1} - I_{D2}}{t_1} t + \frac{(I_{D1} - I_{D2})^2}{t_1^2} t^2 \right) dt \tag{J-4}$$

Perform the integration according to the formula.

$$P = f R_{ON} \left[ I_{D1}^2 t - 2 I_{D1} \frac{I_{D1} - I_{D2}}{2 t_1} t^2 + \frac{(I_{D1} - I_{D2})^2}{3 t_1^2} t^3 \right]_0^{t_1} \tag{J-5}$$

$$= f R_{ON} \left( I_{D1}^2 t_1 - 2 I_{D1} \frac{I_{D1} - I_{D2}}{2 t_1} t_1^2 + \frac{(I_{D1} - I_{D2})^2}{3 t_1^2} t_1^3 \right) \tag{J-6}$$

$$= f R_{ON} \left( I_{D1}^2 t_1 - I_{D1} (I_{D1} - I_{D2}) t_1 + \frac{(I_{D1} - I_{D2})^2}{3} t_1 \right) \tag{J-7}$$

$$= f R_{ON} \left( I_{D1}^2 - I_{D1} (I_{D1} - I_{D2}) + \frac{(I_{D1} - I_{D2})^2}{3} \right) t_1 \tag{J-8}$$

Appendix J (continued)

$$P = f R_{ON} \left( I_{D1} I_{D2} + \frac{I_{D1}^2 - 2 I_{D1} I_{D2} + I_{D2}^2}{3} \right) t_1 \quad (J-9)$$

$$= f R_{ON} \left( \frac{I_{D1}^2 - 2 I_{D1} I_{D2} + I_{D2}^2 - 3 I_{D1}^2 + 3 I_{D1} I_{D2} + 3 I_{D1}^2}{3} \right) t_1 \quad (J-10)$$

$$= \frac{1}{3} R_{ON} (I_{D1}^2 + I_{D1} I_{D2} + I_{D2}^2) t_1 f \quad [W] \quad (J-11)$$

### Appendix K

Calculation of power loss during conduction (when  $I_D$  is constant)

From on-resistance  $R_{ON}$  of the MOSFET and drain current  $I_D$  of the switching waveform, calculate the power loss during conduction ( $0-t_1$ ) using linear approximation. The waveforms to be used for the loss calculation are shown in Figure K-1.

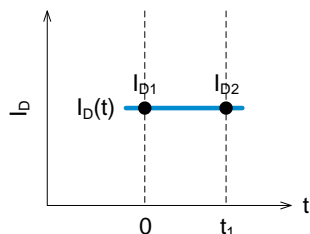


Figure K-1.  $I_D(t)$  in period  $0-t_1$

In Figure K-1, since the MOSFET is energized in period  $0-t_1$ ,  $V_{DS}$  is the product of on-resistance  $R_{ON}$  of the MOSFET and  $I_D$ .

Power loss  $P$  in period  $0-t_1$  can be generally calculated with the integration of the product of the resistance and the square of the current as shown in Equation (K-1).

$$P = f \int_0^{t_1} R_{ON} I_D(t)^2 dt \tag{K-1}$$

where,  $R_{ON}$ : On-resistance of MOSFET [ $\Omega$ ]

$f$ : Switching frequency [Hz]

In addition,  $I_D(t)$  can be represented with Equation (K-2) from the slope in Figure K-1.

$$I_D(t) = I_{D1} \tag{K-2}$$

Substitute (K-2) into (K-1).

$$P = f \int_0^{t_1} R_{ON} I_{D1}^2 dt \tag{K-3}$$

Perform the integration according to the formula.

$$P = f [R_{ON} I_{D1}^2]_0^{t_1} \tag{K-4}$$

$$= R_{ON} I_{D1}^2 t_1 f \quad [W] \tag{K-5}$$

Appendix L

Calculation of power loss during conduction (when  $I_D$  is decreasing)

From on-resistance  $R_{ON}$  of the MOSFET and drain current  $I_D$  of the switching waveform, calculate the power loss during conduction (0- $t_1$ ) using linear approximation. The waveforms to be used for the loss calculation are shown in Figure L-1.

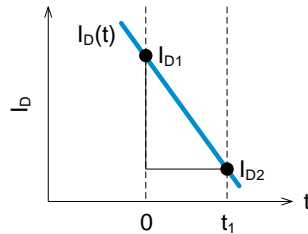


Figure L-1.  $I_D(t)$  in period 0- $t_1$

In Figure L-1, since the MOSFET is energized in period 0- $t_1$ ,  $V_{DS}$  is the product of on-resistance  $R_{ON}$  of the MOSFET and  $I_D$ .

Power loss  $P$  in period 0- $t_1$  can be generally calculated with the integration of the product of the resistance and the square of the current as shown in Equation (L-1).

$$P = f \int_0^{t_1} R_{ON} I_D(t)^2 dt \tag{L-1}$$

where,  $R_{ON}$ : On-resistance of MOSFET [ $\Omega$ ]

$f$ : Switching frequency [Hz]

In addition,  $I_D(t)$  can be represented with Equation (L-2) from the slope in Figure L-1.

$$I_D(t) = I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \tag{L-2}$$

Substitute (L-2) into (L-1).

$$P = f \int_0^{t_1} R_{ON} \left( I_{D1} - \frac{I_{D1} - I_{D2}}{t_1} t \right)^2 dt \tag{L-3}$$

$$= f \int_0^{t_1} R_{ON} \left( I_{D1}^2 - 2 I_{D1} \frac{I_{D1} - I_{D2}}{t_1} t + \frac{(I_{D1} - I_{D2})^2}{t_1^2} t^2 \right) dt \tag{L-4}$$

Perform the integration according to the formula.

$$P = f R_{ON} \left[ I_{D1}^2 t - 2 I_{D1} \frac{I_{D1} - I_{D2}}{2 t_1} t^2 + \frac{(I_{D1} - I_{D2})^2}{3 t_1^2} t^3 \right]_0^{t_1} \tag{L-5}$$

$$= f R_{ON} \left( I_{D1}^2 t_1 - 2 I_{D1} \frac{I_{D1} - I_{D2}}{2 t_1} t_1^2 + \frac{(I_{D1} - I_{D2})^2}{3 t_1^2} t_1^3 \right) \tag{L-6}$$

$$= f R_{ON} \left( I_{D1}^2 t_1 - I_{D1} (I_{D1} - I_{D2}) t_1 + \frac{(I_{D1} - I_{D2})^2}{3} t_1 \right) \tag{L-7}$$

$$= f R_{ON} \left( I_{D1}^2 - I_{D1} (I_{D1} - I_{D2}) + \frac{(I_{D1} - I_{D2})^2}{3} \right) t_1 \tag{L-8}$$

Appendix L (continued)

$$P = f R_{ON} \left( I_{D1} I_{D2} + \frac{I_{D1}^2 - 2 I_{D1} I_{D2} + I_{D2}^2}{3} \right) t_1 \quad (L-9)$$

$$= f R_{ON} \left( \frac{I_{D1}^2 - 2 I_{D1} I_{D2} + I_{D2}^2 - 3 I_{D1}^2 + 3 I_{D1} I_{D2} + 3 I_{D1}^2}{3} \right) t_1 \quad (L-10)$$

$$= \frac{1}{3} R_{ON} (I_{D1}^2 + I_{D1} I_{D2} + I_{D2}^2) t_1 f \quad [W] \quad (L-11)$$

## Notes

- 1) The information contained herein is subject to change without notice.
- 2) Before you use our Products, please contact our sales representative and verify the latest specifications :
- 3) Although ROHM is continuously working to improve product reliability and quality, semiconductors can break down and malfunction due to various factors.  
Therefore, in order to prevent personal injury or fire arising from failure, please take safety measures such as complying with the derating characteristics, implementing redundant and fire prevention designs, and utilizing backups and fail-safe procedures. ROHM shall have no responsibility for any damages arising out of the use of our Products beyond the rating specified by ROHM.
- 4) Examples of application circuits, circuit constants and any other information contained herein are provided only to illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.
- 5) The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM or any other parties. ROHM shall have no responsibility whatsoever for any dispute arising out of the use of such technical information.
- 6) The Products specified in this document are not designed to be radiation tolerant.
- 7) For use of our Products in applications requiring a high degree of reliability (as exemplified below), please contact and consult with a ROHM representative : transportation equipment (i.e. cars, ships, trains), primary communication equipment, traffic lights, fire/crime prevention, safety equipment, medical systems, servers, solar cells, and power transmission systems.
- 8) Do not use our Products in applications requiring extremely high reliability, such as aerospace equipment, nuclear power control systems, and submarine repeaters.
- 9) ROHM shall have no responsibility for any damages or injury arising from non-compliance with the recommended usage conditions and specifications contained herein.
- 10) ROHM has used reasonable care to ensure the accuracy of the information contained in this document. However, ROHM does not warrants that such information is error-free, and ROHM shall have no responsibility for any damages arising from any inaccuracy or misprint of such information.
- 11) Please use the Products in accordance with any applicable environmental laws and regulations, such as the RoHS Directive. For more details, including RoHS compatibility, please contact a ROHM sales office. ROHM shall have no responsibility for any damages or losses resulting non-compliance with any applicable laws or regulations.
- 12) When providing our Products and technologies contained in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, including without limitation the US Export Administration Regulations and the Foreign Exchange and Foreign Trade Act.
- 13) This document, in part or in whole, may not be reprinted or reproduced without prior consent of ROHM.



Thank you for your accessing to ROHM product informations.  
More detail product informations and catalogs are available, please contact us.

## ROHM Customer Support System

<http://www.rohm.com/contact/>