

Linear Regulator Series

Calculating Junction Temperature from Inrush Current

An inrush current flows to electrically charge the output capacitor of the LDO during startup. Even if the current value exceeds the maximum value of the recommended operating range, the over current protection (OCP) circuit limits the amount of current, so there are no problems in operation. Note that it is necessary to make sure that the junction temperature does not exceed 150°C due to over current. This application note explains how to calculate the power consumption from the measured waveforms and calculate the junction temperature from the transient thermal resistance graph.

Calculating the power consumption from the measured waveforms

Since the inrush current is a short-term over current, the junction temperature T_J can be estimated by the following equation using the transient thermal resistance Z_{TH} .

$$T_J = T_A + Z_{TH} \times P \quad [^{\circ}C] \tag{1}$$

 T_A : Ambient temperature [°C]

 Z_{TH} : Transient thermal resistance between junction and ambient environment [°C/W]

P : ICpower consumption [W]

P is the IC power consumption. It can be calculated from the measured waveforms with the approximation equation shown in Equation (2).

$$P \approx \frac{1}{3} (V_{DS1} - V_{DS2}) (I_{D1} - I_{D2}) - \frac{1}{2} I_{D1} (V_{DS1} - V_{DS2}) - \frac{1}{2} V_{DS1} (I_{D1} - I_{D2}) + V_{DS1} I_{D1} [W]$$
(2)

"S" in V_{DS} refers to the source, which represents the input voltage V_{IN} if the output MOSFET is the P-channel type. "D" refers to the drain of MOSFET, which represents the output voltage V_{OUT} . Therefore, V_{DS} is the input-output voltage. V_{DS1} and V_{DS2} represent the start and end voltages, respectively.

 I_D is the current flowing through the output MOSFET, which is the output current I_{OUT} (\approx input current I_{IN}). I_{D1} and I_{D2} represent the start and end currents, respectively.



Figure 1. Measurement circuit

As an example to describe the procedure, we use the waveforms in Figure 2 that are measured with the circuit shown in Figure 1.

- 1. Draw linear trendlines for the V_{OUT} and I_{IN} ($\approx I_{OUT}$) waveforms and read the minimum and maximum values.
- 2. Organize the values.

$$V_{DS1} = V_{IN} - V_{OUT1} = 12 V - 0 V = 12 [V]$$
(3)

$$V_{DS2} = V_{IN} - V_{OUT2} = 12 V - 4.6 V = 7.4 [V]$$
(4)

$$I_{D1} = 0 [A]$$
 (5)

$$I_{D2} = 1.85 [A] \tag{6}$$

3. If $I_{D1} = 0$, Equation (2) can be simplified to Equation (7).

$$P \approx \frac{1}{6} (V_{DS1} + 2 V_{DS2}) I_{D2} \quad [W]$$
(7)

4. Substitute the read values in Equation (7).

$$P \approx \frac{1}{6} (12V + 2 \times 7.4V) \times 1.85A = 8.26 \ [W] \tag{8}$$



Figure 2. Measured waveforms, COUT = 10 µF

Calculating T_J from the transient thermal resistance

Next, calculate the transient thermal resistance from the graph in Figure 3. The waveforms in Figure 2 show that the period of the over current is 34 μ s. In Figure 3, read the transient thermal resistance at 34 μ s. However, use the value at 100 μ s because this is the minimum time on the graph. The transient thermal resistance at 34 μ s is lower than the value at 100 μ s, providing a margin to the design.

Substitute the values collected so far in Equation (1) to calculate the junction temperature. In this example, $60^{\circ}C$ is used as the ambient temperature T_A for the calculation.

$$T_A = 60 \,[^{\circ}\text{C}] \tag{9}$$

$$Z_{TH} = 0.92 \left[{}^{\underline{o}}C/W\right] \tag{10}$$

$$P = 8.26 \, [W] \tag{11}$$

$$T_J = T_A + Z_{TH} \times P = 60 + 0.92 \times 8.26 = 67.6 \,[^{\circ}\text{C}]$$
(12)

The junction temperature is 150°C or less, so there is no problem.

In this way, since the rise in chip temperature is slight when the inrush current flows for a time less than 1 ms, problems with rising temperatures are minimal.

In the measured waveform in Figure 2, the power is consumed in the section where I_{IN} falls from the peak. However, since the power consumption is smaller and the period is shorter compared with the section where the current rises, the calculation is omitted.





Another calculation example

Perform the calculation using the output capacitor of 1,000 μF and a large inrush current as an example.

Figure 4 shows the measured waveforms. Due to a large amount of electric charge in the output capacitor, the output voltage is increased with the over current protection circuit of the IC constantly operated since immediately after the startup.

Follow the procedure described above to perform the calculation.

- 1. Draw linear trendlines for the V_{OUT} and I_{IN} ($\approx I_{OUT}$) waveforms and read the minimum and maximum values.
- 2. Organize the values.

$$V_{DS1} = V_{IN} - V_{OUT1} = 12 V - 0 V = 12 [V]$$
(13)

$$V_{DS2} = V_{IN} - V_{OUT2} = 12 V - 5 V = 7 [V]$$
(14)

$$I_{D1} = 0.76 \ [A] \tag{15}$$

- $I_{D2} = 1.92 \ [A] \tag{16}$
- 3. Substitute the read values in Equation (2).

$$P \approx \frac{1}{3} (V_{DS1} - V_{DS2}) (I_{D1} - I_{D2}) - \frac{1}{2} I_{D1} (V_{DS1} - V_{DS2}) - \frac{1}{2} V_{DS1} (I_{D1} - I_{D2}) + V_{DS1} I_{D1} \approx \frac{1}{3} (12 - 7) (0.76 - 1.92) - \frac{1}{2} \times 0.76 (12 - 7) - \frac{1}{2} \times 12 (0.76 - 1.92) + 12 \times 0.76 \approx 12.25 [W]$$
(17)

4. Read the transient thermal resistance at 3.25 ms from the graph in Figure 5.

$$Z_{TH} = 3.9 \,[^{\circ}\text{C}/W] \tag{18}$$

5. Substitute the values collected so far in Equation (1) to calculate the junction temperature. In this example, 60° C is used as the ambient temperature T_A for the calculation.

$$T_A = 60 \,[^{\circ}\text{C}] \tag{19}$$

$$P = 12.25 \, [W] \tag{20}$$

$$T_J = T_A + Z_{TH} \times P = 60 + 3.9 \times 12.25 = 107.8 \,[^{\circ}\text{C}]$$
(21)

The junction temperature is 150°C or less, so there is no problem.



Figure 4. Measured waveforms, C_{OUT} = 1,000 μ F



JEDEC 1-layer board, copper foil area 49 mm² (footprint)

Application Note

<u>Calculating Power Loss from Measured Waveforms</u>

The approximate equations shown in Equations (2) and (7) are taken from the equations described in case 3 of Table 1 in this application note. Since the waveform of the inrush current is a single pulse, the term " $\Delta t \cdot f$ " in the equations is "1".

Notes	
1)	The information contained herein is subject to change without notice.
2)	Before you use our Products, please contact our sales representative and verify the latest specifica- tions :
3)	Although ROHM is continuously working to improve product reliability and quality, semicon- ductors can break down and malfunction due to various factors. Therefore, in order to prevent personal injury or fire arising from failure, please take safety measures such as complying with the derating characteristics, implementing redundant and fire prevention designs, and utilizing backups and fail-safe procedures. ROHM shall have no responsibility for any damages arising out of the use of our Poducts beyond the rating specified by ROHM.
4)	Examples of application circuits, circuit constants and any other information contained herein are provided only to illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.
5)	The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM or any other parties. ROHM shall have no responsibility whatsoever for any dispute arising out of the use of such technical information.
6)	The Products specified in this document are not designed to be radiation tolerant.
7)	For use of our Products in applications requiring a high degree of reliability (as exemplified below), please contact and consult with a ROHM representative : transportation equipment (i.e. cars, ships, trains), primary communication equipment, traffic lights, fire/crime prevention, safety equipment, medical systems, servers, solar cells, and power transmission systems.
8)	Do not use our Products in applications requiring extremely high reliability, such as aerospace equipment, nuclear power control systems, and submarine repeaters.
9)	ROHM shall have no responsibility for any damages or injury arising from non-compliance with the recommended usage conditions and specifications contained herein.
10)	ROHM has used reasonable care to ensure the accuracy of the information contained in this document. However, ROHM does not warrants that such information is error-free, and ROHM shall have no responsibility for any damages arising from any inaccuracy or misprint of such information.
11)	Please use the Products in accordance with any applicable environmental laws and regulations, such as the RoHS Directive. For more details, including RoHS compatibility, please contact a ROHM sales office. ROHM shall have no responsibility for any damages or losses resulting non-compliance with any applicable laws or regulations.
12)	When providing our Products and technologies contained in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, including without limitation the US Export Administration Regulations and the Foreign Exchange and Foreign Trade Act.
13)	This document, in part or in whole, may not be reprinted or reproduced without prior consent of ROHM.



Thank you for your accessing to ROHM product informations. More detail product informations and catalogs are available, please contact us.

ROHM Customer Support System

http://www.rohm.com/contact/