

## Switching Regulator Series

# Diode Selection Method for Asynchronous Converter

In the design of an asynchronous converter, the selection of the freewheeling diode affects the performance, such as the efficiency of the converter. It is also necessary to consider the risk of heat generation and breakdown. This application note explains the guidelines in selecting the freewheeling diode for asynchronous converters. We hope this will help you select the right components.

### The role of the diode

Asynchronous rectification and synchronous rectification are compared using a buck converter as an example. Figure 1-a shows an asynchronous rectification circuit, and Figure 1-b shows a synchronous rectification circuit.

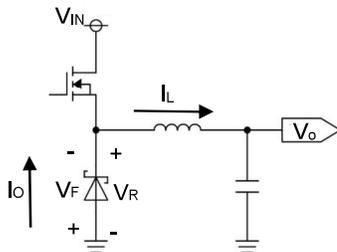


Figure 1-a. Asynchronous Buck Converter

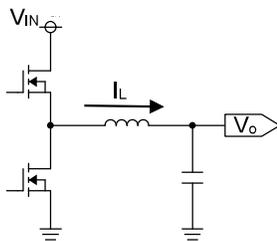


Figure 1-b. Synchronous Buck Converter

The difference between Figure 1-a and 1-b is that the low-side element is a diode for asynchronous rectification, and a MOSFET in synchronous rectification. Both low-side elements perform rectification by supplying the input energy stored in the

inductor when the high-side switch is turned on, to the output side while the high-side switch is off. This output rectifier diode is called freewheeling diode or catch diode.

### Effect of diode characteristics on converter

Since the output voltage increases when the inductor stores a lot of input energy, the ON time (On Duty) of the high-side switch is lengthened with respect to the switching period in order to increase the output voltage. Conversely, when the output voltage is low, the high-side On Duty is small and the low-side On Duty is larger.


At this time, the energy supplied by the inductor is {Output voltage ( $V_O$ ) + Diode forward voltage ( $V_F$ )} x Coil current ( $I_L$ ), but  $V_F$  is a loss. The loss increases as  $V_F$  becomes large, and as the output voltage becomes low, the percentage of loss due to  $V_F$  increases. On the other hand, while the high-side switch is on, it is wanted to store all the input energy in the inductor but at this time, the reverse current ( $I_R$ ) flows through the diode, and the energy leaks. Therefore, low  $V_F$  and low  $I_R$  are ideal, but  $V_F$  and  $I_R$  are inversely proportional. The recommended diode of ROHM's asynchronous converter is the Schottky barrier diode, because of the importance of low  $V_F$ .

Also, from the viewpoint of component assurance of the diode, it is necessary to consider the reverse voltage ( $V_R$ ) applied during the period when the high-side switch is ON and the forward current ( $I_O$ ) that flows when inductor energy is transferred. (These will be explained in later chapters.)

View catalog values for diodes


Table 1 shows the parametric search result (by most relevant representative type name excerpt) of standard Schottky barrier diode in ROHM HP,  $V_F \leq 0.6$  [V],  $I_O \leq 10$  [A]. You can select from the devices in this table.

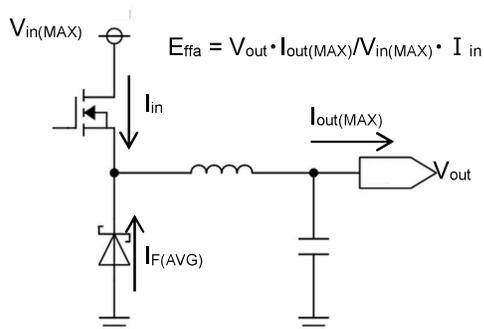Here, we introduce a scheme for selecting parts from the items in Table 1. Figure 2-a/2-b shows the circuit characteristic constants of the buck/boost converter.



$$E_{ffa} = V_{out} \cdot I_{out(MAX)} / V_{in(MAX)} \cdot I_{in}$$

Figure 2-a. Buck Converter

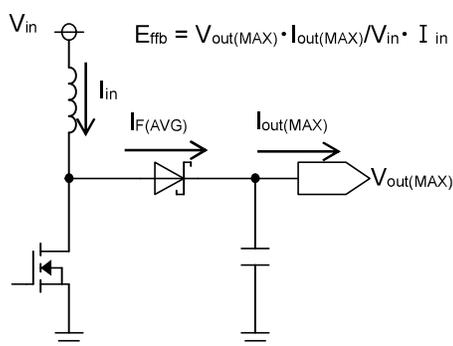

$$E_{ffb} = V_{out(MAX)} \cdot I_{out(MAX)} / V_{in} \cdot I_{in}$$

Figure 2-b. Boost Converter

Table 1. Candidates and Key Characteristics of ROHM Standard Schottky Barrier Diodes

Standard shotokky barrier diode product	Reverse Surge Voltage V <sub>RS</sub> [V]	DC reverse voltage V <sub>R</sub> [V]	Average rectified current I <sub>A</sub> [A]	Forward surge current I <sub>FSM</sub> single [A]	Forward voltage V <sub>F</sub> (Max.) [V]	I <sub>R</sub> @ V <sub>F</sub> [A]	Reverse current I <sub>R</sub> (Max.) [mA]	V <sub>F</sub> @ I <sub>F</sub> [V]
RB050LAM-40	40	40	3	80	0,5	1,5	0,1	40
RB050LAM-60	60	60	3	80	0,52	2	0,1	60
RB051LAM-40	40	20	3	80	0,35	1	0,15	15
RB055LAM-40	40	40	3	70	0,55	1,5	0,1	40
RB056LAM-40	40	40	3	50	0,58	2	0,05	40
RB060LAM-40	40	40	2	80	0,45	1	0,1	40
RB060MM-60	60	60	2	30	0,52	1	0,05	60
RB070MM-30	30	30	1,5	30	0,43	0,5	0,05	30
RB080LAM-30	30	30	5	100	0,51	5	0,15	30
RB081LAM-20	25	20	5	80	0,45	5	0,7	20
RB160LAM-40	40	40	1	50	0,55	1	0,01	6
RB160MM-60	60	60	1	30	0,55	1	0,05	60
RB160VAM-60	60	60	1	3	0,43	0,1	0,04	60
RB161MM-20	25	20	1	30	0,32	0,5	0,7	20
RB162LAM-40	40	40	1	40	0,55	1	0,1	40
RB162MM-40	40	40	1	30	0,55	1	0,1	40
RB215T-60NZ	60	60	20	100	0,58	10	0,6	60
RB400VAM-50	50	40	0,5	3	0,55	0,5	0,03	10
RB411VAM-50	50	20	0,5	3	0,5	0,5	0,03	10
RB500VM-40	45	40	0,1	1	0,45	0,01	0,001	10
RB501VM-40	45	40	0,1	1	0,55	0,1	0,03	10
RB510VM-40	40	40	0,1	0,5	0,48	0,01	0,4	10
RB511VM-40	40	40	0,1	0,5	0,41	0,01	0,004	10
RB520CM-60	60	60	0,1	0,5	0,44	0,01	0,003	60
RB520SM-40	40	40	0,2	1	0,55	0,1	0,01	40
RB520VM-40	40	40	0,2	1	0,39	0,01	0,001	10
RB521SM-30	30	30	0,2	1	0,47	0,2	0,03	10
RB521SM-60	60	60	0,2	1	0,6	0,2	0,1	60
RB521VM-40	40	40	0,2	1	0,3	0,01	0,02	10
RB530CM-60	60	60	0,1	0,2	0,54	0,01	0,001	60
RB531CM-40	40	40	0,1	0,5	0,41	0,01	0,004	10
RB540VM-30	30	30	0,2	1	0,45	0,01	0,0005	10
RB541VM-30	30	30	0,2	1	0,35	0,01	0,01	10
RB550VM-40	40	40	0,2	1	0,51	0,2	0,012	10
RB551VM-40	40	40	0,2	1	0,43	0,2	0,06	10
RB751CM-40	40	30	0,03	0,2	0,37	0,001	0,0005	30
RB751SM-40	40	30	0,03	0,2	0,37	0,001	0,0005	30
RB751VM-40	40	30	0,03	0,2	0,37	0,001	0,0005	30
RBR3LAM40C	40	40	3	45	0,53	3	0,06	30
RBR3LAM40C	40	40	3	75	0,55	3	0,1	40
RBR3LAM60B	60	60	3	75	0,56	3	0,15	60
RBR3MM40B	40	40	3	30	0,58	3	0,1	40
RBR5LAM60A	60	60	5	100	0,55	5	0,25	60
RSX101VAM30	30	30	1	5	0,42	0,7	0,04	5
RSX201LAM30	30	30	2	60	0,44	2	0,15	30
RSX201VAM30	30	30	1,5	8	0,42	1	0,06	5
RSX205LAM30	30	30	2	60	0,49	2	0,2	30
RSX301LAM30	30	30	3	100	0,42	3	0,09	15
RSX501LAM20	25	20	5	100	0,39	3	0,5	20

Items 1) to 4) below are the key characteristics (V<sub>R</sub>, I<sub>O</sub>, V<sub>F</sub>, I<sub>R</sub>) of Schottky barrier diodes in Table 1 that should be considered in order of priority when choosing freewheeling diodes.

1) Forward voltage V<sub>F</sub>

Unless individually recommended, normally select 0.6 [V] or less (Table 1 is already sorted below 0.6 [V]). If a larger voltage is used, the internal elements of the converter IC may be destroyed.

The data sheet of the Schottky barrier diode (SBD) is usually described as a condition of two types of forward current because V<sub>F</sub> varies depending on the forward current. Table 1 shows the larger value (shown as V<sub>F2</sub> etc. in the SBD data sheet). This is because the forward current condition of V<sub>F2</sub> is often close to the I<sub>O</sub> value of 2).

The above situation (in which the forward voltage increases depending on the forward current) also occurs in the protection element in the converter IC, and if the forward voltage of the freewheeling diode is greater than that of the protection element, current may flow and goes through the protection element, and the converter IC may be destroyed.

2) Average rectified current  $I_o$

$$I_o > I_{F(AVG)} \times 1.2 \dots 1.2 \text{ times or more of forward average current } I_{F(AVG)} \text{ flowing in diode}$$

For buck converter,  $I_{F(AVG)}$  is,

$$I_{F(AVG)} = I_{out(MAX)} - I_{in} = I_{out(MAX)} \times \frac{(V_{in(MAX)} - (V_{out}/Eff_a))}{V_{in(MAX)}}$$

For boost converter,  $I_{F(AVG)}$  is,

$$I_{F(AVG)} = I_{out(MAX)} = I_{in} \times Eff_b \times \frac{V_{in}}{V_{out(MAX)}}$$

Keep the peak forward surge current  $I_{FSM}$  lower, including the ripple current.  $I_{FSM}$  is not particularly severe because it is often more than 5 times  $I_o$ . The ripple current is explained in Figure 3 using the symbols in Figure 2 using the buck converter as an example.

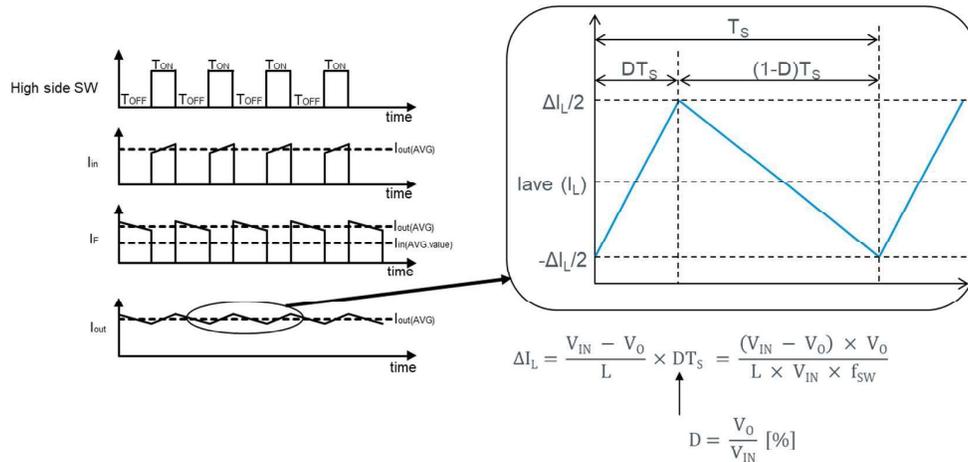


Figure 3. Illustration of Ripple Current

For buck converter, the forward loss  $P_F$  is,

$$P_F = I_{F(AVG)} \times V_F@I_{out(MAX)} = I_{out(MAX)} \times \frac{(V_{in(MAX)} - (V_{out}/Eff_a))}{V_{in(MAX)}} \times V_F@I_{out(MAX)}$$

Similarly, for a boost converter,

$$P_F = I_{in} \times \text{Eff}_b \times \frac{V_{in}}{V_{out(\text{MAX})}} \times V_F @ I_{in}$$

In the case of SBD alone, looking at the data sheet of "RSX301LAW30" in the second row from the bottom of Table 1, there is the following forward characteristic curve.

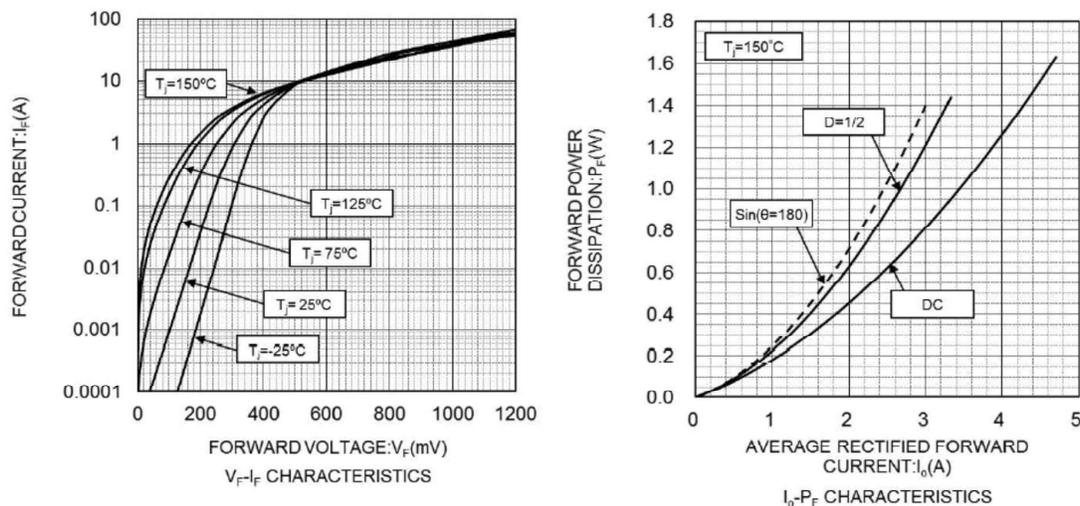


Figure 4. Rohm Schottky Barrier Diode RSX301LAW30 Characteristic Curve for Forward Loss

In 4 Figure,  $T_j = 0.99 [^{\circ}\text{C}]$ , under conditions of DC,  $I_F = 3 [\text{A}]$  is a loss,

$$3 [\text{A}] \times \text{Approx. } 270 [\text{mV}] \text{ (Figure 4 left figure)} = 0.8 [\text{W}] \text{ (Figure 4 right figure)}$$

Interpolate  $T_j$  and Duty conditions (DC: Duty = 100% in the above calculation example) from Figure 4 according to the usage conditions.

3) DC reverse voltage  $V_R$

It must be at least 1.2 times the maximum voltage used in the converter.

For a buck converter,

$$V_R > V_{in(\text{MAX})} \times 1.2$$

For boost converter,

$$V_R > V_{out(\text{MAX})} \times 1.2$$

Keep the peak reverse voltage  $V_{RM}$  lower, including switching spikes. When  $V_{RM} = V_R$ , the peak reverse voltage  $V_{RM}$  must be kept below  $V_R$ , including spike noise.

4) Reverse current  $I_R$

Choose the smallest possible item from those that have cleared items 1) to 3) above. However, SBD with small  $V_F$  tend to have large  $I_R$ . Since  $I_R$  vary drastically with respect to the temperature, care must be taken in the design of the equipment which high-temperature operation is required. The reverse characteristic curve of “RSX301LAM30” is as follows.

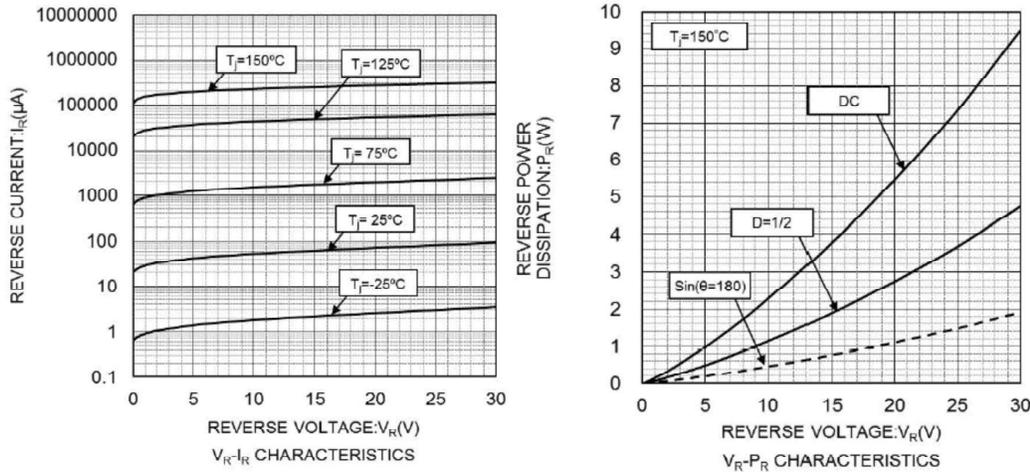


Figure 5. Rohm Schottky Barrier Diode RSX301LAW30 Characteristic Curve for Reverse Loss

Similarly, in Figure 5,  $T_j = 150 [^{\circ}C]$ , under the conditions of DC,  $P_R$  is about 9 [W], and  $P_F$  is equivalent to 10 times. For the loss of free-wheeling diode,  $P_F$  and  $P_R$  must be estimated in consideration of the operating temperature, along with the consideration of the Duty ratio.

## Main target products and recommended diodes

Table 2 lists the major asynchronous converters from ROHM HP and lists the recommended diodes listed in the converter IC datasheet. Many of the recommended diodes listed in the converter IC datasheet are “not recommended for new design”. As of '19/8, recommended products and their key characteristics are added. Although the model name of the datasheet recommended product and the current recommended product are different, the element characteristics remain unchanged.

Table 2. Targeted Asynchronous Converters in this Document and Recommended SBD (as of '19/ 8)

Converter products	Grade	Recommended Di in data sheet	New recommended Di ('19/8 current)	$V_{RM}[V]$	$V_F[V]$	$I_F[A]$	$I_{FSM}[A]$	$V_F(\text{Max})[V]$	$I_F(\text{Max})[\mu A]$
BD8152FVM	Standard	RB161M-20	RB161MM-20	25	20	1	30	0.32	700
BD8158FVM	Standard	RB161M-20	RB161MM-20	25	20	1	30	0.35	700
BD8311NUV	Standard	RSX201L-30	RSX201LAM30	30	30	2	60	0.44	150
BD8314NUV	Standard	RSX201L-30	RSX201LAM30	30	30	2	60	0.44	150
BD8316GWL	Standard	RSX101VA-30	RSX101VAM30	30	30	1	5	0.42	40
BD8317GWL	Standard	RB521S-30	RB521SM-30	-	30	0.2	1	0.47	30
BD9035AEFV-C	Automotive	RB225NS-40	RB225NS-40XX	40	40	30	100	0.63	50
BD9060F-C	Automotive	RB095B-40	RB095BM-40XX	45	40	6	45	0.55	100
BD9060HFP-C	Automotive	RB095B-40	RB095BM-40XX	45	40	6	45	0.55	100
BD90610EFJ-C	Automotive	RB055L-40TF	RB055LAM-40XX	40	40	3	70	0.55	100
BD90620EFJ-C	Automotive	RB095BM-40FH	RB095BM-40XX	45	40	6	50	0.55	100
BD90620HFP-C	Automotive	RB095BM-40FH	RB095BM-40XX	45	40	6	50	0.55	100
BD90640EFJ-C	Automotive	RB095BM-40FH	RB095BM-40XX	45	40	6	50	0.55	100
BD90640HFP-C	Automotive	RB095BM-40FH	RB095BM-40XX	45	40	6	50	0.55	100
BD9227F	Standard	RB060MM-30	RB060MM-30	30	30	2	55	0.45	50
BD9701CP-V5	Standard	RB050LA-40	RBR3LAM40C	40	40	3	75	0.55	100
BD9701FP	Standard	RB050LA-40	RBR3LAM40C	40	40	3	75	0.55	100
BD9701T	Standard	RB050LA-40	RBR3LAM40C	40	40	3	75	0.55	100
BD9701T-V5	Standard	RB050LA-40	RBR3LAM40C	40	40	3	75	0.55	100
BD9702CP-V5	Standard	RB050LA-40	RBR3LAM40C	40	40	3	75	0.55	100
BD9702T	Standard	RB050LA-40	RBR3LAM40C	40	40	3	75	0.55	100
BD9702T-V5	Standard	RB050LA-40	RBR3LAM40C	40	40	3	75	0.55	100
BD9703CP-V5	Standard	RB050LA-40	RBR3LAM40C	40	40	3	75	0.55	100
BD9703FP	Standard	RB050LA-40	RBR3LAM40C	40	40	3	75	0.55	100
BD9703T	Standard	RB050LA-40	RBR3LAM40C	40	40	3	75	0.55	100
BD9703T-V5	Standard	RB050LA-40	RBR3LAM40C	40	40	3	75	0.55	100
BD9778F	Automotive	RB050L-40	RBR3LAM40CXX	40	40	3	75	0.55	1000
BD9778HFP	Automotive	RB050L-40	RBR3LAM40CXX	40	40	3	75	0.55	1000
BD9859EFJ	Standard	RSX301LA-30	RSX301LAM30	30	30	3	100	0.42	90
BD9870FPS	Standard	RB050LA-40	RBR3LAM40C	40	40	3	75	0.55	100
BD9873CP-V5	Standard	RB050LA-40	RBR3LAM40C	40	40	3	75	0.55	100
BD9874CP-V5	Standard	RB050LA-40	RBR3LAM40C	40	40	3	75	0.55	100
BD9E151NUX	Standard	RSX101VA-30	RSX101VAM30	30	30	1	5	0.42	40
BD9G101G	Standard	RB060M-60	RB060MM-60	60	60	2	30	0.52	50
BD9G102G-LB	Industrial	RB060MM-60	RB060MM-60	60	60	2	30	0.52	50
BD9G201EFJ-LB	Industrial	RB050LAM-60TFTR	RB050LAM-60TFTR	60	60	3	80	0.56	100
BD9G201EFJ-M	Automotive	RB050LAM-60TFTR	RB050LAM-60TFTR	60	60	3	80	0.56	100
BD9G341AEFJ	Standard	RB095B-90	RB095BGE-90	90	90	6	45	0.75	150
BD9G341AEFJ-LB	Industrial	RB095B-90	RB095BGE-90	90	90	6	45	0.75	150
BD9G401EFJ-M	Automotive	RB050L-60	RBR3LAM60BXX	60	60	2	75	0.56	150

In the table, “XX” at the end of the model name in the “Recommended Di” column is described as a symbol indicating the name of an on-vehicle product, and contains two or more letters (example: TF).

**History**

Date	Revision	Changes
2019.11.20	001	New Release

## Notes

- 1) The information contained herein is subject to change without notice.
- 2) Before you use our Products, please contact our sales representative and verify the latest specifications :
- 3) Although ROHM is continuously working to improve product reliability and quality, semiconductors can break down and malfunction due to various factors.  
Therefore, in order to prevent personal injury or fire arising from failure, please take safety measures such as complying with the derating characteristics, implementing redundant and fire prevention designs, and utilizing backups and fail-safe procedures. ROHM shall have no responsibility for any damages arising out of the use of our Products beyond the rating specified by ROHM.
- 4) Examples of application circuits, circuit constants and any other information contained herein are provided only to illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.
- 5) The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM or any other parties. ROHM shall have no responsibility whatsoever for any dispute arising out of the use of such technical information.
- 6) The Products specified in this document are not designed to be radiation tolerant.
- 7) For use of our Products in applications requiring a high degree of reliability (as exemplified below), please contact and consult with a ROHM representative : transportation equipment (i.e. cars, ships, trains), primary communication equipment, traffic lights, fire/crime prevention, safety equipment, medical systems, servers, solar cells, and power transmission systems.
- 8) Do not use our Products in applications requiring extremely high reliability, such as aerospace equipment, nuclear power control systems, and submarine repeaters.
- 9) ROHM shall have no responsibility for any damages or injury arising from non-compliance with the recommended usage conditions and specifications contained herein.
- 10) ROHM has used reasonable care to ensure the accuracy of the information contained in this document. However, ROHM does not warrants that such information is error-free, and ROHM shall have no responsibility for any damages arising from any inaccuracy or misprint of such information.
- 11) Please use the Products in accordance with any applicable environmental laws and regulations, such as the RoHS Directive. For more details, including RoHS compatibility, please contact a ROHM sales office. ROHM shall have no responsibility for any damages or losses resulting non-compliance with any applicable laws or regulations.
- 12) When providing our Products and technologies contained in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, including without limitation the US Export Administration Regulations and the Foreign Exchange and Foreign Trade Act.
- 13) This document, in part or in whole, may not be reprinted or reproduced without prior consent of ROHM.



Thank you for your accessing to ROHM product informations.  
More detail product informations and catalogs are available, please contact us.

**ROHM Customer Support System**

<http://www.rohm.com/contact/>