

ROHM Switching Regulator Solutions

# Evaluation Board for ROHM's BD9109FVM Synchronous Buck DC/DC Converter with Integrated FET

BD9109FVMEVK-101 (3.3V | 0.8A Output)

USAP58-A-0004

• **Introduction**

This application note will explain the steps necessary to operate and evaluate ROHM's BD9109FVM synchronous buck DC/DC converter using the BD9109FVMEVK-101 evaluation board. Component selection, board layout recommendations, operating procedures, and application data are included.

• **Description**

This evaluation board has been specifically developed to evaluate the BD9109FVM synchronous buck DC/DC converter with integrated 350mΩ Pch and 250mΩ Nch MOSFETs. Features include an input voltage range of 4.5V to 18.0V, 3.3V output, and a switching frequency of 1MHz. Multiple protection functions are also built in, including a soft start circuit that prevents inrush current during startup, UVLO (Under Voltage Lock Out), TSD (Thermal Shutdown), OCP (Over Current Protection), and timer latch short-circuit protection. An EN pin allows for simple ON/OFF control to reduce standby current consumption, while current mode PWM provides fast response to sudden load changes.

• **Applications**

Power supplies for ICs, including DSPs, MCUs, and ASICs

• **Evaluation Board Operating Limits and Absolute Maximum Ratings**

Parameter	Symbol	Limit			Unit	Conditions
		MIN	TYP	MAX		
<b>Supply Voltage</b>						
	BD9109FVM	V <sub>CC</sub>	4.5	5	5.5	V
<b>Output Voltage / Current</b>						
	BD9109FVM	V <sub>OUT</sub>	3.234	3.300	3.366	V
		I <sub>OUT</sub>	-	-	0.8	A

• **Evaluation Board**

Below is an image of the BD9109FVMEVK-101 evaluation board.

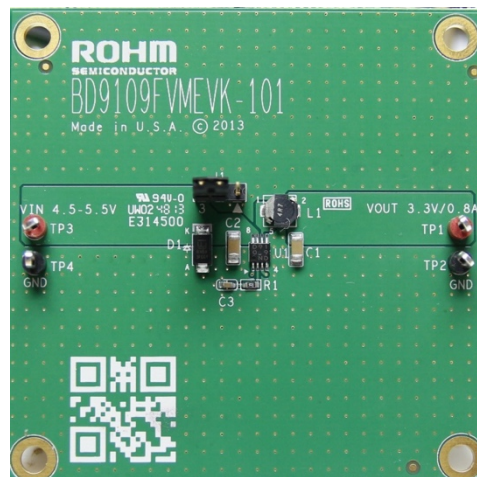


Fig 1: BD9109FVMEVK-101 Evaluation Board

● Board Schematic

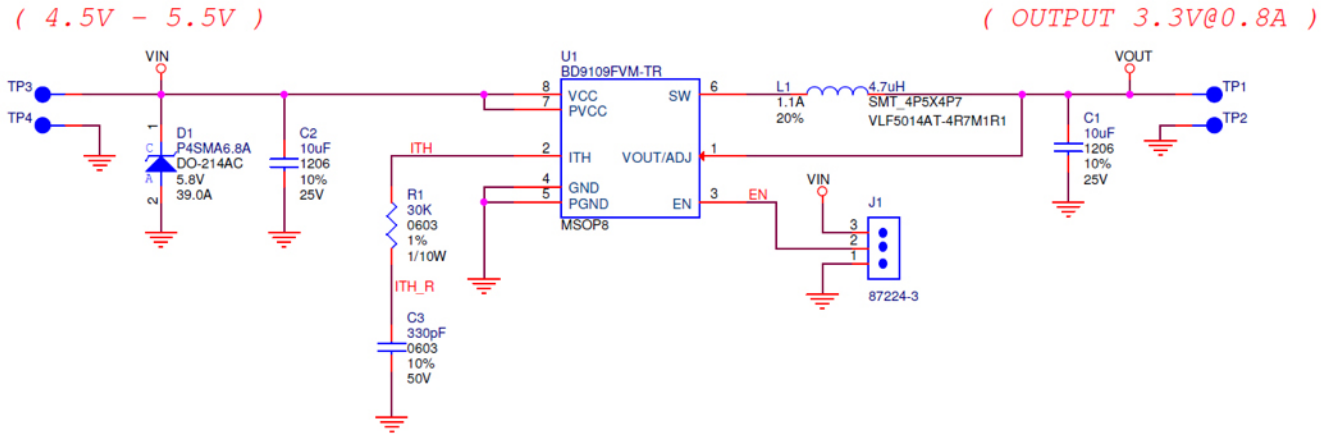


Fig 2: BD9109FVMEVK-101 Evaluation Board Schematic

● Board I/O

Below is a reference application circuit showing the inputs  $V_{IN}$ , EN and output  $V_{OUT}$ .

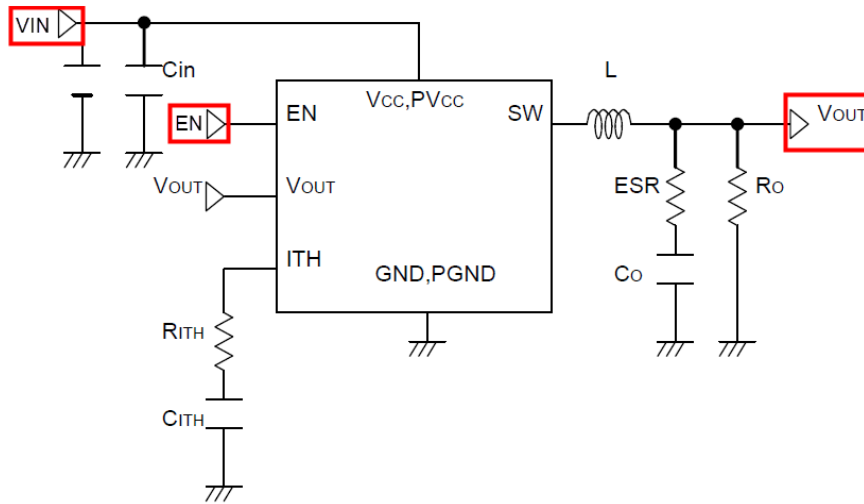


Fig 3: Evaluation Board I/O

● Operating Procedures

1. Connect the power supply's GND terminal to GND test point TP4 on the evaluation board.
2. Connect the power supply's  $V_{CC}$  terminal to  $V_{IN}$  test point TP3 on the evaluation board. This will provide  $V_{IN}$  to the IC U1. Please note that  $V_{CC}$  should be in the range from 4.5V to 5.5V.
3. Check that the shunt jumper J1 is in the ON position (connect Pin 2 to Pin 3, the EN pin of IC of U1 is pulled high as a default).
4. Now the output voltage  $V_{OUT}$  (+3.3V) can be measured at test point TP1 on the evaluation board with a load attached. The load can be increased up to 0.8A MAX.

• Reference Application Data

The following are graphs of the hot plugging test, quiescent current, efficiency, load response, and output voltage ripple response of the BD9109FVMEVK-101 evaluation board.

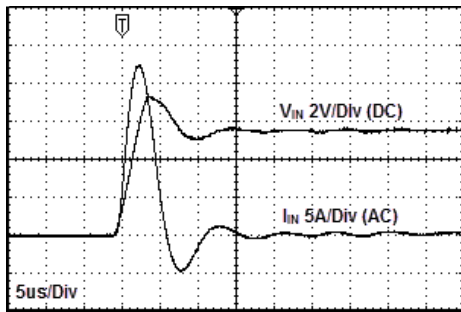


Fig 4: Hot Plug-in Test with Zener Diode SMAJ5.0A,  $V_{IN}=5.5V$ ,  $V_{OUT}=3.3V$ ,  $I_{OUT}=0.8A$

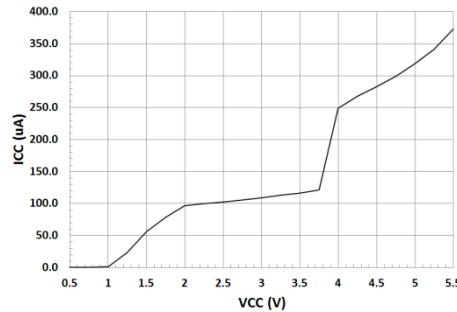


Fig 5: Circuit Current vs. Power Supply Voltage (Temp=25°C)

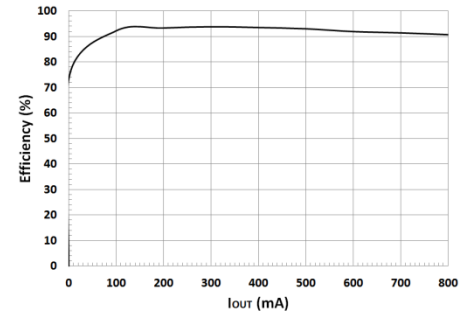


Fig 6: Electric Power Conversion Rate ( $V_{OUT}=3.3V$ )

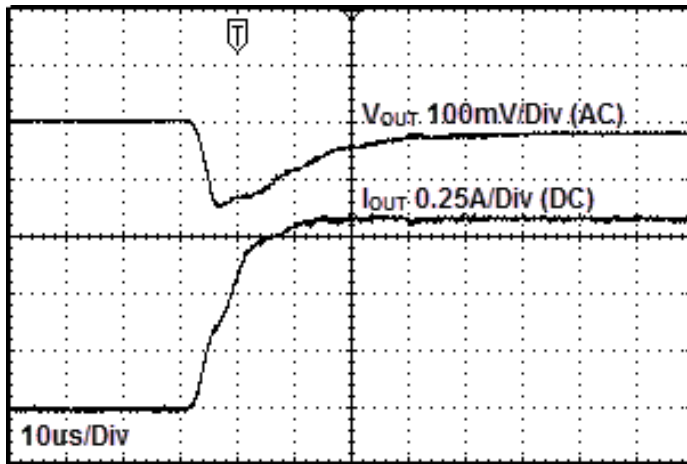


Fig 7: Load Response Characteristics ( $V_{IN}=5V$ ,  $V_{OUT}=3.3V$ ,  $L=4.7\mu H$ ,  $C_{OUT}=10\mu F$ ,  $I_{OUT}=0A \rightarrow 0.8A$ )

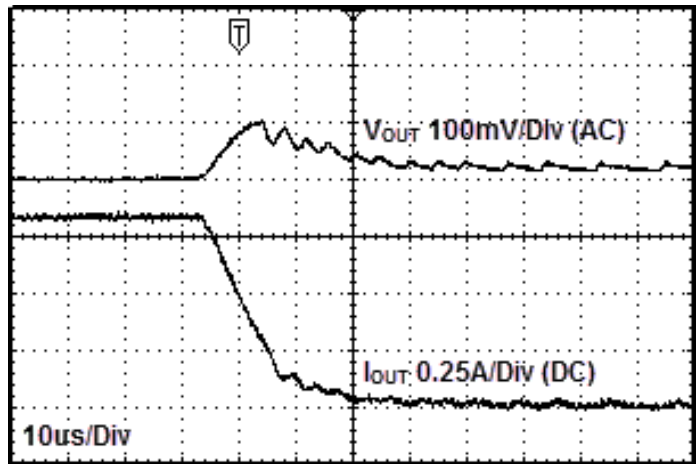


Fig 8: Load Response Characteristics ( $V_{IN}=5V$ ,  $V_{OUT}=3.3V$ ,  $L=4.7\mu H$ ,  $C_{OUT}=10\mu F$ ,  $I_{OUT}=0.8A \rightarrow 0A$ )

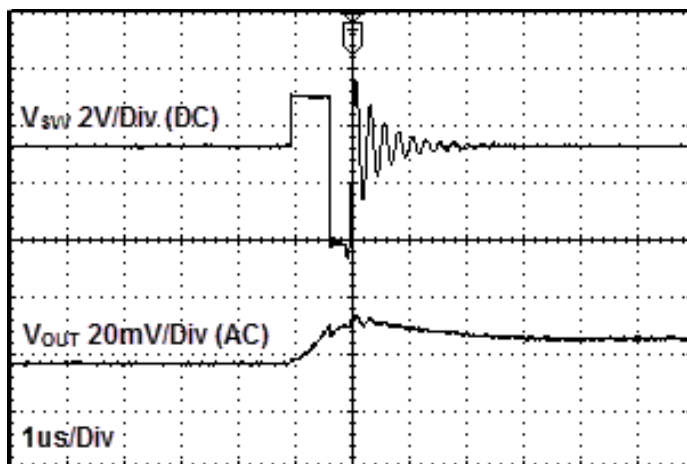


Fig 9: Output Voltage Ripple Response Characteristics ( $V_{IN}=5V$ ,  $V_{OUT}=3.3V$ ,  $L=4.7\mu H$ ,  $C_{OUT}=10\mu F$ ,  $I_{OUT}=0A$ )


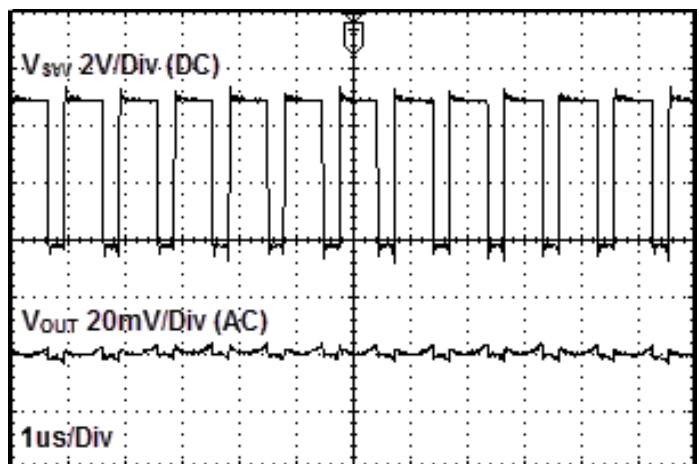


Fig 10: Output Voltage Ripple Response Characteristics ( $V_{IN}=5V$ ,  $V_{OUT}=3.3V$ ,  $L=4.7\mu H$ ,  $C_{OUT}=10\mu F$ ,  $I_{OUT}=0.8A$ )

**Evaluation Board Layout Guidelines**


Below are guidelines that have been tested and recommended for BD9109FVM designs.

Layout is a critical element of good power supply design. There are several signal paths that conduct fast-changing currents or voltages that can interact with stray inductances and parasitic capacitances to generate noise or degrade power supply performance. To help eliminate these problems, the  $V_{CC}$  pin should be bypassed to ground with a low ESR ceramic bypass capacitor with B dielectric.

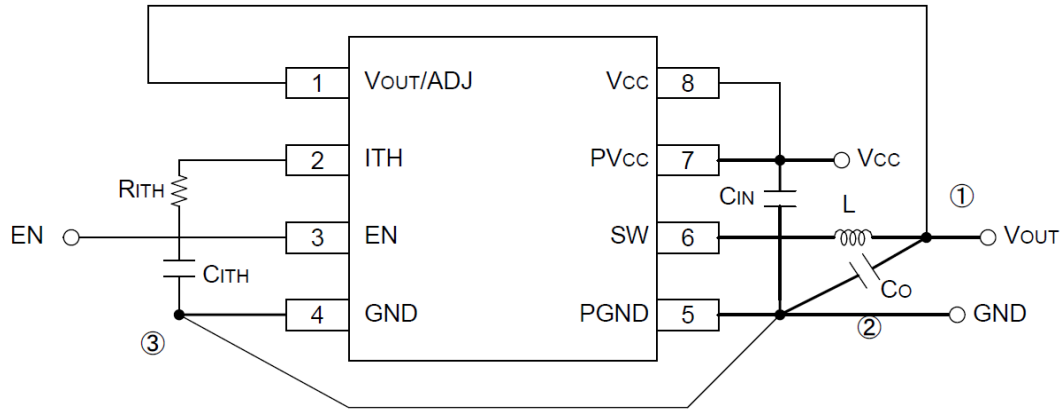

**Fig 11: BD9109FVM Layout Diagram**

- ① For the areas drawn with a heavy line, use a thick conductor pattern and make it as short as possible.
- ② Lay out the input ceramic capacitor  $C_{IN}$  closer to the pins PVCC and PGND and the output capacitor  $C_o$  closer to the PGND pin.
- ③ Connect  $C_{ITH}$  and  $R_{ITH}$  between the pins ITH and GND as cleanly as possible with the least amount of wiring.

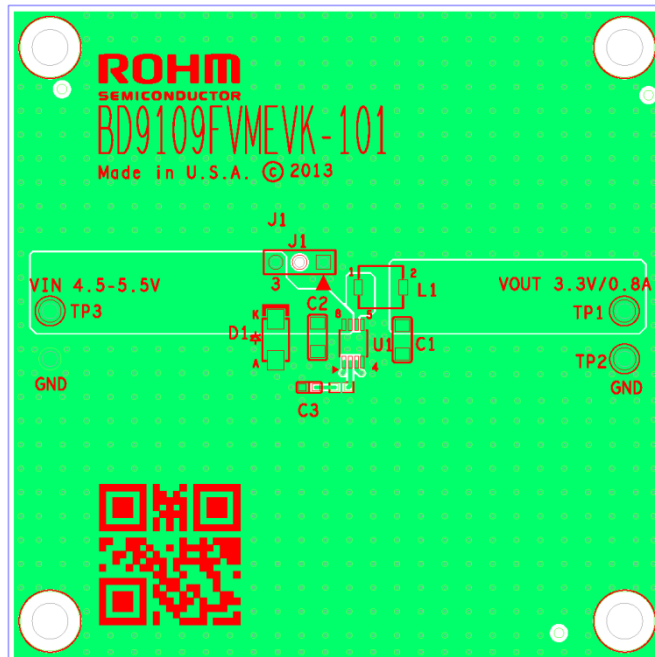

**Fig 12: BD9109FVMEVK-101 PCB Layout**

## • Application Circuit Component Selection

### 1. Inductor (L)

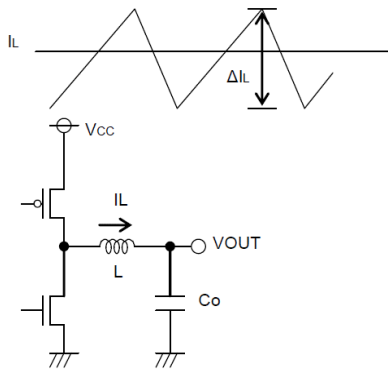


Fig 13: Output Ripple Current

The inductance has a significant effect on the output ripple current.

As seen in the equation (1) below, the ripple current decreases as the inductor and/or switching frequency increases.

$$\Delta I_L = \frac{(V_{CC} - V_{OUT}) \times V_{OUT}}{L \times V_{CC} \times f} \quad [A] \quad (1)$$

The appropriate ripple current at output should be 30% of the maximum output current.

$$\Delta I_L = 0.3 \times I_{OUT\ MAX} \quad [A] \quad (2)$$

$$L = \frac{(V_{CC} - V_{OUT}) \times V_{OUT}}{\Delta I_L \times V_{CC} \times f} \quad [H] \quad (3)$$

(Where  $\Delta I_L$  is the Output Ripple Current and  $f$  is the Switching Frequency)

- \* Current exceeding the current rating of the inductor will result in magnetic saturation of the inductor, decreasing efficiency. The inductor must be selected to allow sufficient margin so that the peak current does not exceed the rated current of the coil.

For example, if  $V_{CC}=5V$ ,  $V_{OUT}=3.3V$ ,  $f=1MHz$ , and  $\Delta I_L=0.3 \times 0.8A=0.24A$ :

$$L = \frac{(5-3.3) \times 3.3}{0.24 \times 5 \times 1M} = 4.675[\mu H] \rightarrow 4.7[\mu H]$$

- \* Select an inductor with low resistance component (such as DCR and ACR) to minimize inductor loss and improve efficiency.

### 2. Output Capacitor (Co)

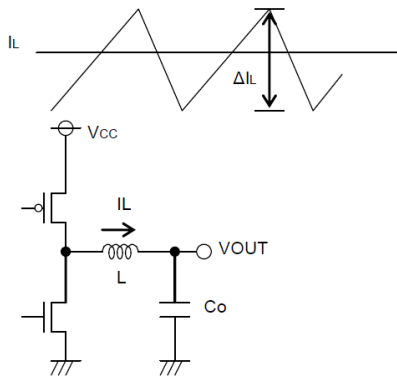


Fig 14: Output Capacitor

The output capacitor should be selected taking into consideration the output voltage stability region and the equivalent series resistance required to smooth the ripple voltage. The output ripple voltage is determined by:

$$\Delta V_{OUT} = \Delta I_L \times ESR \quad [V] \quad (4)$$

(Where  $\Delta I_L$  is the Output Ripple Current and ESR is the Equivalent Series Resistance of the output capacitor)

- \* The capacitor rating should be determined to allow sufficient margin against output voltage. The lower the ESR the lower the output ripple voltage.

As the output rise time must be set to fall within the soft-start time, the capacitance of the output capacitor should be calculated taking into account the conditions of the equation (5) below:

$$C_O \leq \frac{T_{SS} \times (I_{LIMIT} - I_{OUT})}{V_{OUT}} \quad [F] \quad (5)$$

[Where  $t_{SS}$  is the Soft Start time and  $I_{LIMIT}$  is the Overcurrent Detection level (2A typ.)]

For instance, if  $V_{OUT}=3.3V$ ,  $I_{OUT}=0.8A$ , and  $T_{SS}=1ms$ :

$$C_O \leq \frac{1m \times (2 - 0.8)}{3.3} = 364[\mu F]$$

Please note that inappropriate capacitance may cause problems during startup. A 10 $\mu F$  to 100 $\mu F$  ceramic capacitor is recommended.

### 3. Input Capacitor (Cin)

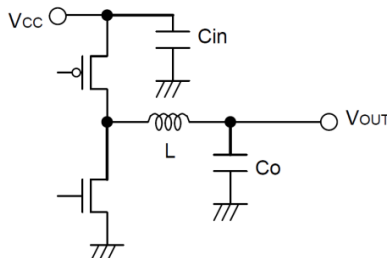


Fig 15: Input Capacitor

A low ESR input capacitor with sufficient size to handle large ripple current in order to prevent large transient voltages is required. The ripple current  $I_{RMS}$  can be calculated by:

$$I_{RMS} = I_{OUT} \times \frac{\sqrt{V_{OUT}(V_{CC} - V_{OUT})}}{V_{CC}} \quad [A] \quad (6)$$

< Worst Case >  $I_{RMS(max)}$


When  $V_{CC}$  is twice  $V_{OUT}$ ,  $I_{RMS} = \frac{I_{OUT}}{2}$

If  $V_{CC}=5V$ ,  $V_{OUT}=3.3V$ , and  $I_{OUT\ max}=0.8A$ ,


$$I_{RMS} = 0.8 \times \frac{\sqrt{3.3(5-3.3)}}{5} = 0.38[A]$$

Therefore, a low ESR 10uF/10V ceramic capacitor is recommended to reduce ESR loss of the input capacitor to improve efficiency.

**4. Phase Compensation Circuit  $R_{ITH}$ ,  $C_{ITH}$**

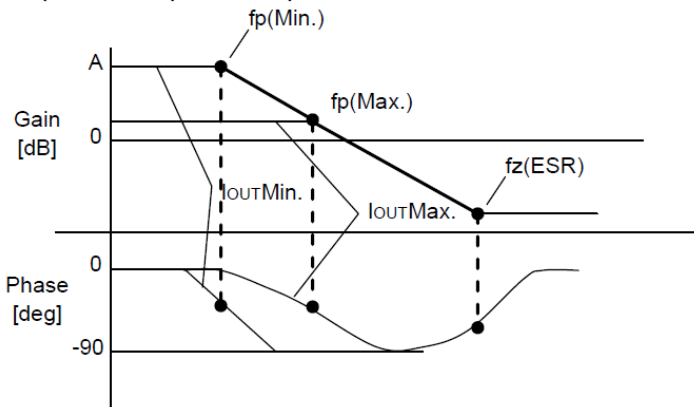

**Fig 16: Open Loop Gain Characteristics**

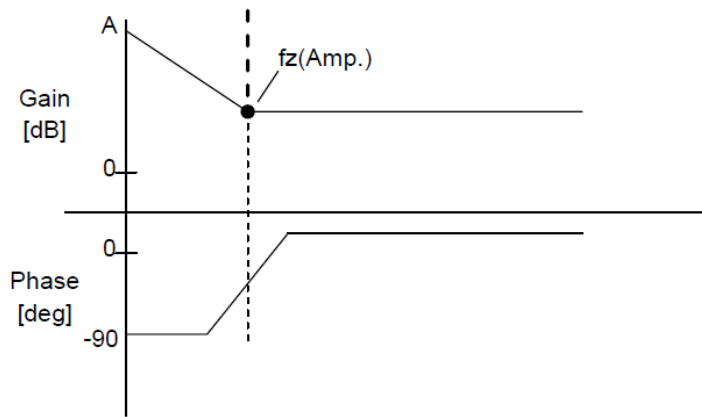

**Fig 17: Error Amp Phase Compensation Characteristics**

With current mode control, since the inductor current is restricted, a pole (phase lag) appears in the low-frequency region due to the CR filter made up of an output capacitor and load resistor, while a zero (phase lead) appears in the high-frequency region due to the output capacitor and ESR. Compensation in order to cancel the pole of the power amplifier can easily be achieved by adding a zero point using a C and R at the error amp output as described below.

$$f_p = \frac{1}{2\pi \times R_o \times C_o}$$

$$f_z(\text{ESR}) = \frac{1}{2\pi \times \text{ESR} \times C_o}$$

Pole at the power amplifier

When the output current decreases, the load resistance  $R_o$  increases and the pole frequency is reduced.

$$f_p(\text{Min.}) = \frac{1}{2\pi \times R_{o\text{max}} \times C_o} \text{ [Hz]} \leftarrow \text{At lighter loads}$$

$$f_p(\text{Max.}) = \frac{1}{2\pi \times R_{o\text{min}} \times C_o} \text{ [Hz]} \leftarrow \text{At heavier loads}$$

Zero at the power amplifier


Increasing the capacitance of the output capacitor reduces the pole frequency while the zero frequency does not change. (This is because when the capacitance doubles, the capacitor ESR is reduced by half.)

$$f_z(\text{Amp}) = \frac{1}{2\pi \times R_{ITH} \times C_{ITH}}$$

Stable feedback loop can be achieved by canceling the pole  $f_p(\text{Min.})$  produced by the output capacitor and load resistance with the CR zero correction of the error amplifier.

$$f_x(\text{Amp}) = f_p(\text{Min})$$

$$\rightarrow \frac{1}{2\pi \times R_{ITH} \times C_{ITH}} = \frac{1}{2\pi \times R_{o\text{max}} \times C_o}$$

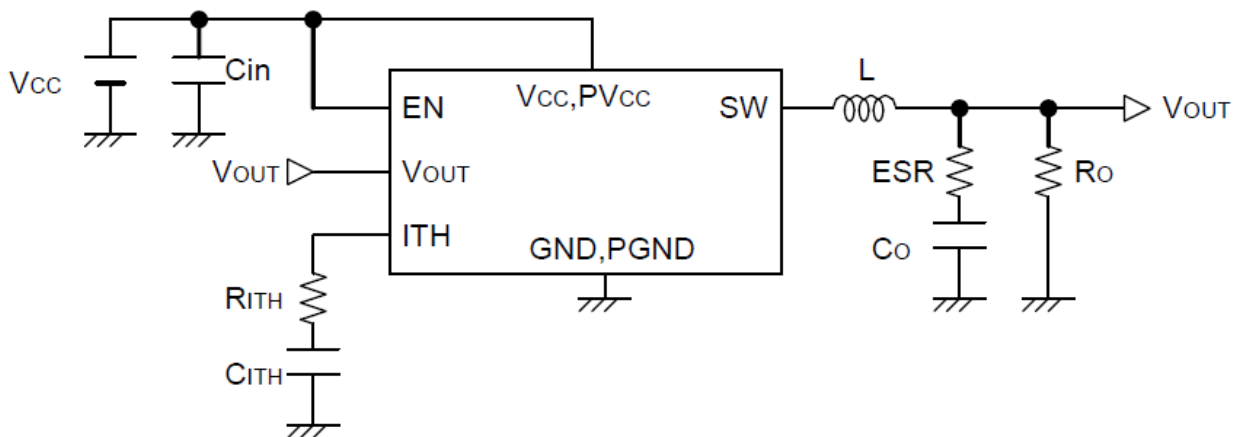

**Fig 18: Typical Application Circuit**

- **Evaluation Board BOM**

Below is a table showing the bill of materials. Part numbers and supplier references are also provided.

No.	Qty.	Ref	Description	Manufacturer	Part Number
1	2	C1,C2	CAP CER 10UF 25V 20% X5R 1206	Murata	GRM31CR61E106MA12L
2	1	C3	CAP CER 330PF 50V 10% X7R 0603	Murata	GRM188R71H331KA01D
3	1	D1	DIODE TVS 400W 6.8V UNI 5% SMD	Littelfuse	P4SMA6.8A
4	1	J1	CONN HEADER VERT .100 3POS 15AU	TE Connectivity	87224-3
5	1	L1	INDUCTOR POWER 4.7UF 1.1A SMD	TDK Corporation	VLF5014AT-4R7M1R1
6	1	R1	RES 30K OHM 1/10W 1% 0603 SMD	Rohm	MCR03ERTF3002
7	2	TP1,TP3	TEST POINT PC MULTI PURPOSE RED	Keystone Electronics	5010
8	2	TP2,TP4	TEST POINT PC MULTI PURPOSE BLK	Keystone Electronics	5011
9	1	U1	IC REG BUCK SYNC 3.3V 0.8A 8MSOP	ROHM	BD9109FVM-TR
10	1		Shunt jumper for header J1 (item #4), CONN SHUNT 2POS GOLD W/HANDLE	TE Connectivity	881545-1

## Notes

No copying or reproduction of this document, whole or in part, is permitted without the consent of ROHM Co., Ltd.

The contents specified herein are subject to change without notice.

The information contained in this document are for the purpose of introducing ROHM products (hereinafter 'Products'). When using any such Products, please be sure to refer to the specifications, which can be obtained from ROHM upon request.

Examples of application circuits, circuit constants and any other information contained herein illustrate the standard usage and operations of the Products, and peripheral conditions must be taken into account when designing circuits for mass production.

Great care was taken to ensure the accuracy of the information specified in this document. However, ROHM shall bear no responsibility for any damages incurred from inaccuracies or the misprint of information.

The technical information specified herein is intended only to show the typical functions and examples of application circuits for the Products. ROHM does not grant, either explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM and other parties. Furthermore, ROHM shall bear no responsibility whatsoever for any disputes arising from the use of such technical information.

The Products specified in this document are intended to be used with general-use electronic equipment or devices (such as audio visual equipment, office automation equipment, communication devices, electronic appliances, and gaming devices).

The Products specified in this document are not designed to be radiation tolerant.

While ROHM makes every effort to enhance the quality and reliability of its Products, Products may fail or malfunction for a variety of reasons.

Please be sure to implement safety measures to guard against the possibility of physical injury, fire, or any other damage that may arise due to Product failure, such as derating, redundancy, fire control, and fail-safe designs. ROHM shall bear no responsibility whatsoever for the use of any Product outside of the prescribed scope or not in accordance with the instruction manual.

The Products are not designed or manufactured to be used with any equipment, device, or system which requires an extremely high level of reliability, the failure or malfunction of which may result in a direct threat to human life or create a risk of human injury (such as medical instruments, transportation equipment, aerospace machinery, nuclear reactor controllers, fuel controllers, or other safety device). ROHM shall bear no responsibility in any way for the use of any Products for the above special purposes. If a Product is intended to be used for any such special purpose, please contact a ROHM sales representative before purchasing.

If intending to export or ship overseas any Product or technology specified herein that are controlled under the Foreign Exchange and Foreign Trade Law, it is necessary to obtain a license or permit under the applicable Law.



Thank you for your interest in ROHM products.  
Please contact us for additional information and product catalogs.

## ROHM Customer Support System

<http://www.rohm.com/contact/>