


## Switching Regulator Series

# BD9E302EFJ Reference Circuit

IC Product Name	BD9E302EFJ
Topology	Buck (Step-Down) Switching Regulator
Type	Non-Isolation

	Input	Output
1	7.0V to 23V	3.3V, 3A
2	7.2V to 28V	5.0V, 3A

Typical Application Circuit

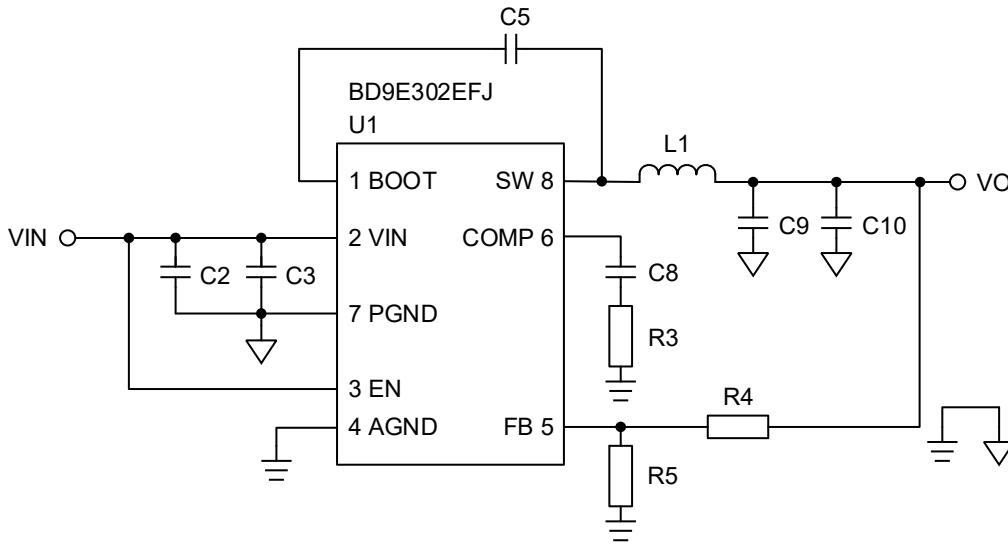

EN pin setting (3-pin)

Terminal state	IC operation
2.5V~VIN	Normal operation
GND~0.8V	Power down

Output voltage setting

$$V_{OUT} = \frac{R_4 + R_5}{R_5} \times 0.8 [V]$$

Input/output voltage conditions are required to satisfy the following equations:

$$V_{OUT} = (V_{IN} \times 0.143)V \sim (V_{IN} \times 0.7)V$$

$$(V_{IN} \times 0.143) \geq 1.0V$$

## Bill of Materials

1.  $V_O=3.3V$  ( $V_{IN}=7.0V$  to  $23V$ )

Count	Reference Designator	Type	Value	Description	Manufacturer Part Number	Manufacturer	Configuration (mm)
1	C2	Ceramic Capacitor	10 $\mu$ F	50V, X5R, $\pm$ 10%	GRM32ER61H106KA12	MURATA	3225
1	C3	Ceramic Capacitor	0.1 $\mu$ F	50V, X5R, $\pm$ 20%	GRM155R61H104ME14	MURATA	1005
1	C5	Ceramic Capacitor	0.1 $\mu$ F	25V, X5R, $\pm$ 20%	GRM155R61E104MA87	MURATA	1005
1	C8	Ceramic Capacitor	6800pF	25V, X7R, $\pm$ 10%	GRM155R71E682KA01	MURATA	1005
2	C9, C10	Ceramic Capacitor	22 $\mu$ F	6.3V, X5R, $\pm$ 20%	GRM32DR60J226MA01	MURATA	3225
1	L1	Inductor	3.3 $\mu$ H	See the recommended inductor list of separate volume.			
1	R3	Resistor	6.8k $\Omega$	0.063W, 50V, 5%	MCR01MZPJ682	ROHM	1005
1	R4	Resistor	75k $\Omega$	0.063W, 50V, 1%	MCR01MZPF7502	ROHM	1005
1	R5	Resistor	24k $\Omega$	0.063W, 50V, 1%	MCR01MZPF2402	ROHM	1005
1	U1	IC	-	Buck DC/DC Converter	BD9E302EFJ	ROHM	HTSOP-J8

2.  $V_O=5.0V$  ( $V_{IN}=7.2V$  to  $28V$ )

Count	Reference Designator	Type	Value	Description	Manufacturer Part Number	Manufacturer	Configuration (mm)
1	C2	Ceramic Capacitor	10 $\mu$ F	50V, X5R, $\pm$ 10%	GRM32ER61H106KA12	MURATA	3225
1	C3	Ceramic Capacitor	0.1 $\mu$ F	50V, X5R, $\pm$ 20%	GRM155R61H104ME14	MURATA	1005
1	C5	Ceramic Capacitor	0.1 $\mu$ F	25V, X5R, $\pm$ 20%	GRM155R61E104MA87	MURATA	1005
1	C8	Ceramic Capacitor	6800pF	25V, X7R, $\pm$ 10%	GRM155R71E682KA01	MURATA	1005
2	C9, C10	Ceramic Capacitor	22 $\mu$ F	16V, X5R, $\pm$ 20%	GRM32ER61C226ME20	MURATA	3225
1	L1	Inductor	4.7 $\mu$ H	See the recommended inductor list of separate volume.			
1	R3	Resistor	10k $\Omega$	0.063W, 50V, 5%	MCR01MZPJ103	ROHM	1005
1	R4	Resistor	430k $\Omega$	0.063W, 50V, 1%	MCR01MZPF4303	ROHM	1005
1	R5	Resistor	82k $\Omega$	0.063W, 50V, 1%	MCR01MZPF8202	ROHM	1005
1	U1	IC	-	Buck DC/DC Converter	BD9E302EFJ	ROHM	HTSOP-J8

## Precautions for use

- (1) This document provides the BOM for evaluation boards. Small parts can also be selected for resistor, capacitor, and coil.
- (2) When miniaturizing a resistor, consider decrease in rated power and withstand voltage.
- (3) When miniaturizing a ceramic capacitor, consider decrease in withstand voltage. In addition, the capacity may be decreased by DC bias characteristics, and the desired characteristics may not be obtained.
- (4) If ceramic capacitor models differ even when they have the same capacity and withstand voltage, the capacity may be decreased by DC bias characteristics depending on the model, and desired characteristics may not be obtained. Be sure to check the DC bias characteristics.
- (5) When miniaturizing a coil, consider increase in direct current resistance and decrease in rated current. An increase in DC resistance can cause a deterioration of power conversion efficiency. A decrease in rated current can saturate the coil when outputting a large current, which may deteriorate efficiency or make it impossible to obtain the desired output current.
- (6) If there is a possibility that the output will short-circuit, use a coil with a rated current that is larger than the maximum IC output current. For example, even when up to 100 mA is actually used for an IC that can output 1 A, select a coil whose rated current is larger than 1 A. If a coil with a small rated current is used, it will be saturated by a large current in the event of output short-circuiting, resulting in a steep increase in output voltage. The IC may be broken down because the processing speed of the overcurrent protecting function of the IC cannot keep up with the increase in voltage.
- (7) This circuit constant is the value for our evaluation board. It may be necessary to adjust the constant for the actual board. Carry out suitable evaluations.

## Notes

- 1) The information contained herein is subject to change without notice.
- 2) Before you use our Products, please contact our sales representative and verify the latest specifications :
- 3) Although ROHM is continuously working to improve product reliability and quality, semiconductors can break down and malfunction due to various factors.  
Therefore, in order to prevent personal injury or fire arising from failure, please take safety measures such as complying with the derating characteristics, implementing redundant and fire prevention designs, and utilizing backups and fail-safe procedures. ROHM shall have no responsibility for any damages arising out of the use of our Products beyond the rating specified by ROHM.
- 4) Examples of application circuits, circuit constants and any other information contained herein are provided only to illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.
- 5) The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM or any other parties. ROHM shall have no responsibility whatsoever for any dispute arising out of the use of such technical information.
- 6) The Products specified in this document are not designed to be radiation tolerant.
- 7) For use of our Products in applications requiring a high degree of reliability (as exemplified below), please contact and consult with a ROHM representative : transportation equipment (i.e. cars, ships, trains), primary communication equipment, traffic lights, fire/crime prevention, safety equipment, medical systems, servers, solar cells, and power transmission systems.
- 8) Do not use our Products in applications requiring extremely high reliability, such as aerospace equipment, nuclear power control systems, and submarine repeaters.
- 9) ROHM shall have no responsibility for any damages or injury arising from non-compliance with the recommended usage conditions and specifications contained herein.
- 10) ROHM has used reasonable care to ensure the accuracy of the information contained in this document. However, ROHM does not warrants that such information is error-free, and ROHM shall have no responsibility for any damages arising from any inaccuracy or misprint of such information.
- 11) Please use the Products in accordance with any applicable environmental laws and regulations, such as the RoHS Directive. For more details, including RoHS compatibility, please contact a ROHM sales office. ROHM shall have no responsibility for any damages or losses resulting non-compliance with any applicable laws or regulations.
- 12) When providing our Products and technologies contained in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, including without limitation the US Export Administration Regulations and the Foreign Exchange and Foreign Trade Act.
- 13) This document, in part or in whole, may not be reprinted or reproduced without prior consent of ROHM.



Thank you for your accessing to ROHM product informations.  
More detail product informations and catalogs are available, please contact us.

## ROHM Customer Support System

<http://www.rohm.com/contact/>