

Switching Regulator IC Series

Inductor Calculation for Buck Converter IC

No.12027ECY01

This application note covers the steps required in choosing the inductor and to calculate the value used in buck regulator IC circuits.

• Buck (Step-Down) Converter

Switching regulators are used in a variety of applications to provide stable and efficient power conversion. A buck converter is a specific type of switching regulator that steps down the input voltage to a lower level output.

Fig. 1 shows a typical buck converter circuit when switching element Q1 is ON. When N-ch MOSFET Q1 is ON, current flowing from input V_{IN} to coil L charges the output capacitor C_o and supplies output current I_o . In this scenario, the current flowing through coil L produces a magnetic field and electric energy is converted to magnetic energy to be stored.

Fig. 2 illustrates the same circuit when switching element Q1 is in an OFF state. When Q1 is OFF, free-wheeling diode D1 is activated, and the energy stored in coil L is released.

 


Fig. 1: Basic Buck Converter Circuit Switching Element ON

 


Fig. 2: Basic Buck Converter Circuit Switching Element OFF

• Inductor Current Waveform

Fig. 3 shows the inductor's current waveform. I_{OUT} is the average inductor current value. When switching element Q1 is ON, current flow is shown during ON period t_{ON} of Q1, and voltage $V_{L(ON)}$ of coil L can be calculated by the following equation:

$$V_{L(ON)} = -(V_{IN} - V_{SW} - V_{OUT}) \quad (1)$$

V_{IN} : Input Voltage (V)
 V_{SW} : Q1 ON-state Voltage Drop (V)
 V_{OUT} : Output Voltage (V)

The relation between current I_L and voltage V_L of coil L, which has self-inductance, can be calculated using the equation below:

$$V_L = -L \frac{dI_L}{dt} \quad (2)$$

From equation (2), it is clear that by applying additional voltage to the inductor, the reverse-current direction increases by slope V/L .

Current flowing through the coil during t_{ON} can be calculated using equation (1), (2), and by the following method; I_{LT} represents current right before switching element Q1 turns ON, I_{LP} represents current right before switching element Q1 turns OFF.

$$I_{LP} - I_{LT} = -\frac{(V_{SW} - V_{IN} + V_{OUT}) \times t_{ON}}{L} \quad (3)$$

The next step is to determine current flow in coil L when the switching element is OFF.

 


Fig. 3: Inductor Current Waveform

From Fig. 2, the coil voltage when Q1 in OFF- state is $V_{L(OFF)}$, can be calculated using the following method:

$$V_{L(OFF)} = V_D + V_{OUT} \quad (4)$$

V_D : Forward Voltage Drop across D1 (V)
 V_{OUT} : Output Voltage (V)

Using equations (2) and (4), the current flowing through coil L when Q1 is OFF is as follows:

$$I_{LP} - I_{LT} = \frac{(V_D + V_{OUT}) \times t_{OFF}}{L} \quad (5)$$

Current flow in the coil L is almost the same as the output current; consequently,

$$I_{LP} + I_{LT} = 2 \times I_{OUT} \quad (6)$$

From equations (3) and (6), I_{LP} during Q1 ON-state is

$$I_{LP} = I_{OUT} + \frac{(V_{IN} - V_{SW} - V_{OUT}) \times t_{ON}}{2 \times L} \quad (7)$$

Using equations (5) and (6), I_{LP} can be calculated during the period when the switching element is OFF:

$$I_{LP} = I_{OUT} + \frac{(V_D + V_{OUT}) \times t_{OFF}}{2 \times L} \quad (8)$$

- On-Duty Calculation

On-duty D is the ratio of time the switching element is ON t_{ON} versus the switching oscillatory cycle T_{SW} :

$$D = \frac{t_{ON}}{T_{SW}} = \frac{t_{ON}}{t_{ON} + t_{OFF}} = t_{ON} \times f_{SW} = 1 - (t_{OFF} \times f_{SW}) \quad (9)$$

Using (7), (8), and (9), the duty can be calculated using the expression below:

$$D = \frac{V_D + V_{OUT}}{V_{IN} - V_{SW} + V_D} \quad (10)$$

By ignoring the voltage drop V_{SW} of the switching element and voltage drop of the diode in equation (10), it is clear that on-duty is fixed by the ratio of output voltage over input voltage:

$$D \cong \frac{V_{OUT}}{V_{IN}} \quad (11)$$

- Maximum Coil Current Value

Use equations (9) and (10) to determine t_{ON} :

$$t_{ON} = \frac{D}{f_{SW}} = \frac{V_D + V_{OUT}}{(V_{IN} - V_{SW} + V_D) \times f_{SW}} \quad (12)$$

The equation below determines the maximum value of I_{LP} by substituting (12) into (7):

$$I_{LP} = I_{OUT} + \frac{(V_{IN} - V_{SW} - V_{OUT}) \times (V_D + V_{OUT})}{(V_{IN} - V_{SW} + V_D) \times 2 \times L \times f_{SW}} \quad (13)$$

Equation (14) is used to determine the minimum value I_{LT} by substituting (13) into (6):

$$I_{LT} = I_{OUT} - \frac{(V_{IN} - V_{SW} - V_{OUT}) \times (V_D + V_{OUT})}{(V_{IN} - V_{SW} + V_D) \times 2 \times L \times f_{SW}} \quad (14)$$

Current-difference between max. and min. ($I_{LP} - I_{LT}$) is as follows:

$$(I_{LP} - I_{LT}) = \frac{(V_{IN} - V_{SW} - V_{OUT}) \times (V_D + V_{OUT})}{(V_{IN} - V_{SW} + V_D) \times L \times f_{SW}} \quad (15)$$

Equations (13) and (15) show that large inductance L and high switching frequency will reduce maximum current (I_{LP}) and current difference between max. and min. ($I_{LP} - I_{LT}$).

- Inductance L Value Calculation

Define the ratio of current-difference flowing in coil L ($I_{LP} - I_{LT}$) versus output current I_{OUT} as current ripple-ratio "r".

$$r = \frac{\Delta I_L}{I_{OUT}} = \frac{I_{LP} - I_{LT}}{I_{OUT}} \quad (16)$$

Substitute (15) into (16):

$$r = \frac{(V_{IN} - V_{SW} - V_{OUT}) \times (V_D + V_{OUT})}{(V_{IN} - V_{SW} + V_D) \times f_{SW} \times L \times I_{OUT}} \quad (17)$$

Then, solve (17) for L to calculate the inductance value:

$$L = \frac{(V_{IN} - V_{SW} - V_{OUT}) \times (V_D + V_{OUT})}{(V_{IN} - V_{SW} + V_D) \times f_{SW} \times r \times I_{OUT}} \quad (H) \quad (18-1)$$

When the output voltage is high, the calculation can be simplified.

$$L = \frac{(V_{IN} - V_{OUT}) \times V_{OUT}}{V_{IN} \times f_{SW} \times r \times I_{OUT}} \quad (H) \quad (18-2)$$

The inductor value can be increased to reduce the ripple-ratio; however, this will typically result in an inductor size that is physically too big for practical use. Consequently, "r" is usually set between 0.2 and 0.5 for buck converters.

- Maximum Current Flow through the Coil

Maximum current flow through the coil can be calculated using the following equation:

$$I_{Lpeak} = I_{OUT} + \frac{r \times I_{OUT}}{2} \quad (A) \quad \text{or} \quad = I_{OUT} + \frac{V_{OUT} \times (V_{IN} - V_{OUT})}{2 \times V_{IN} \times f_{SW} \times L} \quad (A) \quad (19)$$

Current flowing through the coil is a combination of output current and ripple-current. When an abnormality occurs (ex. output short) in a transient load condition and there will be a power surge due to the absence of soft-start feature, and it is possible that the actual current flow through the inductor will exceed the maximum calculated current. Under transient conditions, coil current may increase up to the IC's switching current limit. Therefore, the safest approach is to select an inductor with a saturation current rating that exceeds the switching current limit, and not the maximum coil current.

- Effective RMS current flowing through the coil

Effective current value of triangular wave can be calculated by the following method.

$$I_{Lrms} = \sqrt{\frac{I_{LP}^2 + I_{LT}^2 + I_{LP} \times I_{LT}}{3}} \quad (20)$$

By substituting equations (13) and (14) into (20), we arrive at the following:

$$I_{Lrms} = \sqrt{I_{OUT}^2 + \frac{1}{12} \times \left(\frac{(V_{IN} - V_{SW} - V_{OUT}) \times (V_D + V_{OUT})}{(V_{IN} - V_{SW} + V_D) \times L \times f_{SW}} \right)^2} \quad (A) \quad (21)$$

• Example for Coil selection:

Determine the operating conditions of the buck converter:

- $V_{IN} = 12V$ Input Voltage
- $V_{OUT} = 3.3V$ Output Voltage
- $I_{OUT} = 2A$ Output Current
- $r = 0.3$ Output Current Ripple Ratio
- $V_{SW} = 0.30$ ON State Voltage Drop of Switching Element Q1
- $V_D = 0.26$ * Forward Voltage Drop of Free Wheel Diode
- $f_{sw} = 380$ kHz Switching Frequency

* For synchronized rectifier type power conversion, specify ON-state voltage drop of lower side element Q2 (Fig. 4).

Calculate the inductance value of the coil by substituting the above parameters into equation (18-1) or (18-2).

$$\text{As per equation (18-1), } L = \frac{(12 - 0.30 - 3.3) \times (0.26 + 3.3)}{(12 - 0.30 + 0.26) \times 380000 \times 0.3 \times 2} = 10.663 \text{ } (\mu\text{H})$$

$$\text{As per equation (18-2), } L = \frac{(12 - 3.3) \times 3.3}{12 \times 380000 \times 0.3 \times 2} = 10.493 \text{ } (\mu\text{H})$$

Using equation (19), the maximum current flowing through the coil is as follows:

$$I_{L\text{peak}} = I_{OUT} + \frac{r \times I_{OUT}}{2} = 2 + \frac{0.3 \times 2}{2} = 2.3 \text{ (A)}$$

As per equation (21), the effective current value flowing through the coil is

$$I_{L\text{rms}} = \sqrt{2^2 + \frac{1}{12} \times \left(\frac{(12 - 0.30 - 3.3) \times (0.26 + 3.3)}{(12 - 0.30 + 0.26) \times 10.663 \times 10^{-6} \times 380000} \right)^2} = 2.008 \text{ (A)}$$

Coil selection should be based on the results of the calculations. For this design, 10 μ H is chosen as the closest standard inductance value. If the selected inductor value is different from the calculated result, adjust the current ripple value “r” using equation (17), and substitute the revised value into equation (19) to recalculate the maximum current flowing through the coil.

$$r = \frac{(12 - 0.30 - 3.3) \times (0.26 + 3.3)}{(12 - 0.30 + 0.26) \times 380000 \times 10 \times 10^{-6} \times 2} = 0.329$$

$$I_{L\text{peak}} = 2 + \frac{0.329 \times 2}{2} = 2.33 \text{ (A)}$$

 


Fig. 4: Basic circuit configuration of a buck converter using synchronous rectification power conversion. In this example, the upper switching element is in OFF-state.

Notes

No copying or reproduction of this document, in part or in whole, is permitted without the consent of ROHM Co.,Ltd.

The content specified herein is subject to change for improvement without notice.

The content specified herein is for the purpose of introducing ROHM's products (hereinafter "Products"). If you wish to use any such Product, please be sure to refer to the specifications, which can be obtained from ROHM upon request.

Examples of application circuits, circuit constants and any other information contained herein illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.

Great care was taken in ensuring the accuracy of the information specified in this document. However, should you incur any damage arising from any inaccuracy or misprint of such information, ROHM shall bear no responsibility for such damage.

The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM and other parties. ROHM shall bear no responsibility whatsoever for any dispute arising from the use of such technical information.

The Products specified in this document are intended to be used with general-use electronic equipment or devices (such as audio visual equipment, office-automation equipment, communication devices, electronic appliances and amusement devices).

The Products specified in this document are not designed to be radiation tolerant.

While ROHM always makes efforts to enhance the quality and reliability of its Products, a Product may fail or malfunction for a variety of reasons.

Please be sure to implement in your equipment using the Products safety measures to guard against the possibility of physical injury, fire or any other damage caused in the event of the failure of any Product, such as derating, redundancy, fire control and fail-safe designs. ROHM shall bear no responsibility whatsoever for your use of any Product outside of the prescribed scope or not in accordance with the instruction manual.

The Products are not designed or manufactured to be used with any equipment, device or system which requires an extremely high level of reliability the failure or malfunction of which may result in a direct threat to human life or create a risk of human injury (such as a medical instrument, transportation equipment, aerospace machinery, nuclear-reactor controller, fuel-controller or other safety device). ROHM shall bear no responsibility in any way for use of any of the Products for the above special purposes. If a Product is intended to be used for any such special purpose, please contact a ROHM sales representative before purchasing.

If you intend to export or ship overseas any Product or technology specified herein that may be controlled under the Foreign Exchange and the Foreign Trade Law, you will be required to obtain a license or permit under the Law.



Thank you for your accessing to ROHM product informations.
More detail product informations and catalogs are available, please contact us.

ROHM Customer Support System

<http://www.rohm.com/contact/>