

Switching Regulator IC Series

Calculation of Power Loss (Synchronous)

No.AEK59-D1-0065-2

This application note describes how to obtain the power loss required to calculate the temperature of a semiconductor device. Temperature control is important to ensuring product reliability.

Figure 1 is a circuit diagram of a synchronous rectification type DC/DC converter. Figure 2 shows a switching node voltage waveform and an inductor current waveform, where power loss is generated.

IC power loss comes mainly in the form of the five factors listed below.

1. Conduction loss caused by MOSFET on-resistance P_{ON-L}, P_{ON-H}
2. MOSFET switching loss P_{SW-H}
3. Dead time loss P_D
4. MOSFET gate charge loss P_G
5. Operating loss caused by IC control circuit P_{IC}

Conduction Loss

Conduction loss is calculated between Section A and Section B of the waveform in Fig. 2. In Section A, the high-side MOSFET is ON and the low-side MOSFET is OFF. Therefore, conduction loss can be calculated from the output current, on-resistance and on-duty cycle. In Section B, the high-side MOSFET is OFF and the low-side MOSFET is ON. Therefore, conduction loss can be calculated from the output current, on-resistance and off-duty cycle.

Conduction losses P_{ON-H} and P_{ON-L} can be calculated using the following formulas.

High-side MOSFET

$$P_{ON-H} = I_O^2 \times R_{ON-H} \times \frac{V_O}{V_{IN}} \quad [W] \quad (1)$$

Low-side MOSFET

$$P_{ON-L} = I_O^2 \times R_{ON-L} \times \left(1 - \frac{V_O}{V_{IN}}\right) \quad [W] \quad (2)$$

I_O : Output current [A]

R_{ON-H} : High – side MOSFET on – resistance [Ω]

R_{ON-L} : Low – side MOSFET on – resistance [Ω]

V_{IN} : Input voltage [V]

V_O : Output voltage [V]

Switching Loss

Switching loss is calculated between Section C and Section D of the waveform in Fig. 2. When the high-side MOSFET and the low-side MOSFET alternately turn ON/OFF, switching-loss is generated during the transition to ON. Since the formula that calculates the areas of the two triangles is similar to the formula that calculates the power loss during the rise and fall transition, the calculation of switching-loss can be approximated using a simple figure calculation.

Switching loss P_{SW-H} can be calculated using the following formula.

High-side MOSFET

$$P_{SW-H} = \frac{1}{2} \times V_{IN} \times I_O \times (t_r + t_f) \times f_{SW} \quad [W] \quad (3)$$

V_{IN} : Input voltage [V]

I_O : Output current [A]

t_r : High – side MOSFET rise time [sec]

t_f : High – side MOSFET fall time [sec]

f_{SW} : Switching frequency [Hz]

The low-side MOSFET turns ON at the gate voltage while the body-diode is powered. Then, by turning OFF the FET at the gate voltage, the load current continues running in the same direction through the body-diode. Thus, the drain voltage remains low. Accordingly, switching-loss P_{SWL} becomes minimal.

Dead Time Loss

When both the high-side MOSFET and low-side MOSFET turn ON simultaneously, a short-circuit occurs between VIN and GND, and a very large current spike is generated. To prevent this, the dead time is set to turn OFF both MOSFETs, although the inductor current continuously flows. During the dead time, this inductor current flows to the low-side MOSFET body-diode. Dead time loss P_D is calculated between section E and section F of the waveform in Fig. 2, using the following formula.

$$P_D = V_D \times I_O \times (t_{Dr} + t_{Df}) \times f_{SW} \quad [W] \quad (4)$$

V_D : Low – side MOSFET

Body – diode forward voltage [V]

I_O : Output current [A]

t_{Dr} : Dead time at rising [sec]

t_{Df} : Dead time at falling [sec]

f_{SW} : Switching frequency [Hz]

Gate Charge Loss

Gate charge loss is a power loss ascribed to MOSFET gate charging. It depends on the gate electric charge (or the gate capacity) of the high-side MOSFET and low-side MOSFET. Gate charge loss is calculated using the following formula.

$$P_G = (Q_{g-H} + Q_{g-L}) \times V_{gs} \times f_{sw} \quad [W] \quad (5)$$

or

$$P_G = (C_{g-H} + C_{g-L}) \times V_{gs}^2 \times f_{sw} \quad [W] \quad (6)$$

Q_{g-H} : High – side MOSFET gate electric charge [C]

Q_{g-L} : Low – side MOSFET gate electric charge [C]

C_{g-H} : High – side MOSFET gate capacity [F]

C_{g-L} : Low – side MOSFET gate capacity [F]

V_{gs} : Gate drive voltage [V]

f_{sw} : Switching frequency [Hz]

IC Operating Loss

Consumption power P_{IC} in the IC control circuit is calculated using the following formula.

$$P_{IC} = V_{IN} \times I_{CC} \quad [W] \quad (7)$$

V_{IN} : Input voltage [V]

I_{CC} : IC consumption current [A]

Total Power Loss

IC power loss P is the total of all these values.

$$P = P_{ON-H} + P_{ON-L} + P_{SW-H} + P_D + P_G + P_{IC} \quad [W] \quad (8)$$

P_{ON-H} : Conduction loss (high – side) [W]

P_{ON-L} : Conduction loss (low – side) [W]

P_{SW-H} : Switching loss (high – side) [W]

P_D : Dead time loss [W]

P_G : Gate charge loss [W]

P_{IC} : IC operating loss [W]

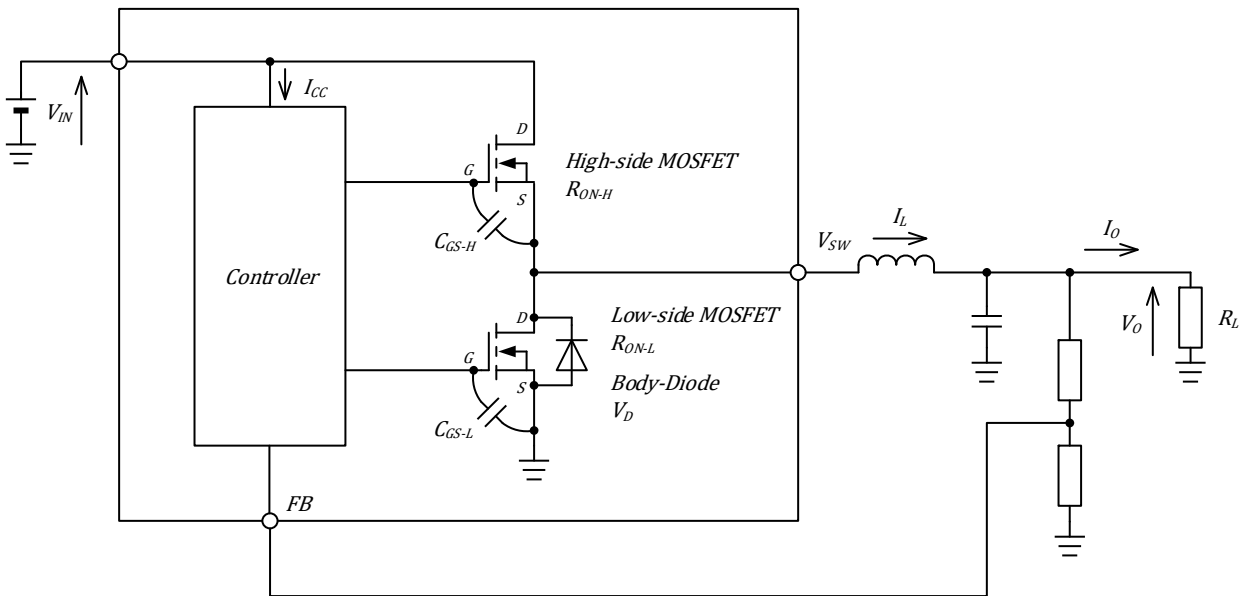


Figure 1. Synchronous Rectification Type DC/DC Converter Circuit

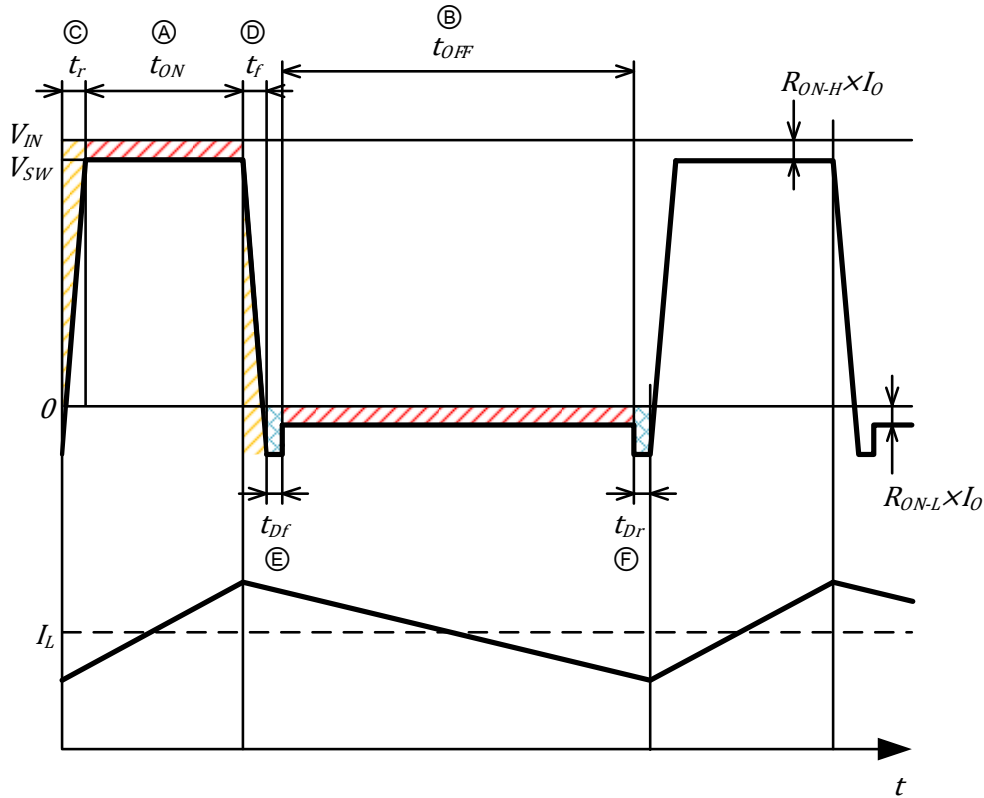


Figure 2. Switching Waveform and Loss

Calculation Example

Formula	Parameter	Result
1. Conduction loss $P_{ON-H} = I_O^2 \times R_{ON-H} \times \frac{V_O}{V_{IN}}$ $P_{ON-L} = I_O^2 \times R_{ON-L} \times \left(1 - \frac{V_O}{V_{IN}}\right)$	V_{IN} : Input voltage 12 V V_O : Output voltage 5.0 V I_O : Output current 3.0 A R_{ON-H} : High – side MOSFET on – resistance 100 mΩ R_{ON-L} : Low – side MOSFET on – resistance 70 mΩ	375 mW 367.5 mW
2. Switching loss $P_{SW-H} = \frac{1}{2} \times V_{IN} \times I_O \times (t_r + t_f) \times f_{SW}$	f_{SW} : Switching frequency 2.0 MHz t_r : High – side MOSFET rise time 4 nsec t_f : High – side MOSFET rise time 6 nsec	360 mW
3. Dead time loss $P_D = V_D \times I_O \times (t_{Dr} + t_{Df}) \times f_{SW} \text{ [W]}$	V_D : Low – side MOSFET body – diode forward voltage 0.5 V t_{Dr} : Dead time in rising 30 nsec t_{Df} : Dead time in falling 30 nsec	180 mW
4. Gate charge loss $P_G = (Q_{g-H} + Q_{g-L}) \times V_{gs} \times f_{SW}$ $P_G = (C_{g-H} + C_{g-L}) \times V_{gs}^2 \times f_{SW}$	Q_{g-H} : High – side MOSFET gate electric charge 1 nC Q_{g-L} : Low – side MOSFET gate electric charge 1 nC C_{g-H} : High – side MOSFET gate capacity 200 pF C_{g-L} : Low – side MOSFET gate capacity 200 pF	20 mW
5. IC operating loss $P_{IC} = V_{IN} \times I_{CC}$	V_{gs} : Gate drive voltage 5.0V I_{CC} : IC consumption current 1.0 mA	12 mW
Total power loss $P = P_{ON-H} + P_{ON-L} + P_{SW-H} + P_D + P_G + P_{IC}$		1.31 W

IC internal parameters such as MOSFET gate capacity and body-diode forward voltage are not open to the public in many cases. Even in such a case, it is possible to make an estimate by using the values in the above calculation example.

Notes

- 1) The information contained herein is subject to change without notice.
- 2) Before you use our Products, please contact our sales representative and verify the latest specifications :
- 3) Although ROHM is continuously working to improve product reliability and quality, semiconductors can break down and malfunction due to various factors.
Therefore, in order to prevent personal injury or fire arising from failure, please take safety measures such as complying with the derating characteristics, implementing redundant and fire prevention designs, and utilizing backups and fail-safe procedures. ROHM shall have no responsibility for any damages arising out of the use of our Products beyond the rating specified by ROHM.
- 4) Examples of application circuits, circuit constants and any other information contained herein are provided only to illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.
- 5) The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM or any other parties. ROHM shall have no responsibility whatsoever for any dispute arising out of the use of such technical information.
- 6) The Products are intended for use in general electronic equipment (i.e. AV/OA devices, communication, consumer systems, gaming/entertainment sets) as well as the applications indicated in this document.
- 7) The Products specified in this document are not designed to be radiation tolerant.
- 8) For use of our Products in applications requiring a high degree of reliability (as exemplified below), please contact and consult with a ROHM representative : transportation equipment (i.e. cars, ships, trains), primary communication equipment, traffic lights, fire/crime prevention, safety equipment, medical systems, servers, solar cells, and power transmission systems.
- 9) Do not use our Products in applications requiring extremely high reliability, such as aerospace equipment, nuclear power control systems, and submarine repeaters.
- 10) ROHM shall have no responsibility for any damages or injury arising from non-compliance with the recommended usage conditions and specifications contained herein.
- 11) ROHM has used reasonable care to ensure the accuracy of the information contained in this document. However, ROHM does not warrants that such information is error-free, and ROHM shall have no responsibility for any damages arising from any inaccuracy or misprint of such information.
- 12) Please use the Products in accordance with any applicable environmental laws and regulations, such as the RoHS Directive. For more details, including RoHS compatibility, please contact a ROHM sales office. ROHM shall have no responsibility for any damages or losses resulting non-compliance with any applicable laws or regulations.
- 13) When providing our Products and technologies contained in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, including without limitation the US Export Administration Regulations and the Foreign Exchange and Foreign Trade Act.
- 14) This document, in part or in whole, may not be reprinted or reproduced without prior consent of ROHM.



Thank you for your accessing to ROHM product informations.
More detail product informations and catalogs are available, please contact us.

ROHM Customer Support System

<http://www.rohm.com/contact/>