

## Voltage Detector (Reset IC) Series

# Setting for Output Pull-up Resistance

In this application note, we consider methods for setting the pull-up resistor values of Reset ICs with an open drain or open collector output.

### Pull-up resistor value: recommended setting range for each product

Table 1. Recommended values for pull-up

Table 1 shows the recommended setting ranges for each product that is listed in the data sheet.

These pull-up voltages are assumed to be within the output voltage range of the products.

To judge whether a pull-up resistor value is reasonable or not under a specific condition, the following estimation method can be used.

Type	Series name	Min RL [ $\Omega$ ]	Max RL [ $\Omega$ ]
Standard	BU48xx (VDET=0.9V~1.4V)	10k	1M
	BU48xx (VDET=1.5V~4.8V)	100k	1M
	BD48xx / 48E,K,Lxx	10k	1M
Adjustable delay	BU42xx (VDET=0.9V~1.4V)	50k	1M
	BU42xx (VDET=1.5V~4.8V)	100k	1M
	BD52xx	10k	1M
	BD52Exx/52xx-2C	50k	1M
Fixed delay	BD45xx/45Exx	50k	1M
Bipolar	BD47xx	2k	470k
Oversvoltage detection	BD71L4L-1	10k	1M

Note: the recommended resistor value is a standard.

Check carefully under actual conditions.

### Estimation of VOL for pull-up resistance/voltage setting

Procedures for VOL calculation

1. Check the power supply voltage VDD2 on the receiving side (microcomputer, etc.) and the output pull-up resistance RL, and calculate the required output current from  $VDD2/RL = IOL$ .
2. Estimate the maximum value of VOL from the IOL-VOL characteristic of the Reset IC.  
(Confirm the following conditions: for the power supply voltage of the Reset IC, VDD, check the minimum power supply voltage with which you want to maintain the L output; for the temperature, check the high temperature side where VOL reaches maximum.)
3. Check if the specification for the "L" level input voltage on the receiving side (microcomputer, etc.) is satisfied.

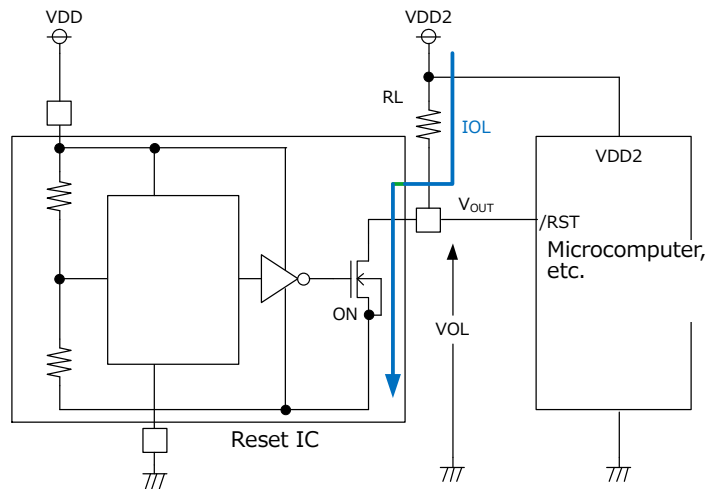


Figure 1. Output current path and connection to rear stage of open drain output Reset IC

### Calculation example

Open drain output type Reset IC (power supply VDD):	BD48xx
Microcomputer power supply voltage at steady state:	VDD2 = 5 V
"L" level input voltage of output connection destination:	VIL < 0.5 V
Pull-up resistance:	RL = 10kΩ
Detection voltage:	VDD = VDET = 3 V
VDD with which you want to maintain the reset L:	1.5 V (Min) (refer to the figure for a lower VDD condition when no figure is applicable)

(1) Calculate the output current from the pull-up resistance and voltage.

Output current  $I_{OL} = VDD2/RL = 5\text{ V}/10\text{ k}\Omega = 500\ \mu\text{A}$

(2) Based on the IOL-VOL data, estimate the VOL that is generated when a current estimated in (1) is supplied to the output. Refer to the figure for VDD = 1.5 V. From the figure, it can be read that VOL at high temperature (105°C) is 0.12 V. Allow for a variation by a factor of 2.

Namely, set VOL = 0.24 V.

(3) Confirm that VOL satisfies VIL < 0.5 V for the "L" level input voltage of the output destination.

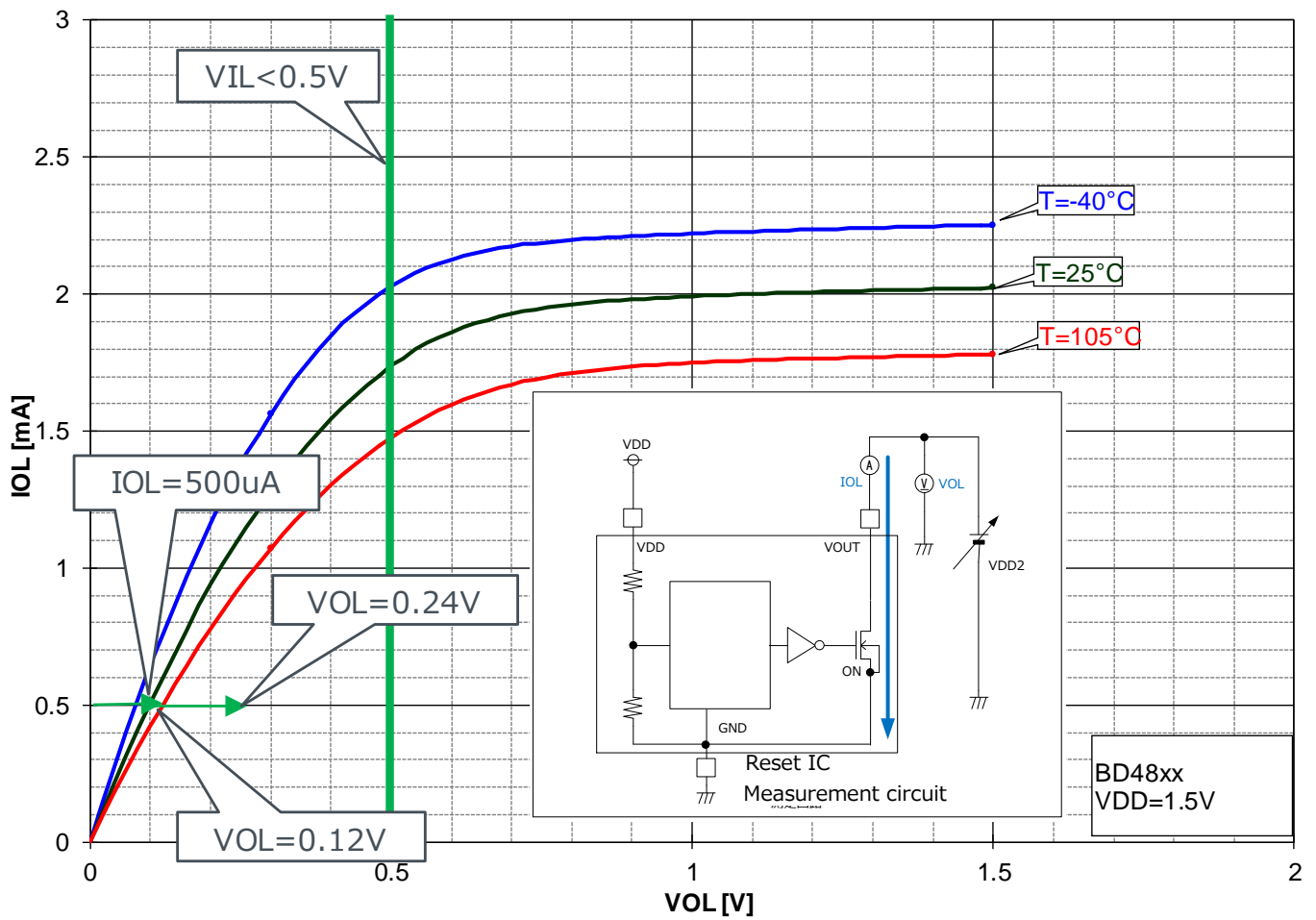


Figure 2. Output current  $I_{OL}$ –output voltage  $V_{OL}$  characteristic of open drain Reset IC

Reference data for the  $I_{OL}$ – $V_{OL}$  characteristic is shown in the following pages. Refer to the data for the estimation.

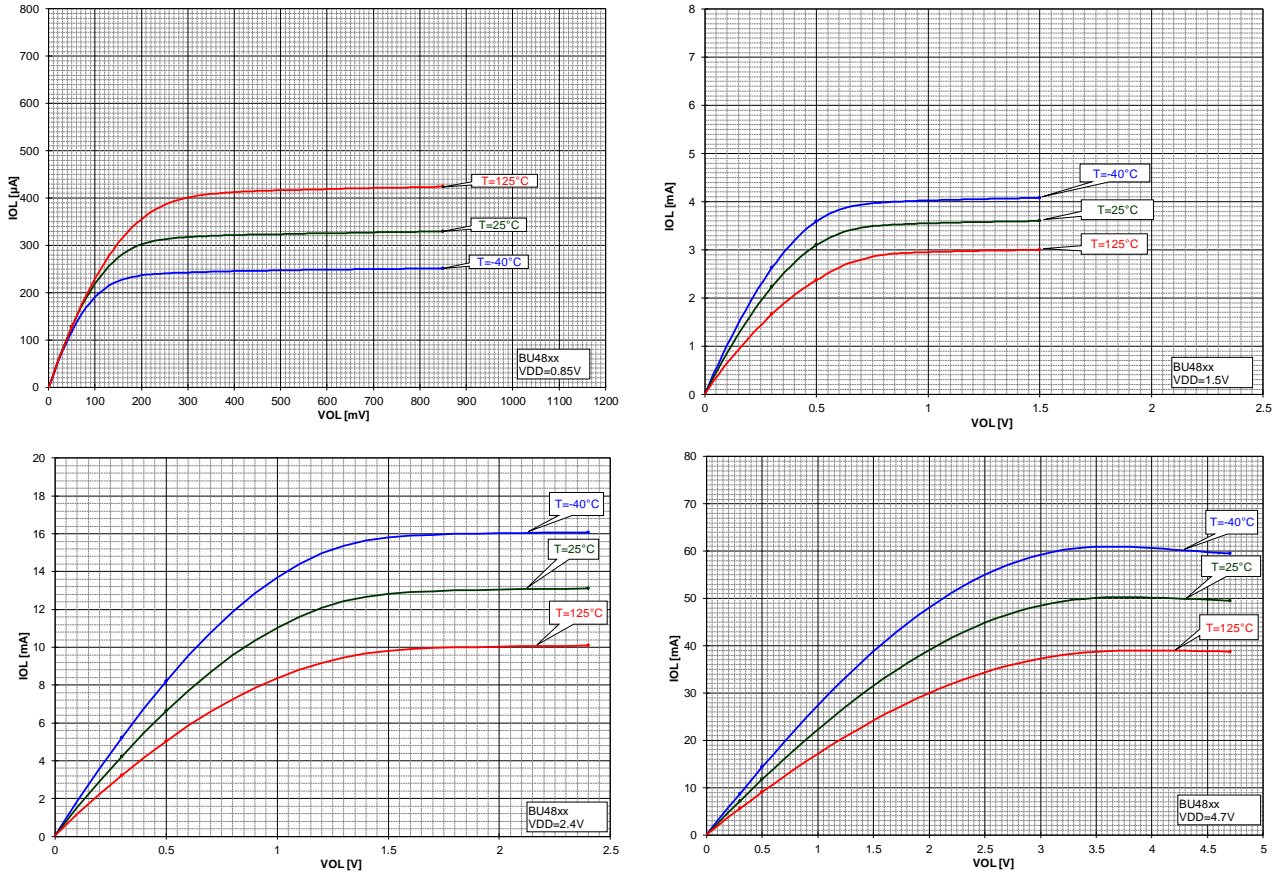


Figure 3. BU48xx output current–output voltage characteristic ( $V_{DD} = 0.85/1.5/2.4/4.7 [V]$ )

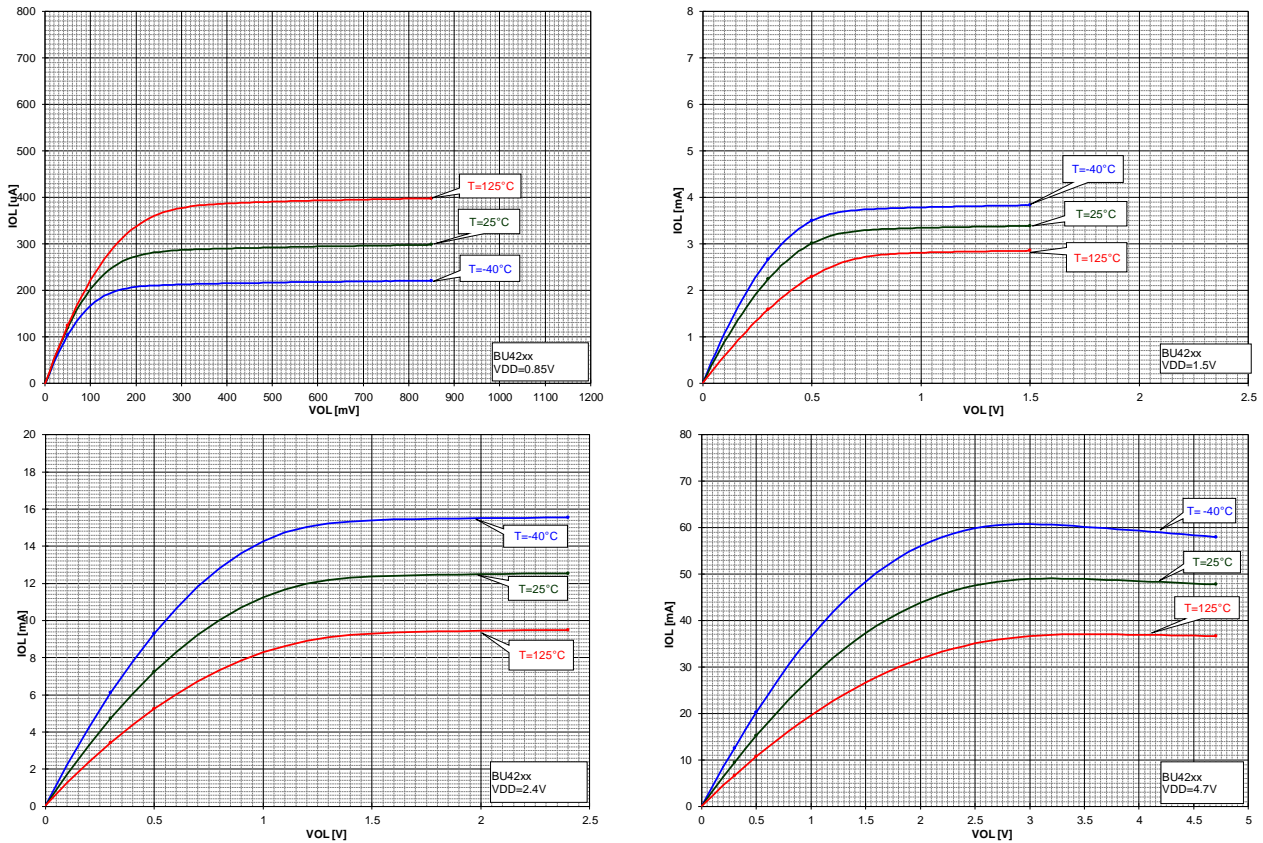


Figure 4. BU42xx output current–output voltage characteristic ( $V_{DD} = 0.85/1.5/2.4/4.7 [V]$ )



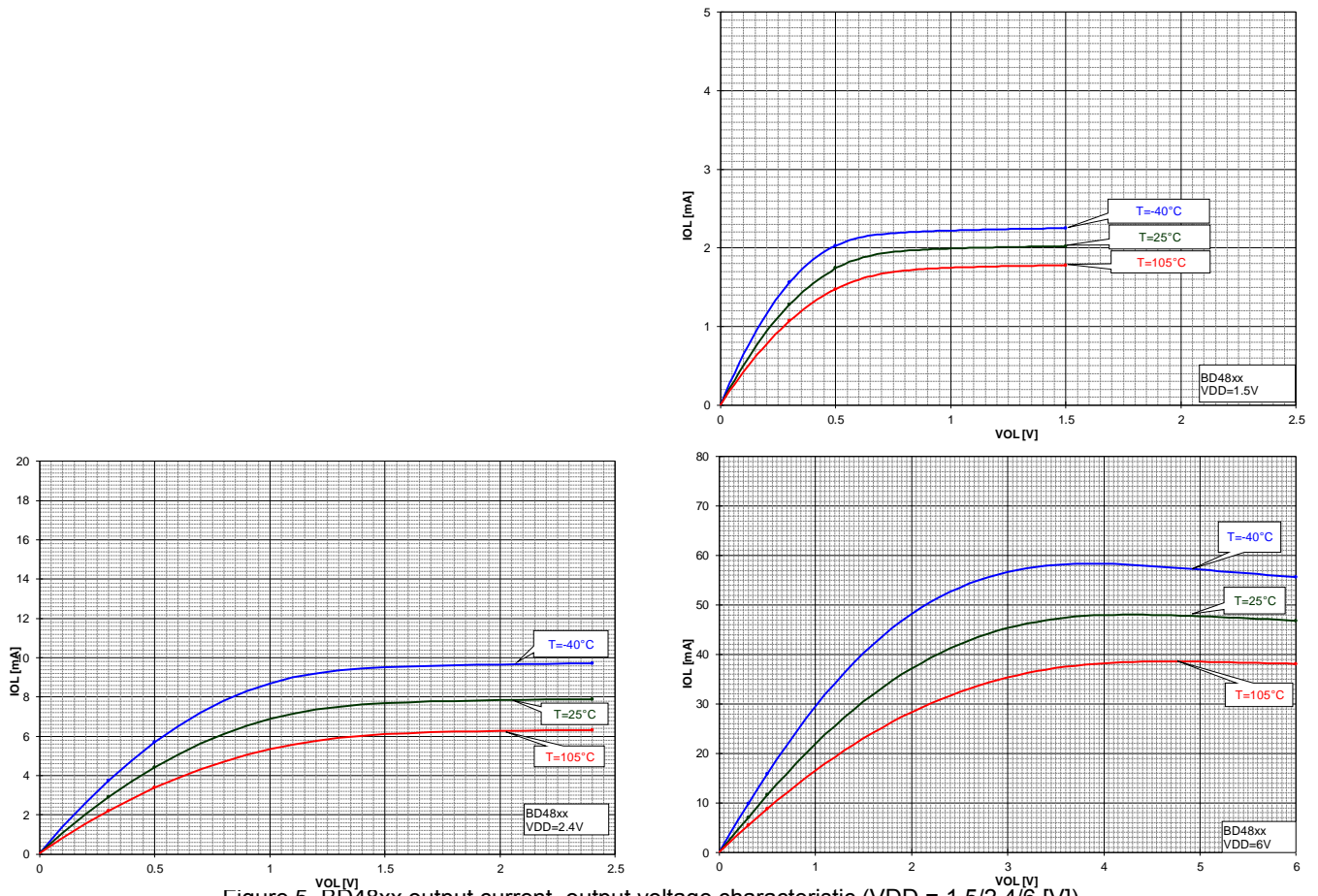


Figure 5. BD48xx output current-output voltage characteristic (VDD = 1.5/2.4/6 [V])

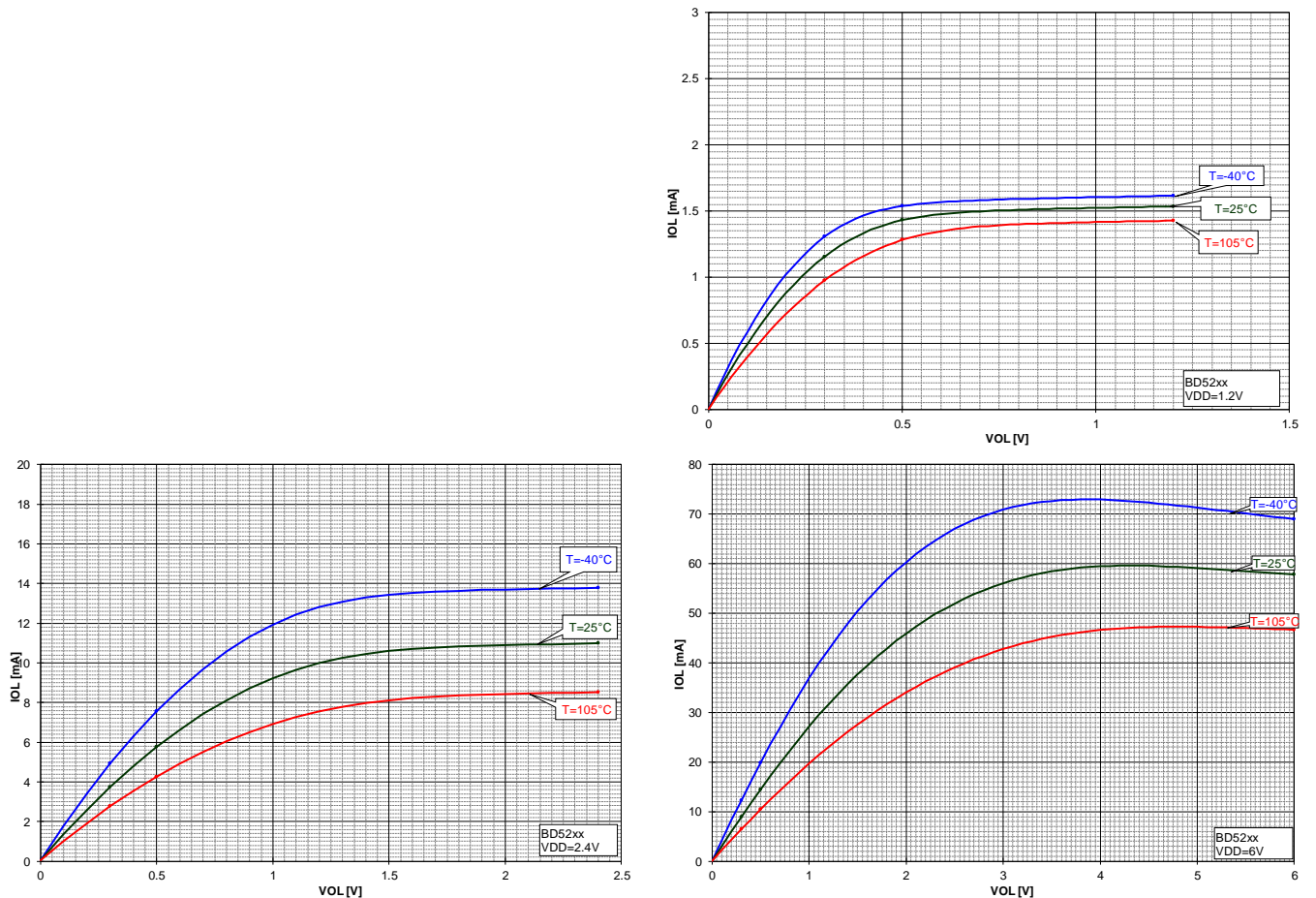


Figure 6. BD52xx output current-output voltage characteristic (VDD = 1.2/2.4/6 [V])

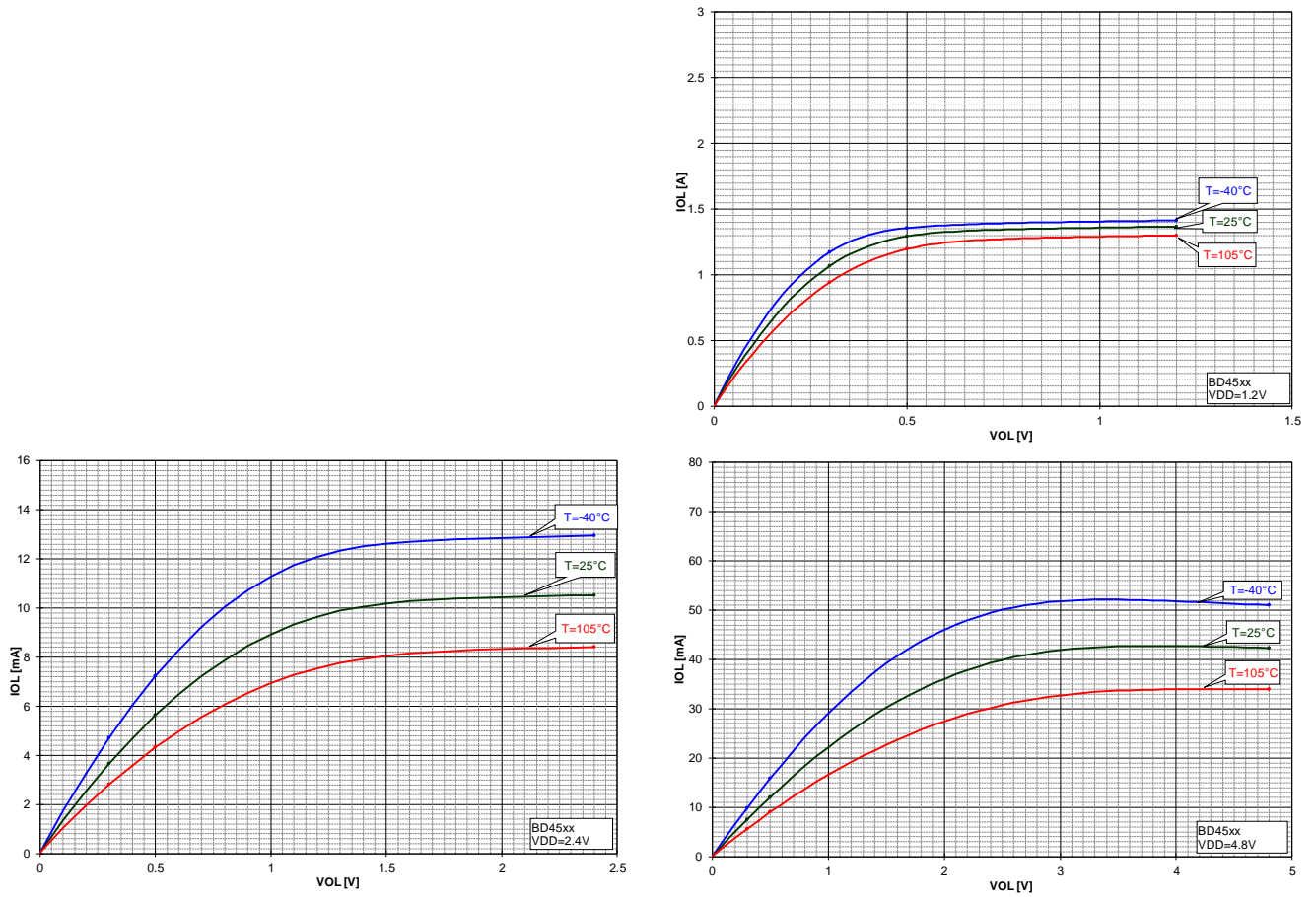


Figure 7. BD45xx output current–output voltage characteristic (VDD = 1.2/2.4/4.8 [V])

## Notes

- 1) The information contained herein is subject to change without notice.
- 2) Before you use our Products, please contact our sales representative and verify the latest specifications :
- 3) Although ROHM is continuously working to improve product reliability and quality, semiconductors can break down and malfunction due to various factors.  
Therefore, in order to prevent personal injury or fire arising from failure, please take safety measures such as complying with the derating characteristics, implementing redundant and fire prevention designs, and utilizing backups and fail-safe procedures. ROHM shall have no responsibility for any damages arising out of the use of our Products beyond the rating specified by ROHM.
- 4) Examples of application circuits, circuit constants and any other information contained herein are provided only to illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.
- 5) The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM or any other parties. ROHM shall have no responsibility whatsoever for any dispute arising out of the use of such technical information.
- 6) The Products are intended for use in general electronic equipment (i.e. AV/OA devices, communication, consumer systems, gaming/entertainment sets) as well as the applications indicated in this document.
- 7) The Products specified in this document are not designed to be radiation tolerant.
- 8) For use of our Products in applications requiring a high degree of reliability (as exemplified below), please contact and consult with a ROHM representative : transportation equipment (i.e. cars, ships, trains), primary communication equipment, traffic lights, fire/crime prevention, safety equipment, medical systems, servers, solar cells, and power transmission systems.
- 9) Do not use our Products in applications requiring extremely high reliability, such as aerospace equipment, nuclear power control systems, and submarine repeaters.
- 10) ROHM shall have no responsibility for any damages or injury arising from non-compliance with the recommended usage conditions and specifications contained herein.
- 11) ROHM has used reasonable care to ensure the accuracy of the information contained in this document. However, ROHM does not warrant that such information is error-free, and ROHM shall have no responsibility for any damages arising from any inaccuracy or misprint of such information.
- 12) Please use the Products in accordance with any applicable environmental laws and regulations, such as the RoHS Directive. For more details, including RoHS compatibility, please contact a ROHM sales office. ROHM shall have no responsibility for any damages or losses resulting from non-compliance with any applicable laws or regulations.
- 13) When providing our Products and technologies contained in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, including without limitation the US Export Administration Regulations and the Foreign Exchange and Foreign Trade Act.
- 14) This document, in part or in whole, may not be reprinted or reproduced without prior consent of ROHM.



Thank you for your accessing to ROHM product informations.  
More detail product informations and catalogs are available, please contact us.

## ROHM Customer Support System

<http://www.rohm.com/contact/>