

Voltage Detector (Reset IC) Series

Resistance Division and Inrush Current

If the detection voltage of the voltage to be monitored (V_{IN}) is higher than the detection voltage of the reset IC (V_{DET}), V_{IN} may be divided by the resistance and supplied to the reset IC as V_{DD} . This application note summarizes the precautions when utilizing this resistance division method.

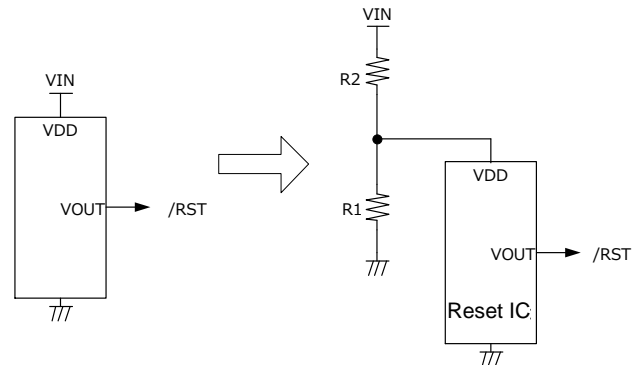


Figure 1. Example of resistance division for reset IC

Location of inrush current occurrence and power supply voltage

In a CMOS inverter, generally, PMOS and NMOS are simultaneously ON near the threshold for the output H/L switching.

In a reset IC, an inrush current occurs in the inverter on the output front stage (inside the blue dotted circle) near the release voltage.

The inrush current flows from V_{IN} to $R2$ and the voltage on the power supply terminal of the reset IC (V_{DD}) drops.

As a result, even when V_{IN} has reached the release voltage, V_{DD} may still be below the release voltage and V_{OUT} may not be switched to H.

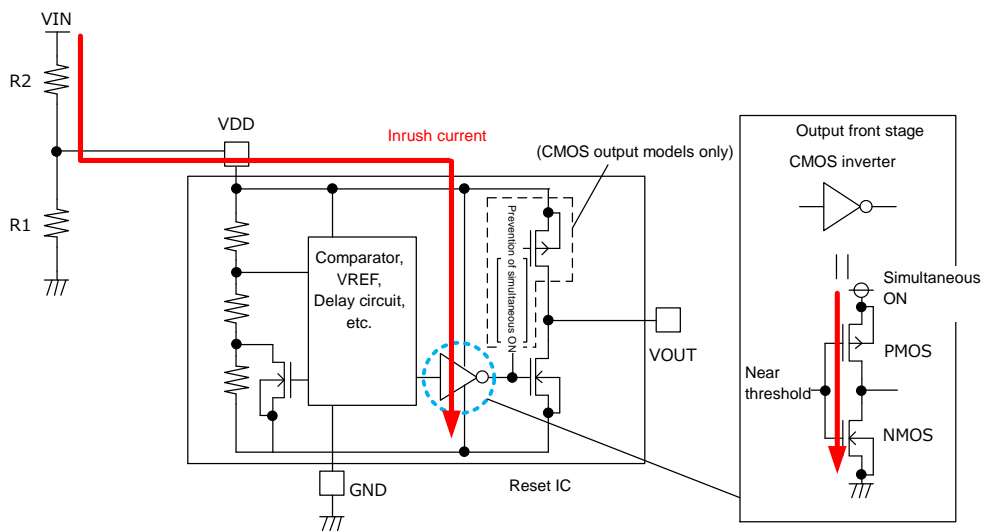


Figure 2. Location of inrush current occurrence in reset IC

Voltage drop and unstable operation caused by inrush current (1)

When the inrush current is large, an oscillation of the VDD voltage occurs near the release voltage following the sequence below.

- (1) When the voltage approaches the release voltage, the amount of inrush current increases.
- (2) R2 causes a voltage drop in proportion to the amount of inrush current.
- (3) The VDD voltage drops along with (2).
- (4) Since the VDD voltage drops, the amount of inrush current decreases.
- (5) Since the amount of inrush current decreases, the VDD voltage increases.
- (6) Returns to (1).


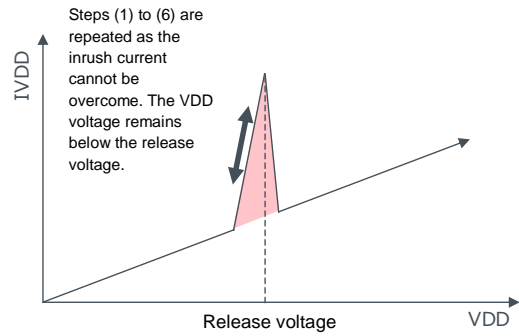
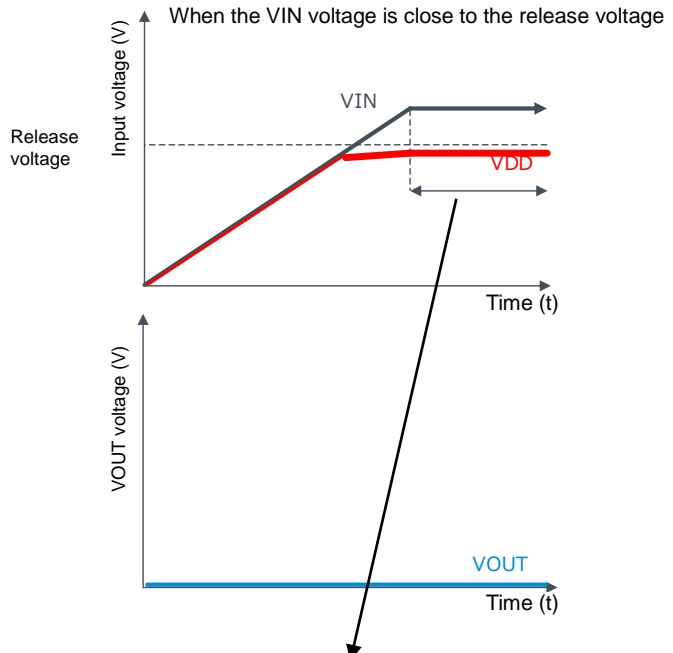


Figure 3. Inrush current near release voltage

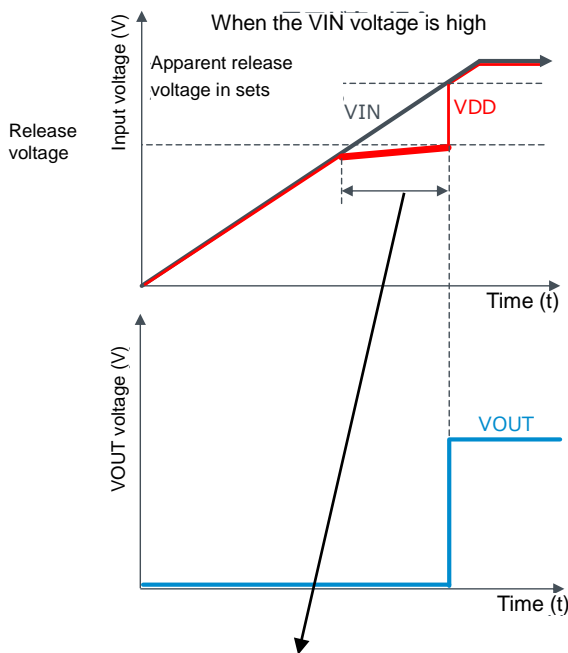Voltage drop and unstable operation caused by inrush current (2)



In this section, it appears that VDD stops increasing near the release voltage. However, VDD is still increasing slightly with VIN while oscillating slightly. When VDD exceeds the release voltage, the inrush current disappears. Therefore, it appears that the state has suddenly changed from a VDD clamped state to VOUT = H and VDD ≈ VIN. It also appears that the release voltage for VIN is higher than the setting.

When the VIN voltage remains at a value that keeps the VDD voltage in this section, the VDD voltage cannot exceed the release voltage and VOUT = L is maintained. It appears as if no reset release is performed even when the input voltage exceeds the release voltage for VIN.

Figure 4. Effect of inrush current on rise waveform of power supply

Countermeasure using input capacitor

When the capacitor C_{IN} is located between the VDD terminal and ground, the electric charge that is necessary to increase the voltage over the release voltage is compensated and the comparator can reach a state above the release voltage.

After that, the voltage drop of VDD disappears as the inrush current disappears, resulting in $V_{DD} \approx V_{IN}$.

Therefore, as the value of C_{IN} increases, it becomes more effective.


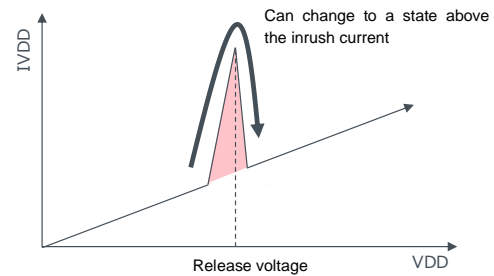


Figure 5. Reduction of inrush current effect by C_{IN} capacitor

Notes

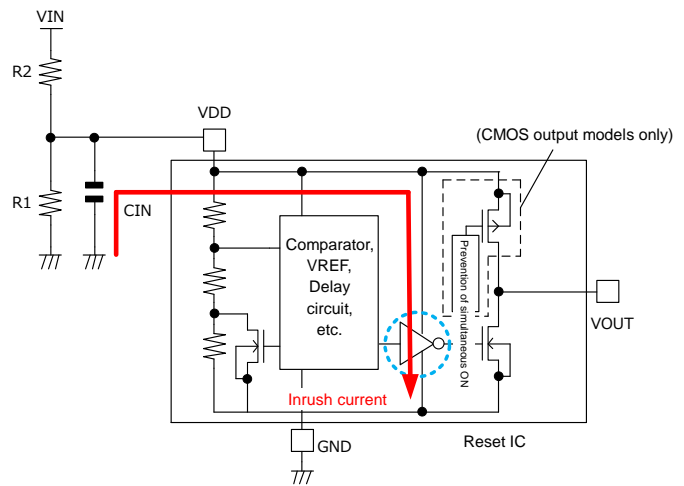- 1) The information contained herein is subject to change without notice.
- 2) Before you use our Products, please contact our sales representative and verify the latest specifications :
- 3) Although ROHM is continuously working to improve product reliability and quality, semiconductors can break down and malfunction due to various factors.
Therefore, in order to prevent personal injury or fire arising from failure, please take safety measures such as complying with the derating characteristics, implementing redundant and fire prevention designs, and utilizing backups and fail-safe procedures. ROHM shall have no responsibility for any damages arising out of the use of our Products beyond the rating specified by ROHM.
- 4) Examples of application circuits, circuit constants and any other information contained herein are provided only to illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.
- 5) The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM or any other parties. ROHM shall have no responsibility whatsoever for any dispute arising out of the use of such technical information.
- 6) The Products are intended for use in general electronic equipment (i.e. AV/OA devices, communication, consumer systems, gaming/entertainment sets) as well as the applications indicated in this document.
- 7) The Products specified in this document are not designed to be radiation tolerant.
- 8) For use of our Products in applications requiring a high degree of reliability (as exemplified below), please contact and consult with a ROHM representative : transportation equipment (i.e. cars, ships, trains), primary communication equipment, traffic lights, fire/crime prevention, safety equipment, medical systems, servers, solar cells, and power transmission systems.
- 9) Do not use our Products in applications requiring extremely high reliability, such as aerospace equipment, nuclear power control systems, and submarine repeaters.
- 10) ROHM shall have no responsibility for any damages or injury arising from non-compliance with the recommended usage conditions and specifications contained herein.
- 11) ROHM has used reasonable care to ensure the accuracy of the information contained in this document. However, ROHM does not warrant that such information is error-free, and ROHM shall have no responsibility for any damages arising from any inaccuracy or misprint of such information.
- 12) Please use the Products in accordance with any applicable environmental laws and regulations, such as the RoHS Directive. For more details, including RoHS compatibility, please contact a ROHM sales office. ROHM shall have no responsibility for any damages or losses resulting from non-compliance with any applicable laws or regulations.
- 13) When providing our Products and technologies contained in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, including without limitation the US Export Administration Regulations and the Foreign Exchange and Foreign Trade Act.
- 14) This document, in part or in whole, may not be reprinted or reproduced without prior consent of ROHM.



Thank you for your accessing to ROHM product informations.
More detail product informations and catalogs are available, please contact us.

ROHM Customer Support System

<http://www.rohm.com/contact/>