

ROHM Solution Simulator

Current Sense Amplifier

BD14210G-LA - High-Side Current Sensing Circuit - DC Sweep simulation

This circuit simulates the DC sweep response of a high-side current sensing circuit using the BD14210G-LA current sense amplifier. You can observe the output voltage and the difference between the output and reference pin voltage as load current is changed. You can customize the parameters of the components shown in blue, such as VSOURCE1, or peripheral components, and simulate the high-side current sensing circuit with the desired operating condition.

General Cautions

- Caution 1: The values from the simulation results are not guaranteed. Please use these results as a guide for your design.
- Caution 2: These model characteristics are specifically at Ta=25°C. Thus, the simulation result with temperature variances may significantly differ from the result with the one done at actual application board (actual measurement).
- Caution 3: Please refer to the Application note of Current Sense Amplifiers for details of the technical information.
- Caution 4: The characteristics may change depending on the actual board design and ROHM strongly recommend to double check those characteristics with actual board where the chips will be mounted on.

1 Simulation Schematic

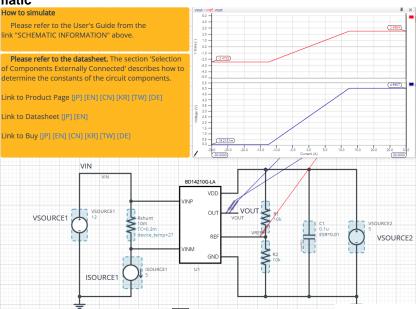


Figure 1. Simulation Schematic

How to simulate

The simulation settings, such as parameter sweep or convergence options. are configurable from the 'Simulation Settings' shown in Figure 2, and Table 1 shows the default setup of the simulation.

In case of simulation convergence issue, you can change advanced options to solve. Nothing is stated in the default statement in 'Manual Options'. You can modify it.

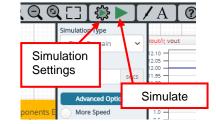


Figure 2. Simulation Settings and execution

Table 1. Simulation settings default setup

Table 1. Cilitation Settings deladit Setup						
Parameters Default		Note				
Simulation Type	tion Type DC Do not change Simulation Type					
Parameter Sweep	ISOURCE1	CURRENT_LEVEL from -30A to 30A by 0.3A				
Advanced options	Simulation Resolution	1e-7				
Advanced options	Convergence Assist	-				
Manual Options	-	-				

©2024 ROHM Co., Ltd. No. 67UG064E Rev.001 Aug.2024 1/3

3 Simulation Conditions

Table 2. List of the simulation condition parameters

Instance Type		Parameters	Default	Variable Range		Units
		Faiameters	Value	Min	Max	Office
VSOURCE1		Voltage_level	12	-0.2	26	V
	Voltage Source	AC_magnitude	0.0	fixed		V
		AC_phase	0.0	fixed		0
VSOURCE2	Voltage Source For Current Sense Amplifier	Voltage_level	5	2.7 (Note1)	5.5 ^(Note1)	V
		AC_magnitude	0.0	fixed		V
		AC_phase	0.0	fixed		0
ISOURCE1		Current_level	5	-30	30	Α
	Current Source	AC_magnitude	0.0	fixed		Α
		AC_phase	0.0	fixed		0

(Note 1) Set it to the guaranteed operating range of the Amplifier.

4 Amplifier model

Table 3 shows the model pin function implemented. Note that the Amplifier model is the behavioral model for its input/output characteristics, and neither protection circuits nor functions unrelated to the purpose are implemented.

Table 3. Amplifier model pins used for the simulation

Pin Name	Description		
VINP	Input of supply side of shunt resistor.		
VINM	Input of load side of shunt resistor.		
VDD	Power supply.		
OUT	Current detection output.		
REF	Reference input.		
GND	Ground.		

©2024 ROHM Co., Ltd.

No. 67UG064E Rev.001

Aug.2024

5 **Peripheral Components**

5.1 Bill of Material

Table 4 shows the list of components used in the simulation schematic. The default values of equivalent components are set to zero except for the ESR of C1. The model parameters of Rshunt are shown below. You can modify the values of each component.

Table 4. List of capacitors used in the simulation circuit

Туре	Instance Name	Default Value	Variable Range		Units
			Min	Max	Offics
	Rshunt	10m	free		Ω
Resistor	R1	10k	free		Ω
	R2	10k	free		Ω
Capacitor	C1	0.1	fre	ee	μF

5.2 Rshunt Model Parameters



Figure 3. Rshunt property editor

Figure 3 shows the model parameters of Rshunt. The default values of Rshunt and TC are 10m Ω and 0.3m Ω /°C respectively.

(Note 2) These parameters can take any positive value or zero in simulation but it does not guarantee the operation of the IC in any condition. Refer to the datasheet to determine adequate value of parameters.

6 **Recommended Products**

6.1 Current Sense Amplifier

BD14210G-LA: Current Sense Amplifier. [JP] [EN] [CN] [KR] [TW] [DE]

6.2 **Shunt Resistor**

LTR50UZPFU : High Power Low Ohmic Chip Resistor. [JP] [EN] [CN] [KR] [TW] [DE]

Technical Articles and Tools can be found in the Design Resources on the product web page.

Notice

- The information contained in this document is intended to introduce ROHM Group (hereafter referred to asROHM) products. When using ROHM products, please verify the latest specifications or datasheets before use.
- 2) ROHM products are designed and manufactured for use in general electronic equipment and applications (such as Audio Visual equipment, Office Automation equipment, telecommunication equipment, home appliances, amusement devices, etc.) or specified in the datasheets. Therefore, please contact the ROHM sales representative before using ROHM products in equipment or devices requiring extremely high reliability and whose failure or malfunction may cause danger or injury to human life or body or other serious damage (such as medical equipment, transportation, traffic, aircraft, spacecraft, nuclear power controllers, fuel control, automotive equipment including car accessories, etc. hereafter referred to as Specific Applications). Unless otherwise agreed in writing by ROHM in advance, ROHM shall not be in any way responsible or liable for any damages, expenses, or losses incurred by you or third parties arising from the use of ROHM Products for Specific Applications.
- 3) Electronic components, including semiconductors, can fail or malfunction at a certain rate. Please be sure to implement, at your own responsibilities, adequate safety measures including but not limited to fail-safe design against physical injury, and damage to any property, which a failure or malfunction of products may cause.
- 4) The information contained in this document, including application circuit examples and their constants, is intended to explain the standard operation and usage of ROHM products, and is not intended to guarantee, either explicitly or implicitly, the operation of the product in the actual equipment it will be used. As a result, you are solely responsible for it, and you must exercise your own independent verification and judgment in the use of such information contained in this document. ROHM shall not be in any way responsible or liable for any damages, expenses, or losses incurred by you or third parties arising from the use of such information.
- 5) When exporting ROHM products or technologies described in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, such as the Foreign Exchange and Foreign Trade Act and the US Export Administration Regulations, and follow the necessary procedures in accordance with these provisions.
- 6) The technical information and data described in this document, including typical application circuits, are examples only and are not intended to guarantee to be free from infringement of third parties intellectual property or other rights. ROHM does not grant any license, express or implied, to implement, use, or exploit any intellectual property or other rights owned or controlled by ROHM or any third parties with respect to the information contained herein.
- 7) No part of this document may be reprinted or reproduced in any form by any means without the prior written consent of ROHM.
- 8) All information contained in this document is current as of the date of publication and subject to change without notice. Before purchasing or using ROHM products, please confirm the latest information with the ROHM sales representative.
- 9) ROHM does not warrant that the information contained herein is error-free. ROHM shall not be in any way responsible or liable for any damages, expenses, or losses incurred by you or third parties resulting from errors contained in this document.



Thank you for your accessing to ROHM product informations.

More detail product informations and catalogs are available, please contact us.

ROHM Customer Support System

https://www.rohm.com/contactus