

Double Pulse Test Simulation with P05SCT4018KR-EVK-001 Simulation Model

<Getting Started>

Table of Contents

- Outlines
- Simulation Circuit
- Simulation Settings
- Component List
- PCB Pattern Parasitic Inductors
- Analytical Tools

How to use ROHM Solution Simulator

Please visit [ROHM Solution Simulator page](https://www.rohm.com/solution-simulator)
(<https://www.rohm.com/solution-simulator>)

- Hands-On User's Manual [Link](#)
- Tutorial Short Videos available

Double Pulse Test Simulation with P05SCT4018KR-EVK-001 Simulation Model

<Simulation Circuit>

Table 1. Parameter Settings

Parameters	Descriptions	Default	Simulation Setting Range
VDC	DC Voltage	800 V	
HS_VCC2, LS_VCC2	Gate drive positive voltage	18 V	15 to 20 V
HS_VEE, LS_VEE	Gate drive negative voltage	0 V	0 to 4 V
Tj	Q51, Q151 Device Junction Temperature	25 °C	
HS_VPULSE	High-side pulse period	5 μs	Fixed
	Low-side pulse width	2.4 μs	
LS_VPULSE	"L" (DC)		

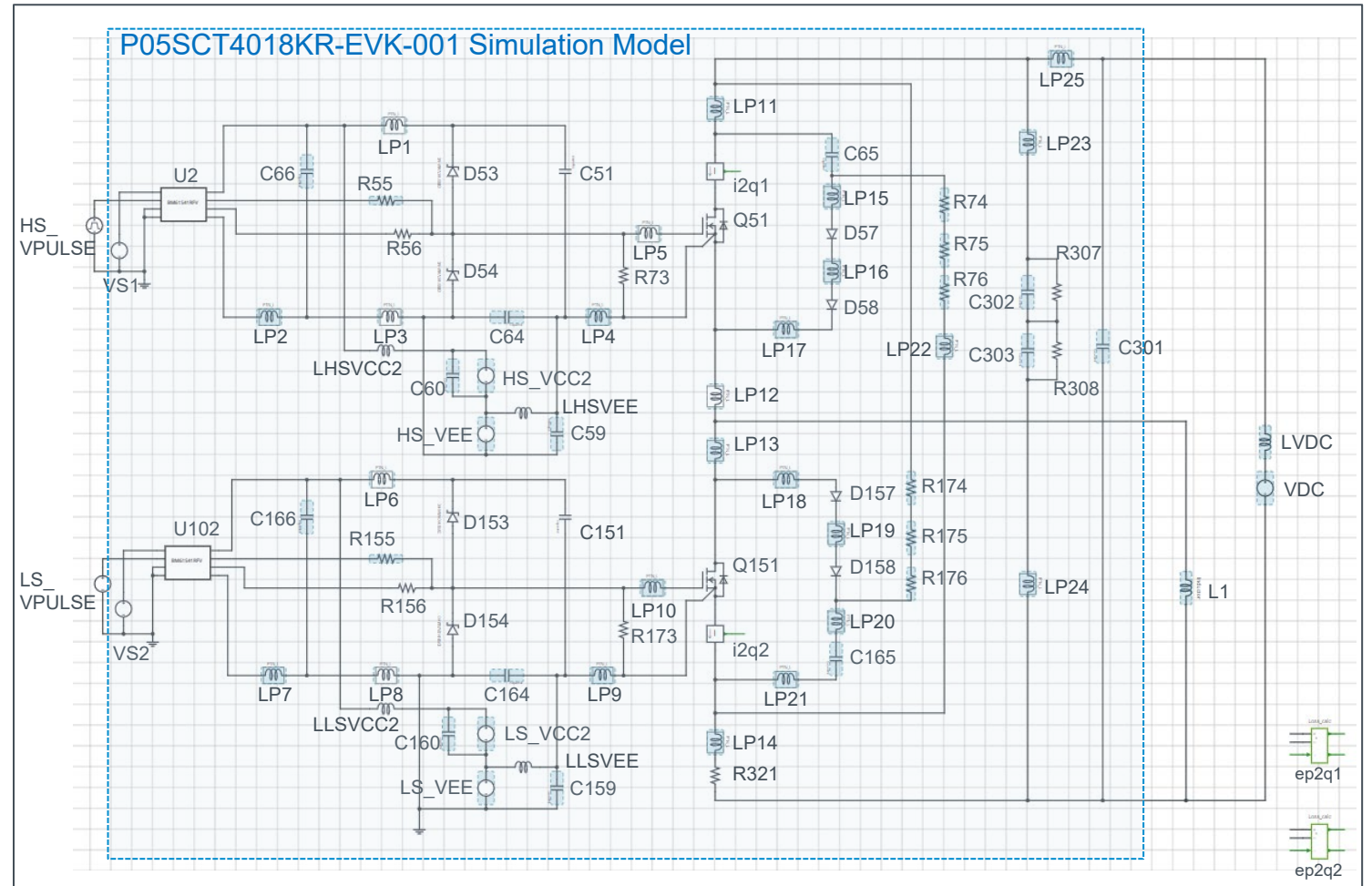


Figure 2. Simulation Circuit

Double Pulse Test Simulation with P05SCT4018KR-EVK-001 Simulation Model

<Simulation Settings>

How to setup the gate drive pulse

1. Gate drive voltage Vgs

Figure 3 shows a simplified gate driver circuit, and Figure 4 shows an example of the Vgs waveform. The voltage source VEE gives the voltage of the DS pin of the SiC MOSFET with respect to the GND2 voltage of the gate driver IC. The voltage source VCC2 gives the supply voltage VCC of the gate driver IC with respect to the DS pin voltage. As a result, the gate voltage Vgs of the SiC MOSFET is VCC for 'H' voltage and (-VEE) for 'L' voltage.

Set HS_VCC and HS_VEE for the high-side circuit, and LS_VCC and LS_VEE for the low-side circuit, respectively.

2. Gate Drive Pulse timing

Voltage source 'HS_VPULSE' generate the gate drive pulse timing. The period $T = 5\mu\text{s}$ and the pulse width = $2.5\mu\text{s}$. The actual gate drive pulse output is at the 'out' pin of BM61S41RFV-C, the gate driver IC.

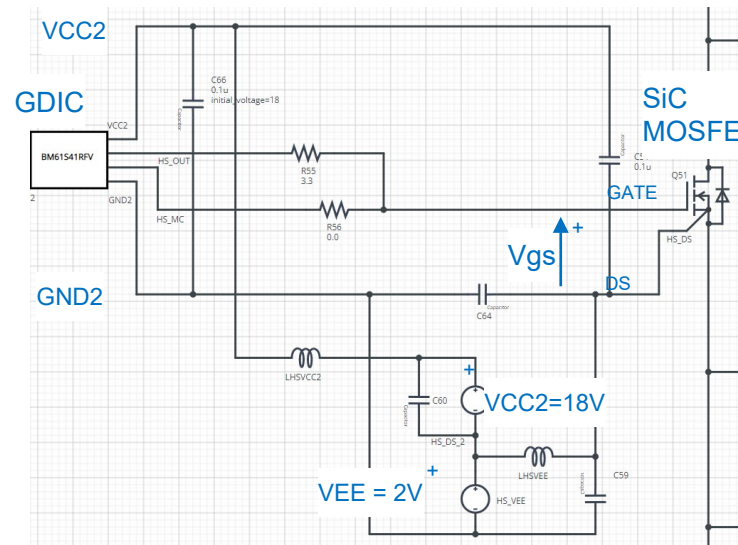


Figure 3. Simplified Gate Drive Circuit (common for high-side and low-side)

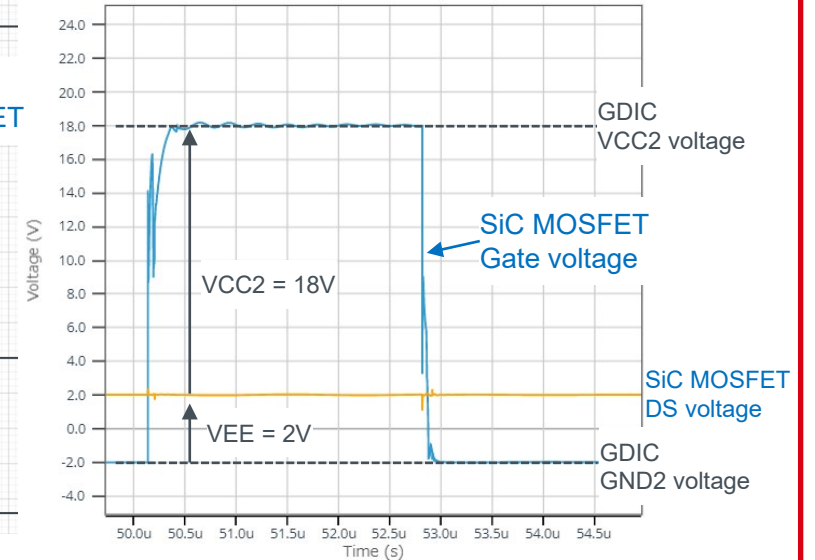


Figure 4. SiC MOSFET Vgs Voltage

Double Pulse Test Simulation with P05SCT4018KR-EVK-001 Simulation Model


<Simulation Settings>

How to set simulation parameters

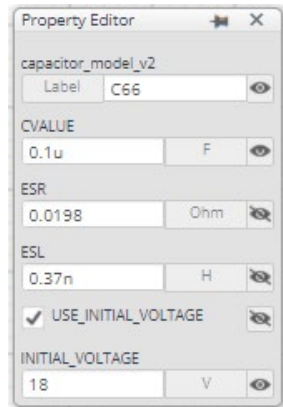
1. Using Property Editor

To open the Property Editor, right-click on a component and select "Properties" from the pull-down menu. Figure 5 shows an example of the Property Editor. You can browse the parameters of the component from the Property Editor.

Components shown in blue have "tunable" parameters, and you can change the parameters in the white text box in the Property Editor. Apply the values within the displayed tolerance range.



(a) Capacitor

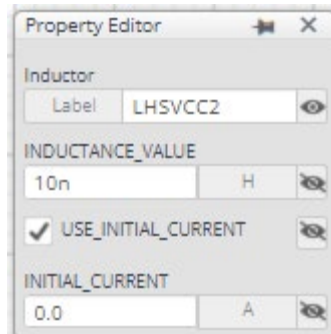

(b) Inductor

Figure 5. Property Editor Examples

2. 'USE_INITIAL_VOLTAGE' and 'USE_INITIAL_CURRENT'

The capacitor property 'USE_INITIAL_VOLTAGE' and the inductor property 'USE_INITIAL_CURRENT' are used to improve the convergence of the simulation and speed up the simulation. Initial voltage or initial current value will be applied to the component as the initial condition. It will improve simulation convergence.

When changing simulation parameters, the initial voltage and the initial current should be revised.

Table 2 and Table 3 shows the recommendation of the initial voltage and the initial current.

Table 2. Initial Voltage Recommendation

Symbol	Initial Voltage Recommendation
C64, C164	(-HS_VEE), (-LS_VEE)
C66, C166	(HS_VEE+HS_VCC2), (LS_VEE+LS_VCC2)
C59, C159	HS_VEE, LS_VEE
C65, C165	VDC
C302, C303	(VDC/2)
C301	VDC

Table 3. Initial Current Recommendation

Symbol	Initial Current Recommendation
LP16	0
LP19	0
LP20	0

Double Pulse Test Simulation with P05SCT4018KR-EVK-001 Simulation Model

<Component List>

Table 4. Power Device / Gate Driver IC Component List

Symbol	Part Number	Device
Q51, Q151	SCT4018KR	4G-SiC MOSFET, 1200V, 18mohm
D53, D54, D153, D154	RB160VAM-60	Schottky Barrier Diode
D57, D58, D157, D158	RFN1LAM7S	Super Fast Recovery Diode
U2, U102	BM61S41RFV-C	1ch Gate Driver Providing Galvanic Isolation

Part Number of Q51 and Q151 are selectable from the property editor. The list of the part number is shown below. To change the MOSFET, see instruction 'How to change MOSFET model' or refer to the hands-on manual from the link on Page 1.

Table 5. SiC MOSFET Part Number List

Symbol	Part Number	Features
Q51, Q151	SCT4018KR*	1200V, 18mohm
	SCT4036KR	1200V, 36mohm

* Default device

Note) We have not been able to confirm operation with all combinations. Please read the disclaimer carefully.

Table 6. Resistor Component List

Symbol	R value [ohm]	Tun-able	Comments
R55, R155	3.3	✓	Gate resistors
R56, R156	0		
R73, R173	4.7k		
R74, R75, R76, R174, R175, R176	10	✓	RCD Snubber resistors
R307, R308	1M		C Snubber resistors
R321	0.1m		Shunt resistor

Note) The value is constant unless otherwise specified as 'Tunable'.

How to change MOSFET Model

1. Right-click on the device
2. Select "Properties"
3. Pull down "SpiceLib Part"
4. Select the product

Double Pulse Test Simulation with P05SCT4018KR-EVK-001 Simulation Model

<Component List>

Table 7. Inductor Component List

Symbol	Inductor Values					Simulation Settings		Descriptions
	L [H]	PAR_RES [ohm]	SER_RES [ohm]	PAR_CAP[F]	Tunable	Use Initial current = 0 Option		
L1	250μ	51k	0.13	2.124p	✓	✓		DPT Inductive Load

Note) Refer to Figure 5 for the model composition.

Note) The value is constant unless otherwise specified as 'Tunable'.

Table 8. Capacitor Component List

Symbol	Capacitor Values				Simulation Settings			Descriptions
	C [F]	ESR [ohm]	ESL [H]	Tunable	Initial Voltage [V]	Tunable	Use Initial Voltage	
C51, C151	0.1μ	19.8m	0.37n		0			
C64, C164	0.1μ	19.8m	0.37n		0	✓	✓	
C66, C166	0.1μ	19.8m	0.37n		18	✓	✓	
C59, C159	4.7μ	3.2m	0.48n		0	✓	✓	
C60, C160	4.7μ	3.2m	0.48n		18	✓	✓	
C65, C165	33n	12m	0.65n	✓	800	✓	✓	RCD Snubber capacitors
C302, C303	0.47μ	8.4m	0.65n	✓	400	✓	✓	C Snubber capacitors
C301	10μ	9.9m	11n	✓	800	✓	✓	

Note) Refer to Figure 6 for the model composition.

Note) The value is constant unless otherwise specified as 'Tunable'.

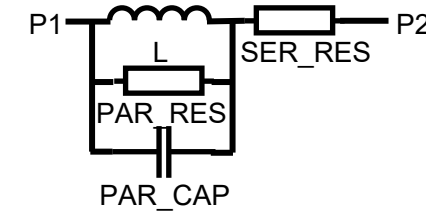


Figure 5. Inductor Model



Figure 6. Capacitor Model

Note) We have not been able to confirm operation with all combinations. Please read the disclaimer carefully.

Double Pulse Test Simulation with P05SCT4018KR-EVK-001 Simulation Model

<PCB Pattern Parasitic Inductors>

Table 9. EVK PCB Pattern Parasitic Inductor model

Symbol	Inductor Values			Sim Settings	Symbol	Inductor Values			Sim Settings
	SERL [nH]	SERR [mohm]	Tun-able	Initial Current = 0 Option		SERL [nH]	SERR [mohm]	Tun-able	Initial Current = 0 Option
LP1	1.086	4	✓		LP14	5.58	79	✓	
LP2	0.9024	5	✓		LP15	0.868	2	✓	
LP3	3.914	20	✓		LP16	1.23	4	✓	✓
LP4	3.818	10	✓		LP17	1.255	4	✓	
LP5	1.922	9	✓		LP18	0.7346	2	✓	
LP6	1.598	8	✓		LP19	1.571	4	✓	✓
LP7	1.194	6	✓		LP20	2.481	6	✓	✓
LP8	5.384	25	✓		LP21	2.136	8	✓	
LP9	3.413	90	✓		LP22	4.358	13	✓	
LP10	2.634	12	✓		LP23	3.147	103	✓	
LP11	1.637	33	✓		LP24	3.372	34	✓	
LP12	5.58	16.5	✓		LP25	3.194	83	✓	
LP13	5.58	16.5	✓						

Note) Refer to Figure 7 for the model composition.

Note) The value is constant unless otherwise specified as 'Tunable'.

Note) The inductor models are defined from the analysis of the PCB pattern design data and the accuracy is not guaranteed.

Note) We have not been able to confirm operation with all combinations. Please read the disclaimer carefully.

LP1 through LP25 are PCB pattern inductor models. These are defined from the electro-magnetic analysis of the PCB pattern layout and applied to the simulation circuit as discrete components. Figure 7 shows the model equivalent circuit. The resistor of 10 ohm in parallel is for stabilizing simulation.

You can modify these inductors, for example, referring to the layout design constraints to relatively evaluate how the pattern layout would affect the switching behaviors.

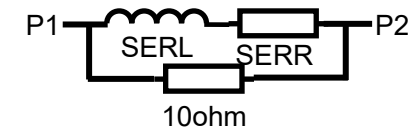


Figure 7. Parasitic L model

Double Pulse Test Simulation with P05SCT4018KR-EVK-001 Simulation Model

<Analytical Tools>

Analytical tools are used in the simulation circuit for current sensing and device loss calculation.

1. Current Sensing Tool

The component 'Current to Continuous Quantity' outputs the current flow 'p1' through 'p2' (See Figure 8.)

It is used to measure the drain current of the SiC MOSFET.

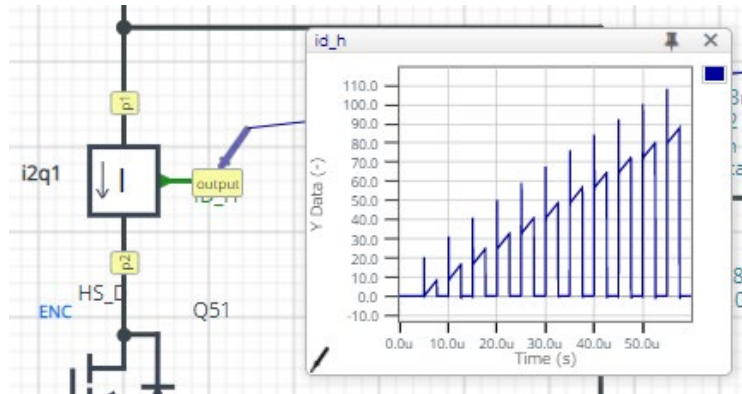


Figure 8. Current to Continuous Quantity

2. Device Loss Calculation Tool

The component 'Loss_Calc3' calculates the voltage difference between 'p1' and 'p2', and outputs the products of the voltage difference and 'i_sense' current input as 'loss_out' and its integration as 'loss_integ_out' (See Figure 9.)

$$loss_out(t) = v(t) \times i_sense(t)$$

$$loss_integ_out(t) = \int_0^t loss_out(t)dt$$

* $v(t)$: voltage difference between p1 and p2



Figure 9. Loss_Calc3

Note) The Loss_calc component is a utility module to support power loss calculation, and does not affect the simulation results of circuit operation or performance.

Notes

- 1) The information contained herein is subject to change without notice.
- 2) Before you use our Products, please contact our sales representative and verify the latest specifications :
- 3) Although ROHM is continuously working to improve product reliability and quality, semiconductors can break down and malfunction due to various factors.
Therefore, in order to prevent personal injury or fire arising from failure, please take safety measures such as complying with the derating characteristics, implementing redundant and fire prevention designs, and utilizing backups and fail-safe procedures. ROHM shall have no responsibility for any damages arising out of the use of our Products beyond the rating specified by ROHM.
- 4) Examples of application circuits, circuit constants and any other information contained herein are provided only to illustrate the standard usage and operations of the Products. The peripheral conditions must be taken into account when designing circuits for mass production.
- 5) The technical information specified herein is intended only to show the typical functions of and examples of application circuits for the Products. ROHM does not grant you, explicitly or implicitly, any license to use or exercise intellectual property or other rights held by ROHM or any other parties. ROHM shall have no responsibility whatsoever for any dispute arising out of the use of such technical information.
- 6) The Products specified in this document are not designed to be radiation tolerant.
- 7) For use of our Products in applications requiring a high degree of reliability (as exemplified below), please contact and consult with a ROHM representative : transportation equipment (i.e. cars, ships, trains), primary communication equipment, traffic lights, fire/crime prevention, safety equipment, medical systems, servers, solar cells, and power transmission systems.
- 8) Do not use our Products in applications requiring extremely high reliability, such as aerospace equipment, nuclear power control systems, and submarine repeaters.
- 9) ROHM shall have no responsibility for any damages or injury arising from non-compliance with the recommended usage conditions and specifications contained herein.
- 10) ROHM has used reasonable care to ensure the accuracy of the information contained in this document. However, ROHM does not warrants that such information is error-free, and ROHM shall have no responsibility for any damages arising from any inaccuracy or misprint of such information.
- 11) Please use the Products in accordance with any applicable environmental laws and regulations, such as the RoHS Directive. For more details, including RoHS compatibility, please contact a ROHM sales office. ROHM shall have no responsibility for any damages or losses resulting non-compliance with any applicable laws or regulations.
- 12) When providing our Products and technologies contained in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, including without limitation the US Export Administration Regulations and the Foreign Exchange and Foreign Trade Act.
- 13) This document, in part or in whole, may not be reprinted or reproduced without prior consent of ROHM.



Thank you for your accessing to ROHM product informations.
More detail product informations and catalogs are available, please contact us.

ROHM Customer Support System

<http://www.rohm.com/contact/>