

REF68020 : 2.5kW LLC Converter Reference Design

Contents

1. REF68020 : Reference Design Brief
2. What is LLC Converter?
3. Reference Designs for Power Supply Unit (PSU)
4. Simulate LLC Converter Circuits (Simulation tools and Demo Circuits)
5. Recommended Products for 3kW~5.5kW Power Supply Unit (PSU)
6. Important Notes on the Use of Reference Designs




2.5kW LLC Converter, DC390Vin, DC48Vout

REF68020 –Reference Design

Feature

- Full-bridge LLC converters used in a variety of applications
- DC390Vin, Output DC48V, 53A (2.5kW)
- High efficiency (97.3% peak) achieved by using SiC MOSFETs for primary side.
- This board was developed by Nuvoton Technology. ([LLC EVB – Nuvoton](#) Jump to an external website)

<Block Diagram>

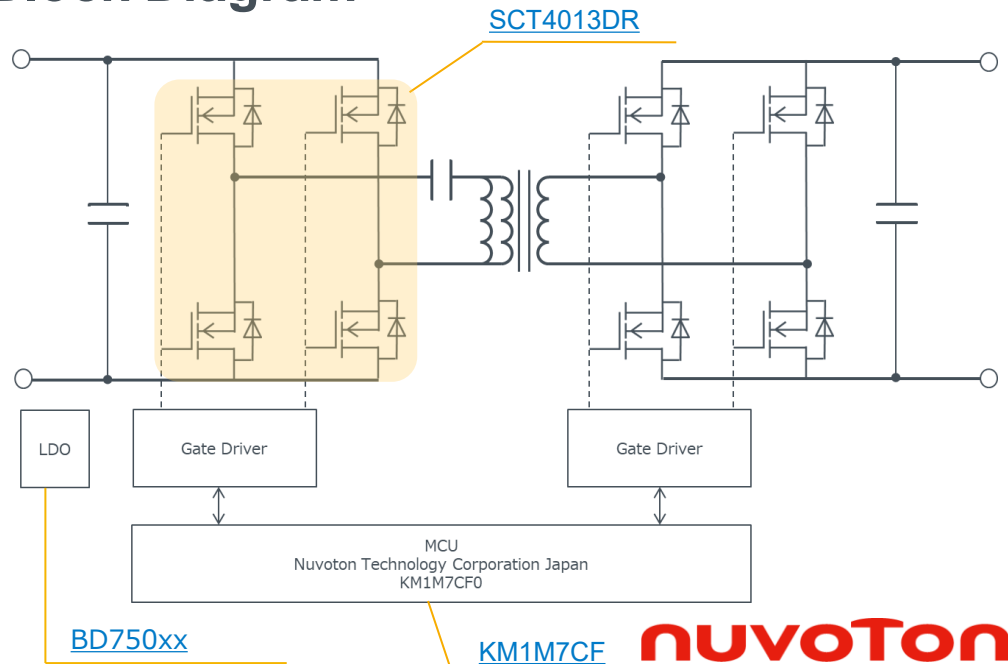

* Jump to an external website



<Specification>

Input : DC390V
 Output : DC48V, 53A
 fsw = 125kHz (Normal state)
 Efficiency : 97.3%

<Circuit configuration>

Full bridge LLC Converter
 High-resolution PWM with 32-bit MCU(Nuvoton KM1M7CF0)
 Controlling the primary and secondary sides with a single MCU
 Using SiC MOSFETs for Primary side switching

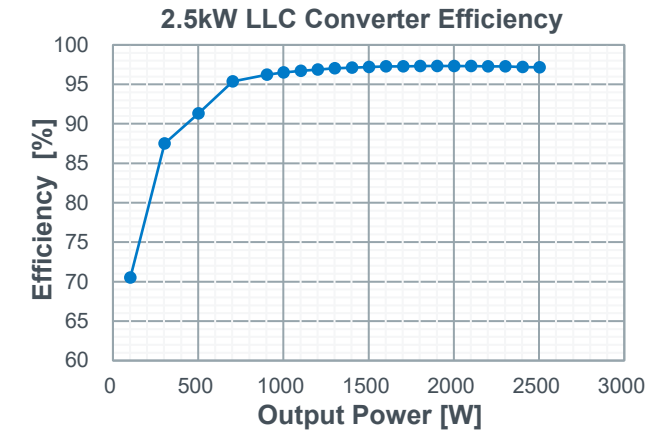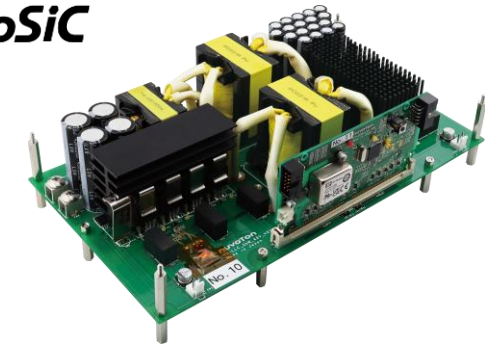* For more details about the board, please contact Nuvoton Technology Cooperation Japan.




What is LLC Converter?

LLC converters are power conversion circuits that utilize resonance phenomena, consisting of a primary-side excitation inductance, resonant inductor, resonant capacitor, switching element, and secondary-side rectifier circuit. By employing soft-switching technologies such as ZVS (Zero Voltage Switching) (primary-side switch) and ZCS (Zero Voltage Switching) (secondary-side switch), switching losses are significantly reduced, achieving high efficiency and low EMI by suppressing switching noise. They are applicable to a variety of power conversion circuits.


LLC converters that accept DC 400V input are used in applications where the DC voltage is converted from a commercial AC power input via a PFC (Power Factor Correction) and then converted to the voltage required by the system for distribution (server power supplies, industrial power supplies, PV hybrid inverters, ESS, UPS, xEV OBC (onboard charger), etc.), as well as for voltage conversion from the 400V battery of xEVs (xEV DC-DC converters, etc.). The secondary-side full-bridge rectifier circuit is a topology commonly used for relatively high power (up to several tens of kW) and relatively high output voltage (>48V).

This reference design is a DC 390V input, 48V output, 2.5kW LLC converter that incorporates Nuvoton Technology's high-resolution 32-bit MCU (KM1M7CF0) for power control and uses SiC MOSFETs as the primary switching element.


Data Center / AI Server PSU

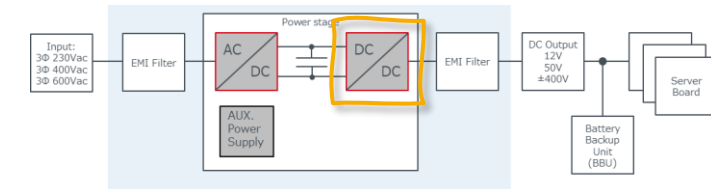


Industrial PSU

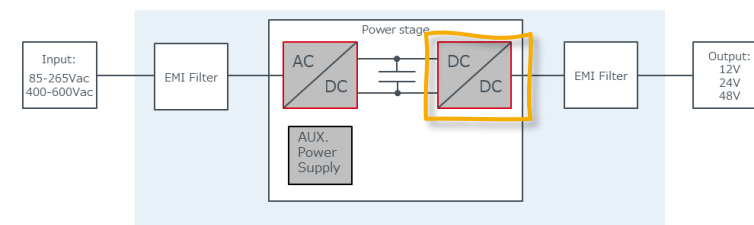

xEV OBC

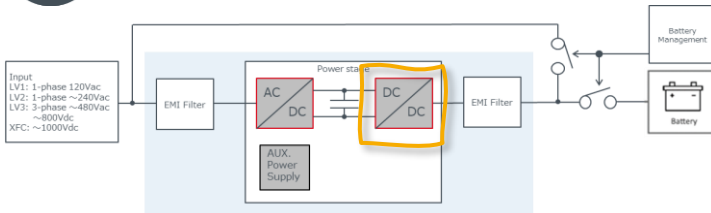

xEV DC-DC

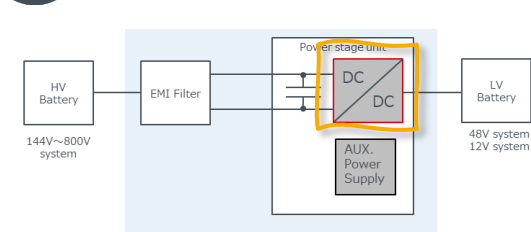

Reference Designs for Power Supply Unit (PSU)




REF67010 : 3.6kW Interleaved PFC
APEVK66001 : 3.6kW Totem Pole PFC



REF68020
2.5kW LLC Converter



REFACDC025
24W 12Vout
AC-DC Converter

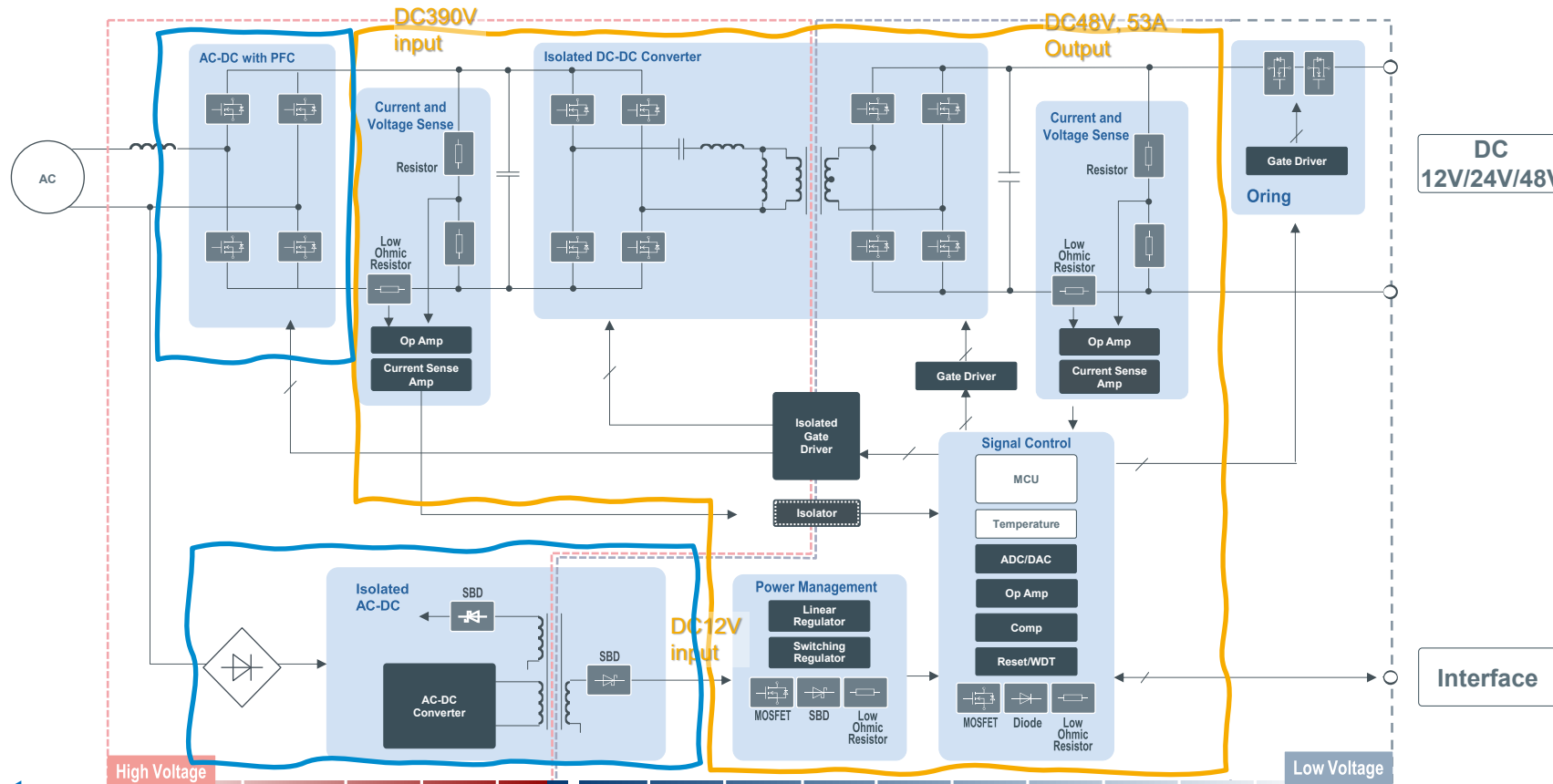









 : Target application
 : Sub system
 : ROHM product category
 : ROHM product category (Discrete device)
 : ROHM product category (Contact us)
 : Non ROHM product

Simulate LLC Converter Circuits (Simulation tools and Demo Circuits)



Reduce design time by utilizing simulation during power electronics circuit design. ROHM provides online tools and demo circuits for offline tools, allowing you to immediately perform simulations or obtain simulation circuits via the web.

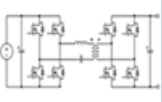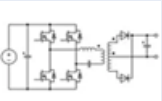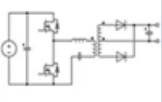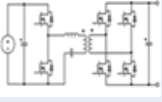Contents		ROHM Solution Simulator	ROHM PLECS Simulator	LTSpice® Demo Circuits	PLECS® Demo Circuits	
Online / For Offline		Online simulation available		Downloadable circuits for offline tools		
Simulation tool		PARTQUEST™ Explore 	PLECS® 	LTSpice® 	PLECS® 	
Features		High analog waveform reproducibility, AC analysis possible.	Loss and heat can be verified in seconds.	High analog waveform reproducibility, AC analysis possible.	Loss and heat can be verified in seconds.	
Used for		Verify surges, ringing, AC characteristics, and so on, to design for stability and safety.	Select devices based on the losses and heat generation at the topology circuit.	Verify surges, ringing, AC characteristics, and so on, to design for stability and safety.	Select devices based on the losses and heat generation at the topology circuit.	
LLC Converter Simulation Circuit			ROHM PLECS Simulator C-014-D : Discrete Package C-014-DOT : DOT-247 Package	C-014-D4 : Full Bridge LLC, Full Bridge Recti. TO-247-4L package C-014-DOT : Full Bridge LLC, Full Bridge Recti. DOT-247 package	C-014-D : Full Bridge LLC, Full Bridge Recti. Discrete Package C-014-DOT : Full Bridge LLC, Full Bridge Recti. DOT-247 package	
		C-013. Full Bridge LLC, Diode Recti.				
		C-012. Half Bridge LLC, Diode Recti.			C-012 : Half Bridge LLC, Diode Recti. TO-247N package	
			ROHM PLECS Simulator C-023-D : Discrete Package C-023-DOT : DOT-247 Package		C-023-D : Half Bridge LLC, Full Bridge Recti. Discrete Package C-023-DOT : Half Bridge LLC, Full Bridge Recti. DOT-247 Package	


Recommended Products for 3kW~5.5kW Power Supply Unit (PSU)

Totem Pole PFC
Fast Leg : SCT40xxDR(TO-247-4L) SCT40xxDLL(TOLL)
Slow Leg : R60xxWNZ4(TO-247N)* R60xxWNJ3(DFN8080)*

Isolated Gate Driver
For SiC : BM61S41RFV-C
For SJ-MOS : BM61M41RFV-C

AUX power supply
AC-DC Converter Built in 1700V SiC : BM2SC Series AC-DC Controller : BD768x Series

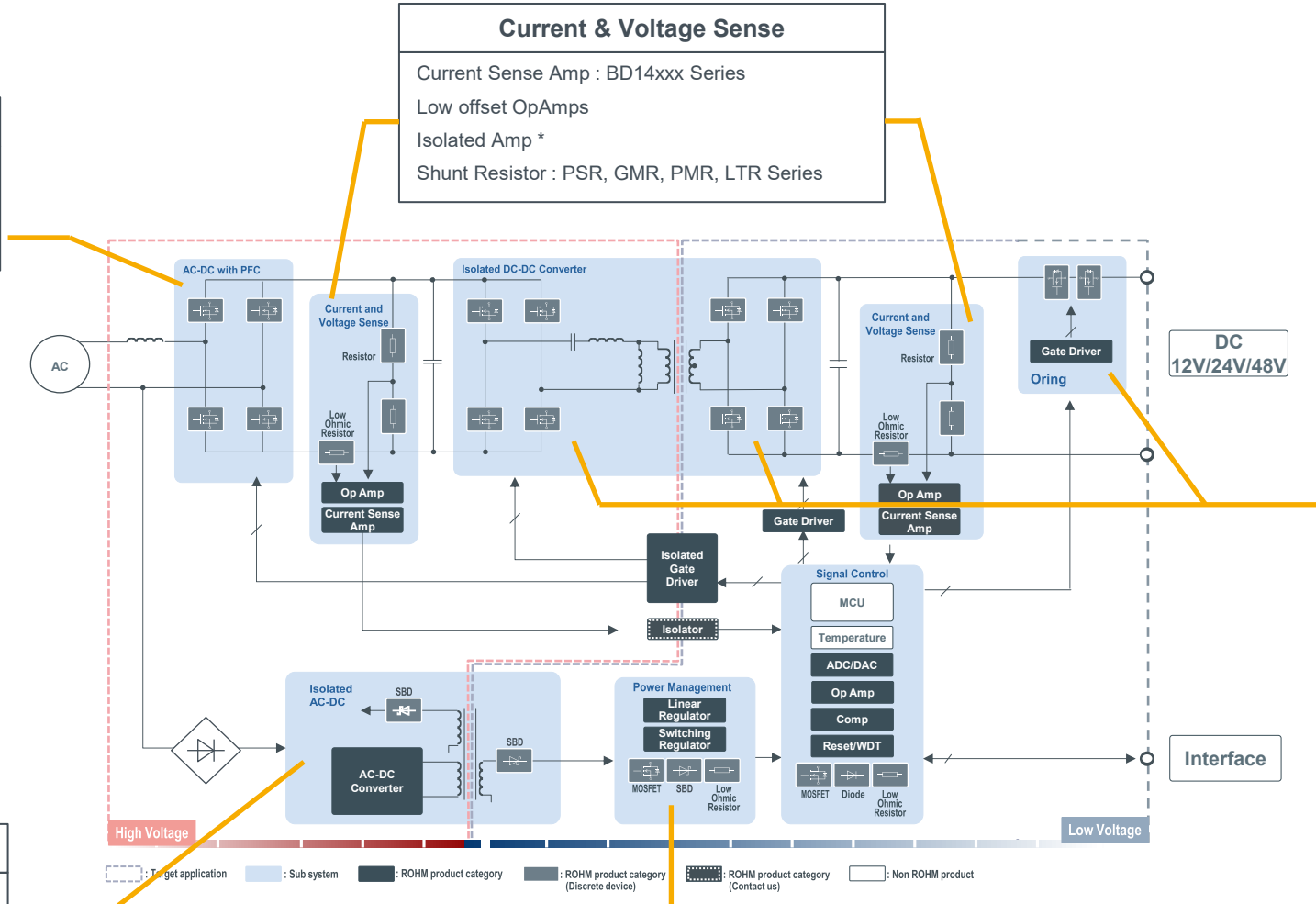Current & Voltage Sense
Current Sense Amp : BD14xxx Series Low offset OpAmps Isolated Amp * Shunt Resistor : PSR, GMR, PMR, LTR Series



LLC Converter(Primary)
SJ-MOS R60xxWNZ4(TO-247N)* R60xxWNJ3(DFN8080)*
SiC-MOS SCT40xxDWA(TO-263-7L) SCT40xxDLL(TOLL)
GaN HEMT GNP30xxTD-Z(TOLL)*
Gate Driver for SJ-MOS BM62T40RFU *
Gate Driver for SiC-MOS BM61S41RFV
Gate Driver for GaN-HEMT BM6GD11BFJ

LLC Converter(Secondary) Oring [option]
Si-MOSFET 30V RS6Exx, RS7Exx 40V RS6Gxx, RS7Gxx, RH6Gxx 60V RH6, RH8, RS6L, RG6L, RS7L 80V RS7N200BH(DFN5060)* 100V RS7P200CH *
Gate Driver for Si-MOSFET BD2310G BD2320EFJ BM60214FU *

Power Management
LDOs DC/DC Converter Flyback DC-DC Converter : BD7Fxx Series

* : Under Development
As Of Apr.2026



Electronics for the Future

Important Notes on the Use of Reference Designs

- 1) The contents of this document are subject to change without notice for the purpose of improvement.
- 2) ROHM provides reference designs (including, but not limited to, circuit diagrams, layout data, parts lists, reference boards and their evaluation results, etc.) and all materials related to evaluation boards (hereinafter collectively referred to as "Reference Designs, etc.") to customers for the purpose of referencing them in the development of devices, equipment, software, etc. incorporating ROHM products (hereinafter collectively referred to as "Customer Products"). The design, verification, etc. required for the development of the Customer's Product shall be done at the customer's responsibility and expense. In no event shall the customer use the Reference Designs, etc. for any purpose other than the purpose mentioned above.
- 3) Reference Designs, etc. are provided on an "as is" basis. ROHM disclaims all warranties, express or implied, including, but not limited to, warranties of usefulness, functionality, accuracy, merchantability, and fitness for a particular purpose. In no event shall ROHM be liable for any damages (including, but not limited to, lost profits or other incidental, consequential, or punitive damages) arising out of, related to or in connection with the use of or application of the Reference Designs, etc. whether in contract or tort. For the avoidance of doubt, ROHM does not warrant that the Reference Designs, etc. will work with the Customer's Product.
- 4) When using Reference Designs, etc. be sure to request and verify the latest specifications (including the specifications of the products that compose the Reference Design, etc.) separately.
- 5) The customer shall be responsible for implementing safety measures such as derating, redundant design, fire prevention, backup, and fail-safe measures, etc., to prevent personal injury, fire damage, etc., caused by the Customer's Product developed with Reference Designs, etc. ROHM assumes no liability whatsoever for any use in excess of the ratings or in case of failure to observe the instructions for use.
- 6) The application circuit examples, constants, and other information provided in Reference Designs, etc. are intended to illustrate standard operation and usage. Therefore, when designing for mass production, please take into account various external conditions.
- 7) Reference Designs, etc. are intended to show typical operations and examples of application circuits, etc., and do not constitute a license, express or implied, to implement or use any intellectual property rights or any other rights of ROHM or any other company. ROHM shall not be liable for any disputes arising from, related to or in connection with the use of the Reference Designs, etc.
- 8) Please make sure to contact ROHM and obtain ROHM's consent before using the Reference Designs, etc. for the following Customer's Product that requires particularly high reliability. Transportation equipment (in-vehicle, ship, railroad, etc.), trunk line communication equipment, traffic signal equipment, disaster and security equipment, safety equipment, medical equipment, servers, solar cells, power transmission systems, etc.
- 9) Do not use Reference Designs, etc. for the following Customer's Product that requires extremely high reliability. Aerospace equipment, nuclear power control equipment, submarine relay equipment, etc.
- 10) Do not use Reference Designs, etc. for military use, such as development of weapons of mass destruction, or for any other military purpose.
- 11) ROHM does not assume any liability for any accidents or damages caused by non-compliance with the descriptions in this document.
- 12) The information contained in this document has been carefully prepared to ensure accuracy. However, ROHM shall not be liable for any loss or damage incurred by customers due to errors or misprints in this document.
- 13) Do not reproduce or duplicate any part of this document in any form or by any means without ROHM's permission.



Thank you for your accessing to ROHM product informations.
More detail product informations and catalogs are available, please contact us.

ROHM Customer Support System

<http://www.rohm.com/contact/>