

DC-DC Buck Synchro Converter 2-Phase $V_o=250V$ $I_o=200A$

Input : $V_{in}=800V$

Output : $V_o=250V$
 $I_o=200A$

Gate Drive : $V_d=18V$
 $R_{source}=2\Omega$
 $R_{sink}=1\Omega$


Q1 : BSM120D12P2C005
SiC Power Module
(1200V 120A)

L1, L2 : 100uH



C1 : 10uF

$T_j=100^\circ C$




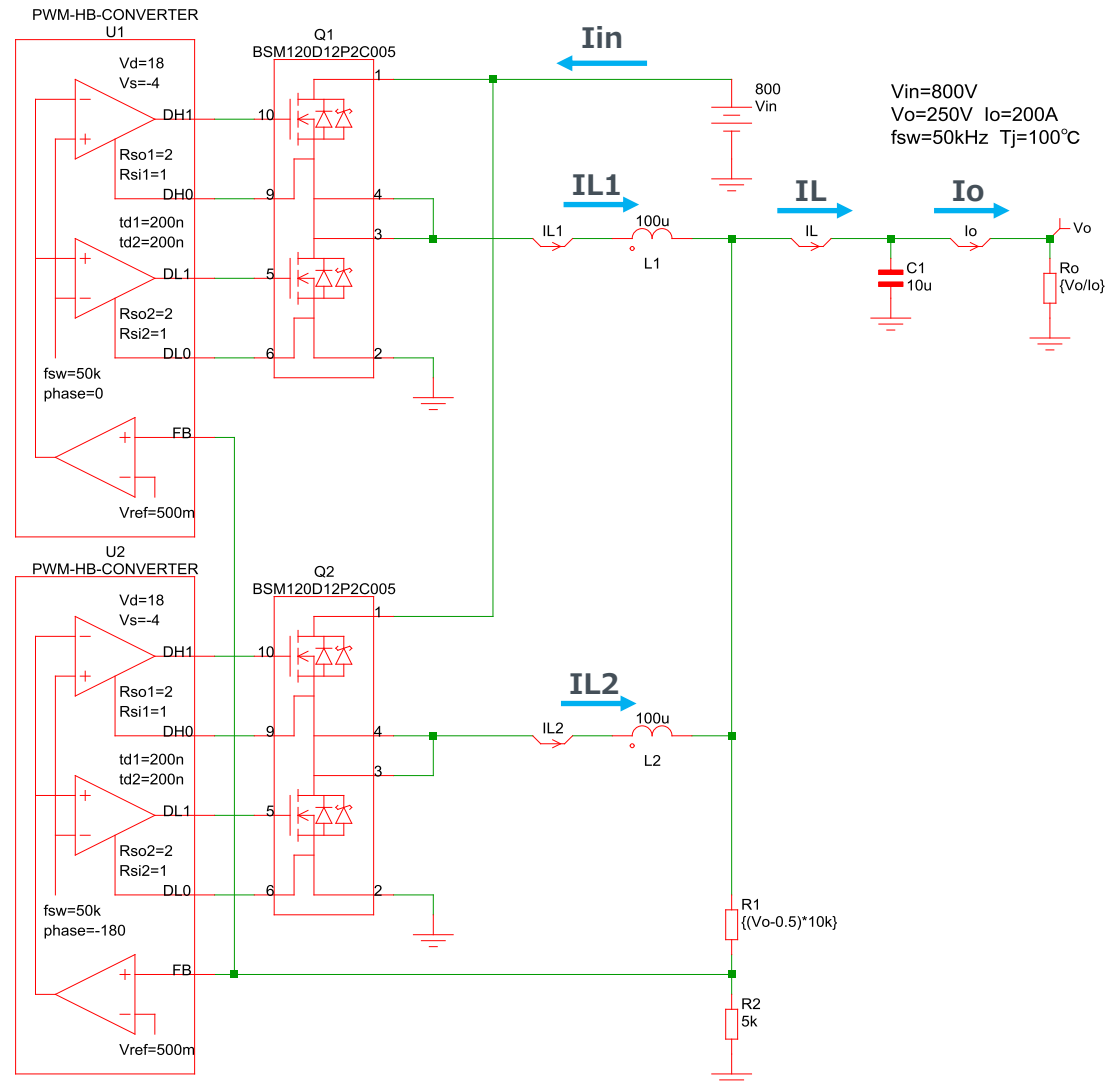
DC-DC Buck Synchro Converter 2-Phase $V_o=250V$ $I_o=200A$ Simulation Circuit



Simulation Waveform

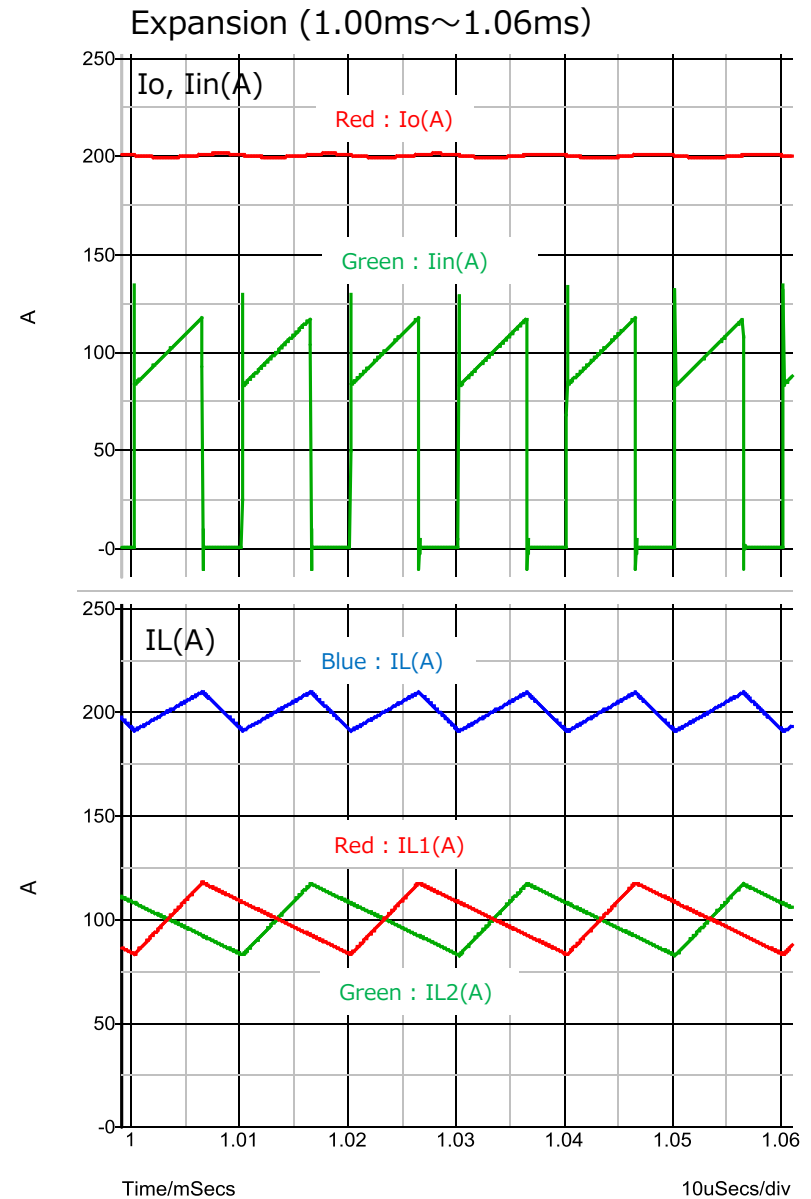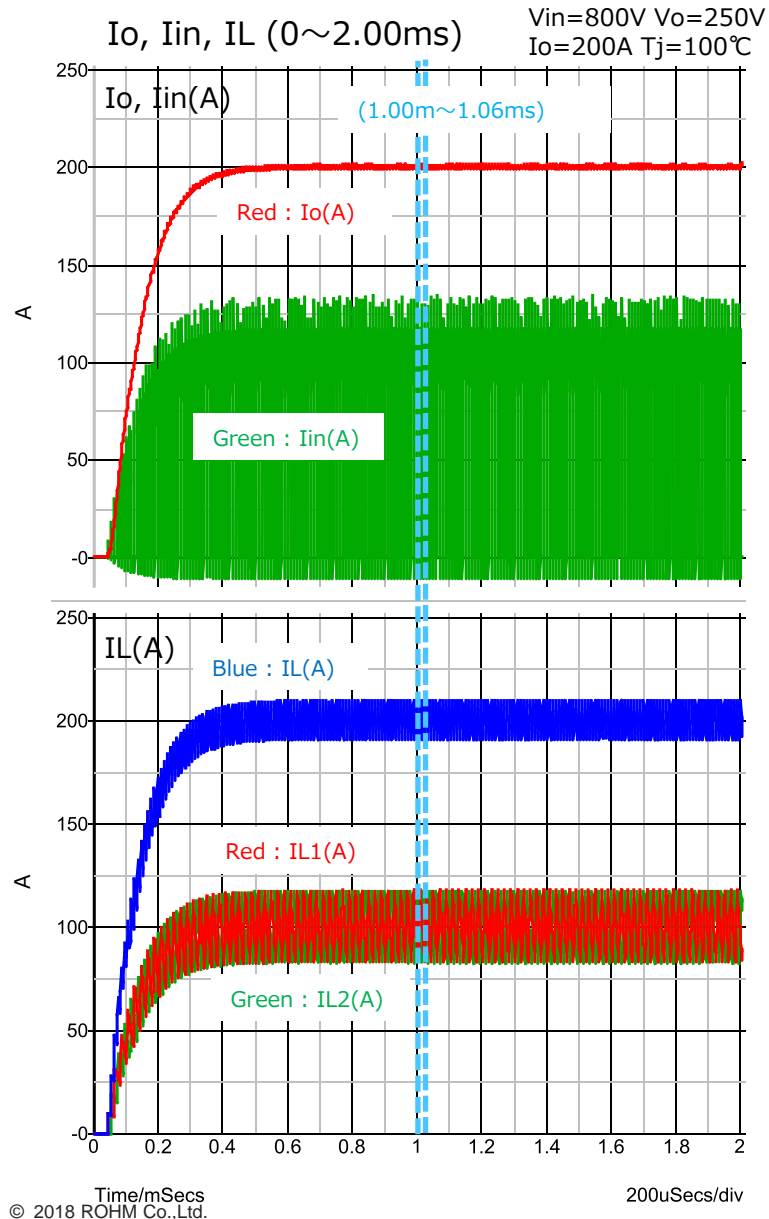

Efficiency, Power Dissipation 1

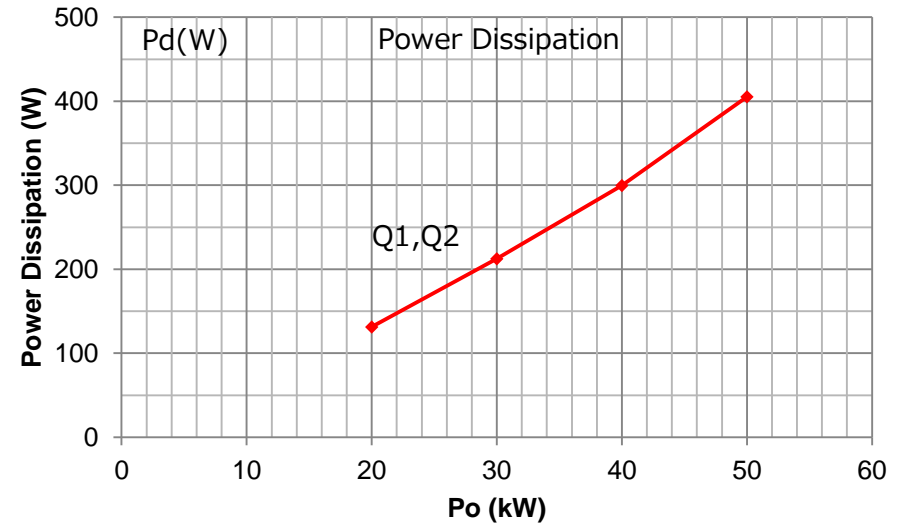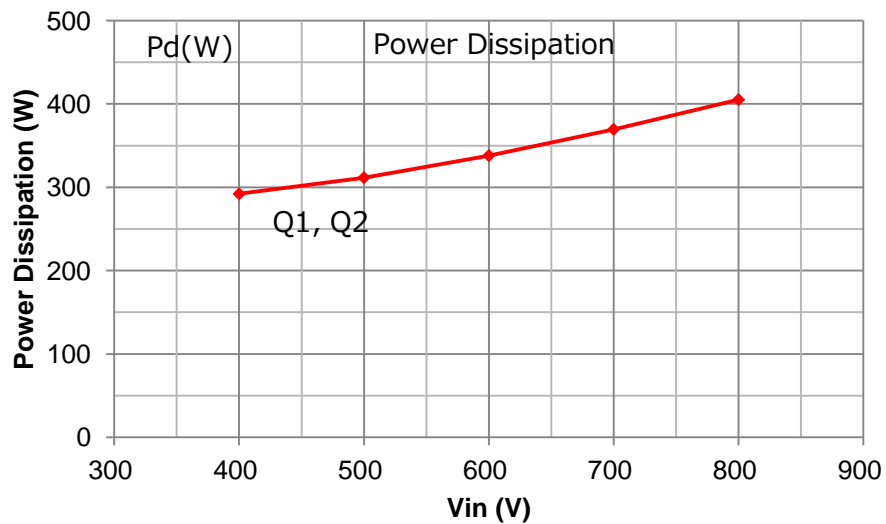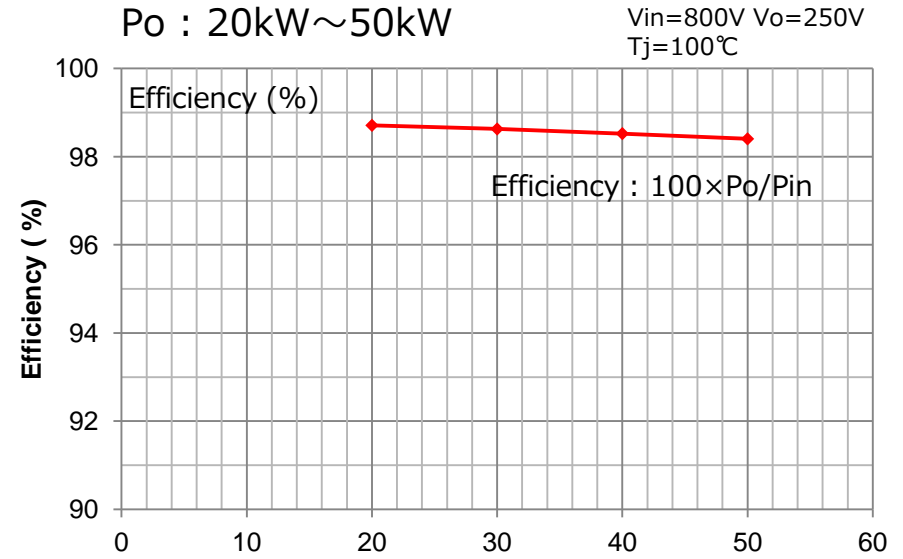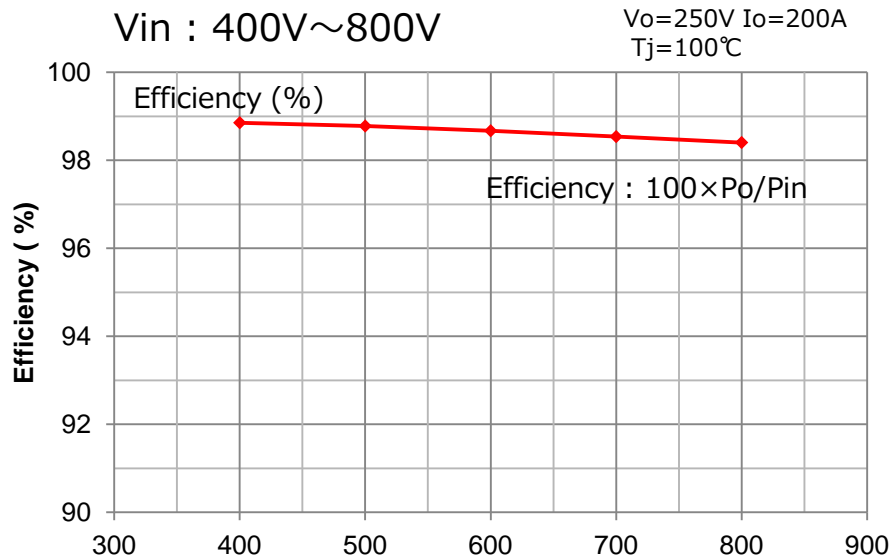

Efficiency, Power Dissipation 2

