

# DC-DC Buck Synchro Converter $V_o=250V$ $I_o=100A$

## DC-DC Buck Synchro Converter $V_o=250V$ $I_o=100A$ Simulation Circuit

Input :  $V_{in}=800V$

Output :  $V_o=250V$   
 $I_o=100A$


Gate Drive :  $V_d=18V$   
 $R_{source}=2\Omega$   
 $R_{sink}=1\Omega$

**Q1 : BSM120D12P2C005**  
**SiC Power Module**  
**(1200V 120A)**

**L1 : 100uH**


**C1 : 10uF**

**$T_j=100^\circ C$**

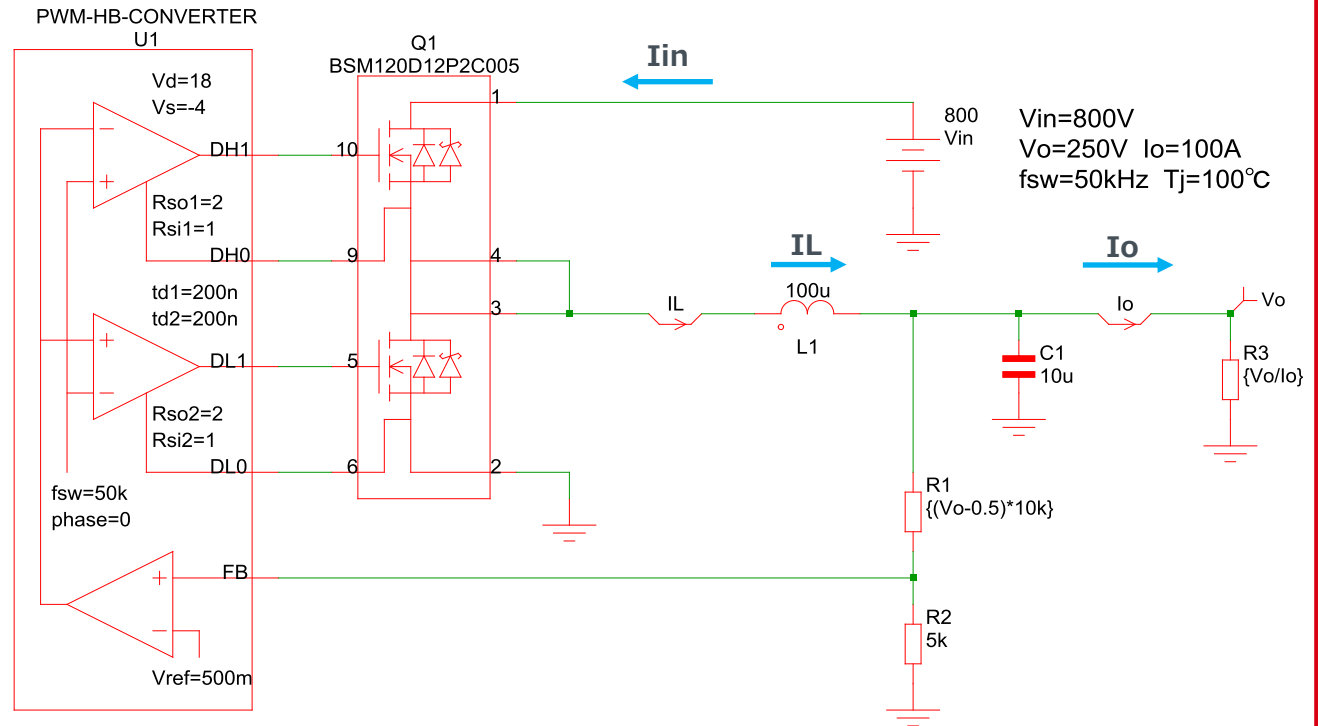

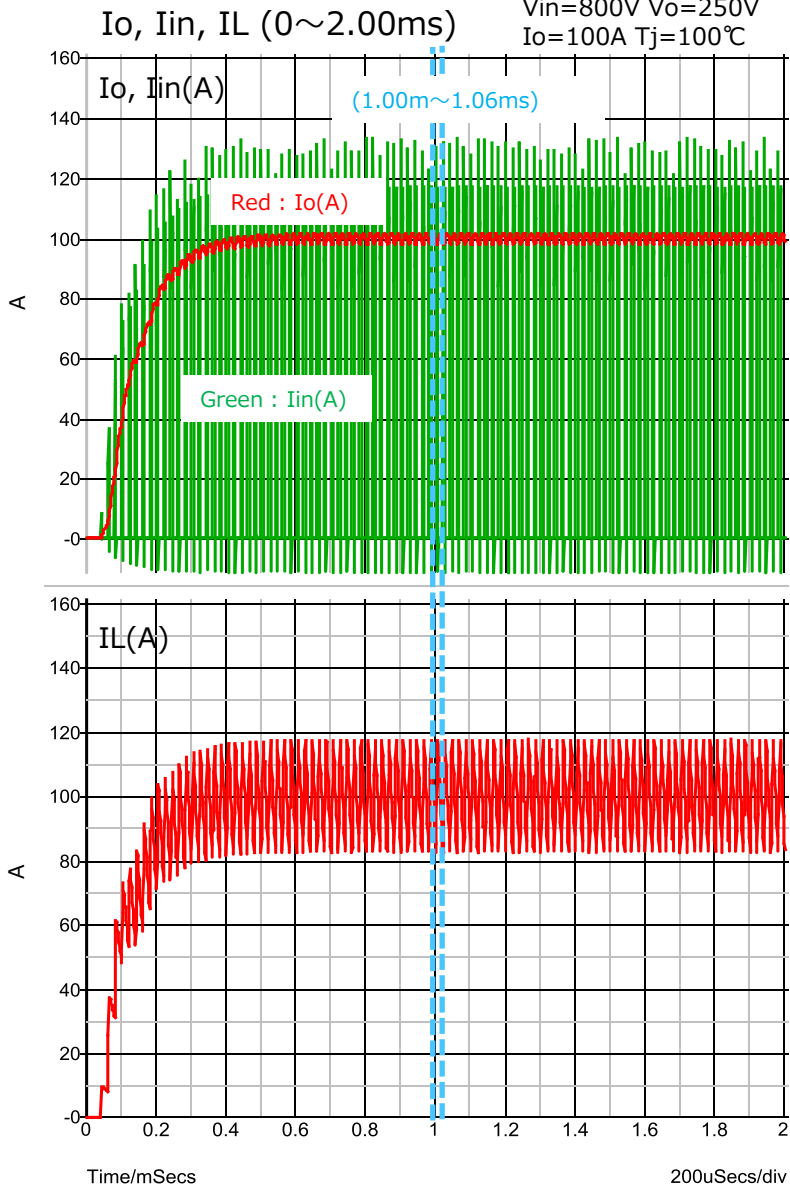
# Simulation Waveform





$V_{in}=800V$   $V_o=250V$   
 $I_o=100A$   $T_j=100^{\circ}C$



Expansion (1.00ms~1.06ms)

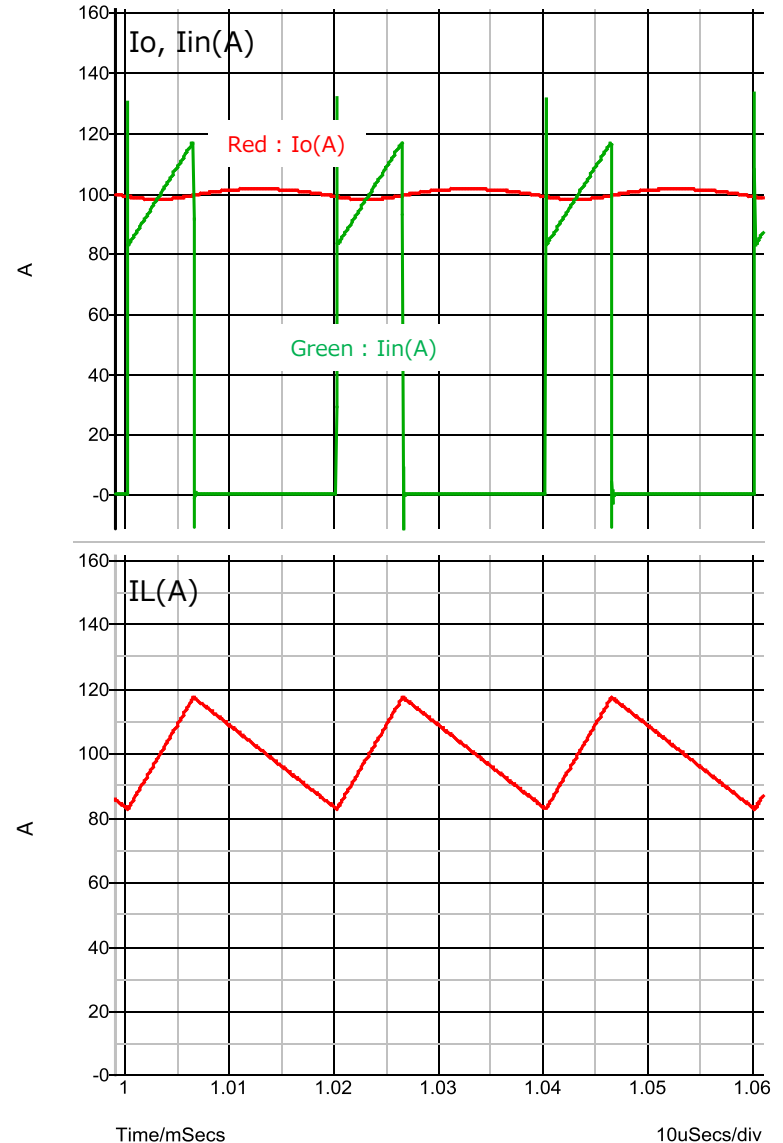

# Efficiency, Power Dissipation 1

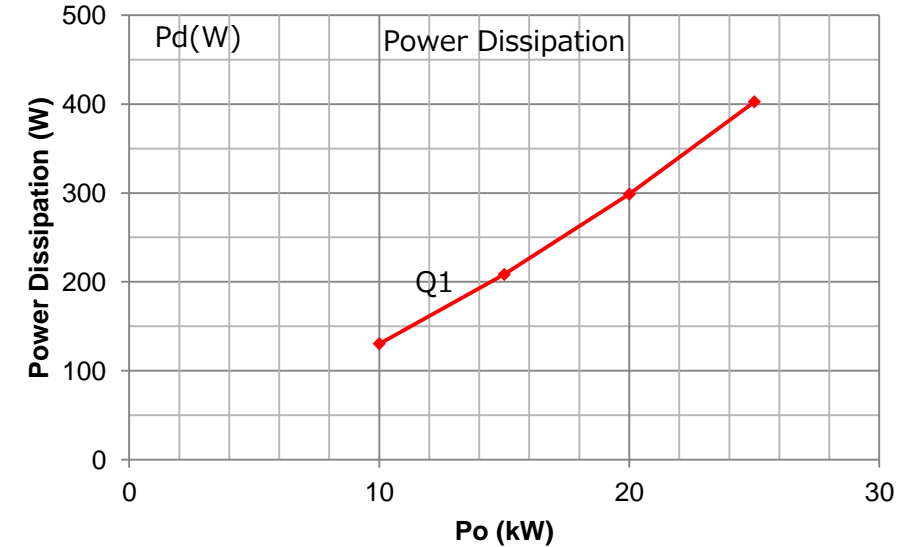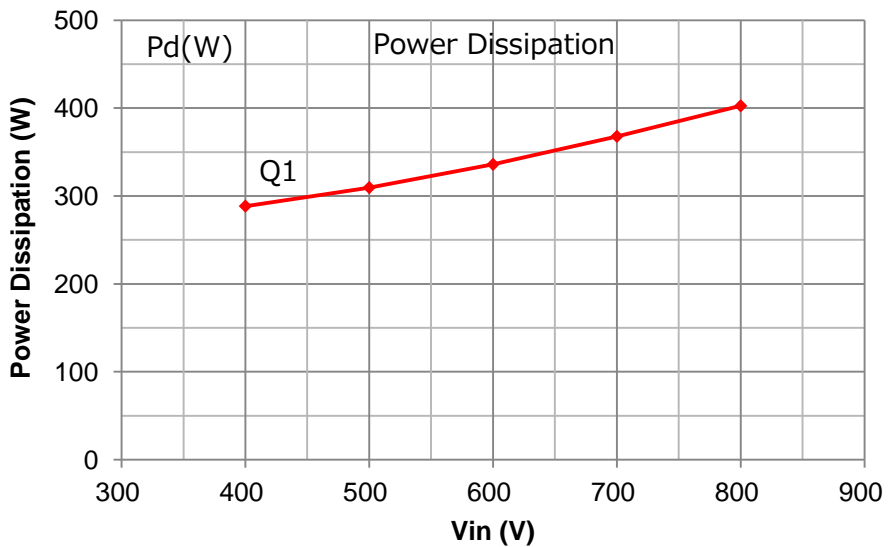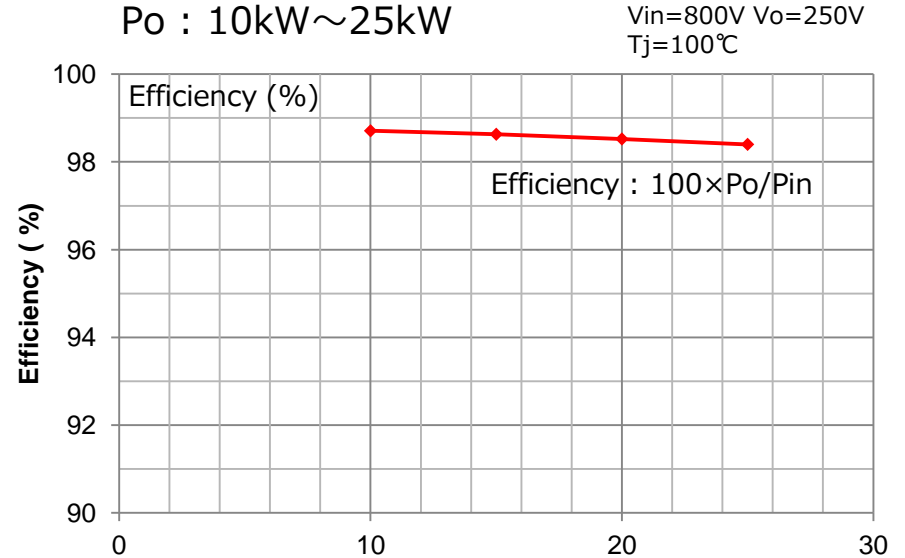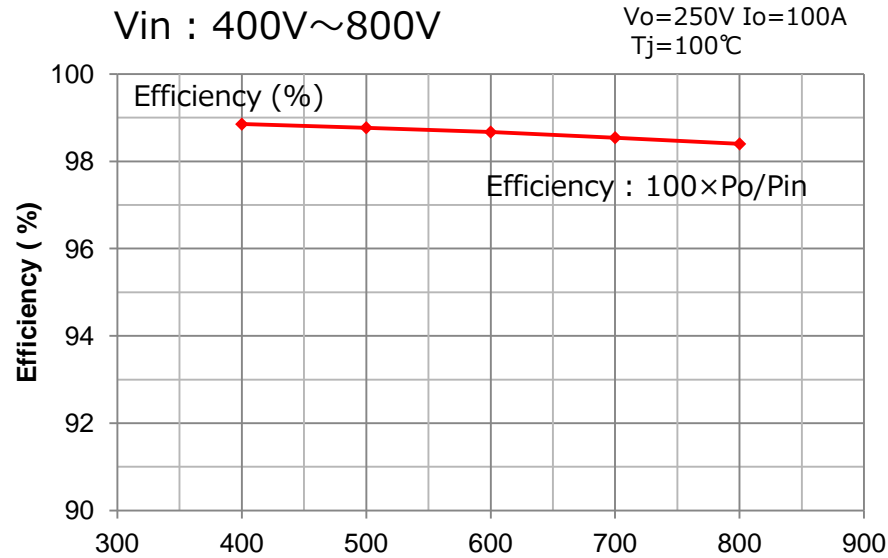

# Efficiency, Power Dissipation 2

