

3-Phase 4-Wire PS Inverter Po=6kW

3-Phase 4-Wire PS Inverter Simulation Circuit

Input: $V_{in}=200V_{dc} + 200V_{dc}$

Output: $P_o=6kW$ 50Hz
115/200Vac 17.32Aac

PWM: $f_{sw}=20kHz$
 $td1=100ns$
 $td2=100ns$

Gate Drive: $V_d=10V$ $V_s=-2V$
 $R_{source}=5\Omega$
 $R_{sink}=2\Omega$

Q1,2,3,4,5,6: R6030MNX
Si MOSFET (600V 30A)


L1,2,3: 1mH

$T_j=100^\circ C$

SIMetrix SPICE Simulation Data File




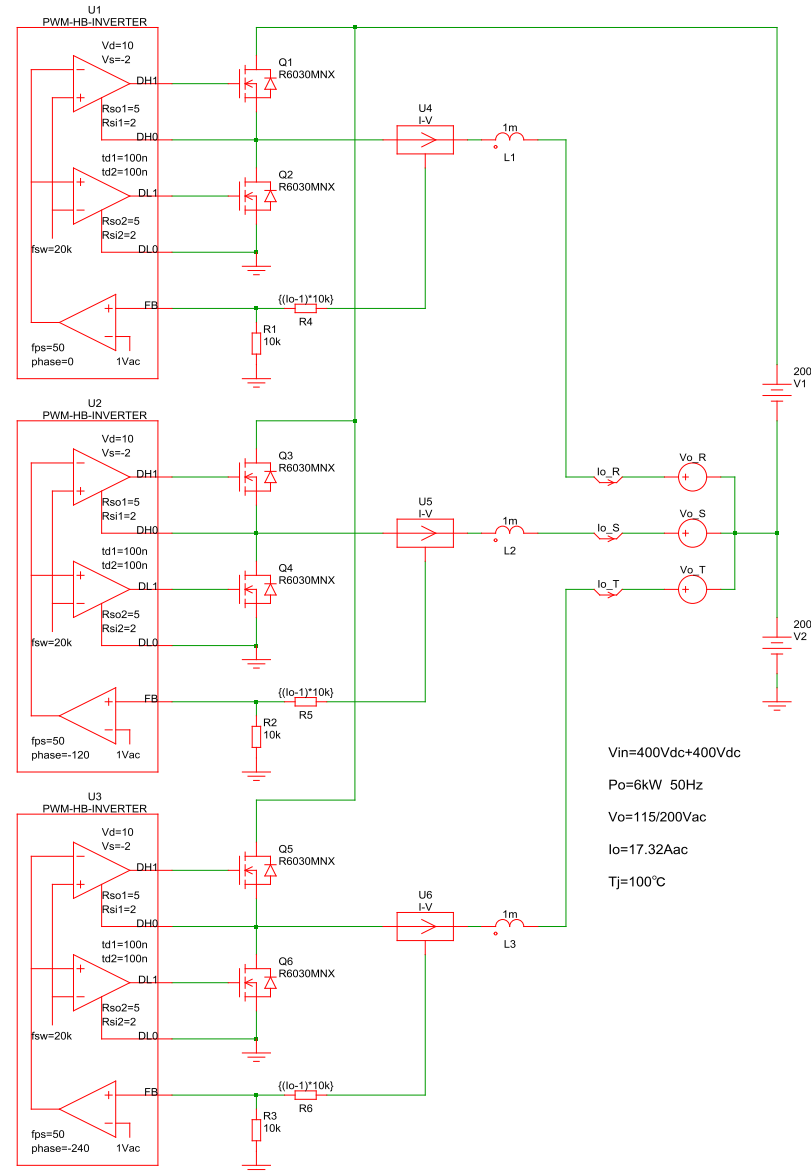DC-AC 3-Phase 4-Wire PS Inverter Po=6kW.wxsch




Simulation Waveform 1



Id_Q5,Q3,Q1
Io_R,S,T (0~20ms)

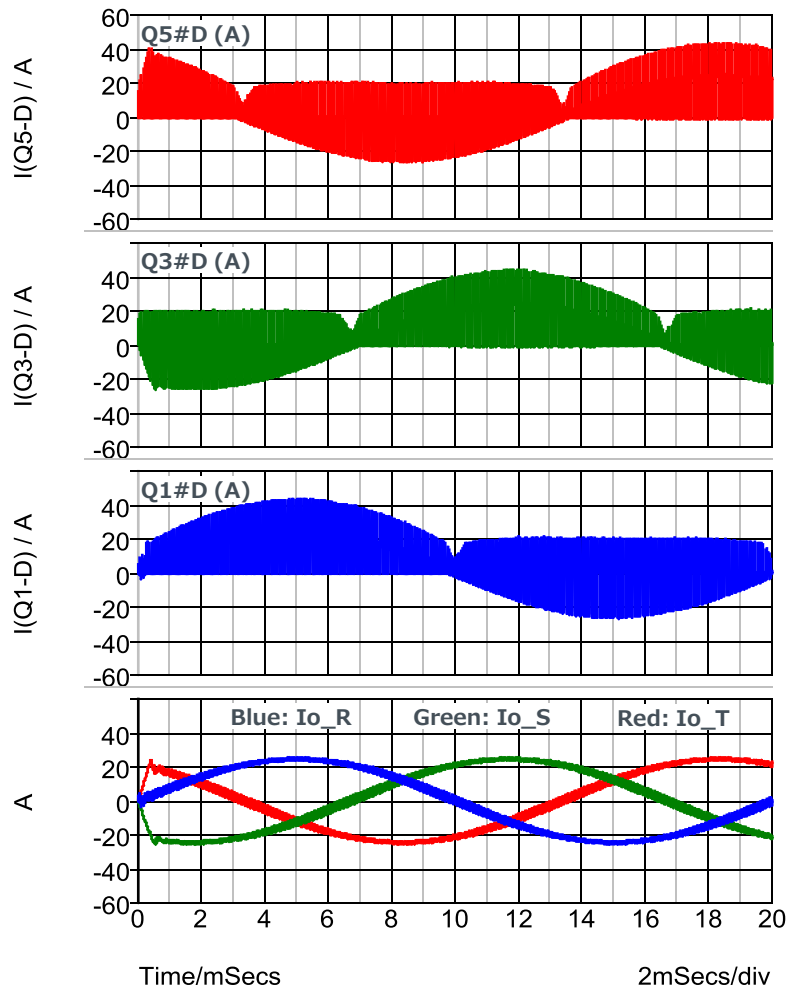


E_Q1,Q2
Pd_Q1,Q2 (0~20ms)

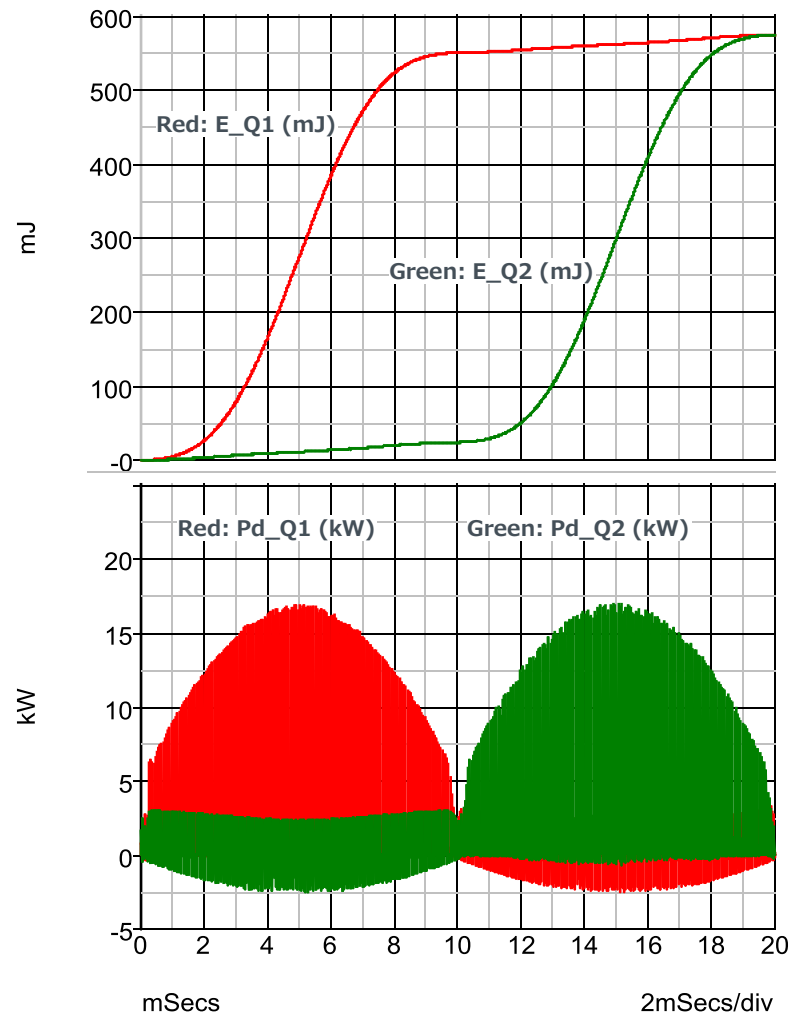

Simulation Waveform 2

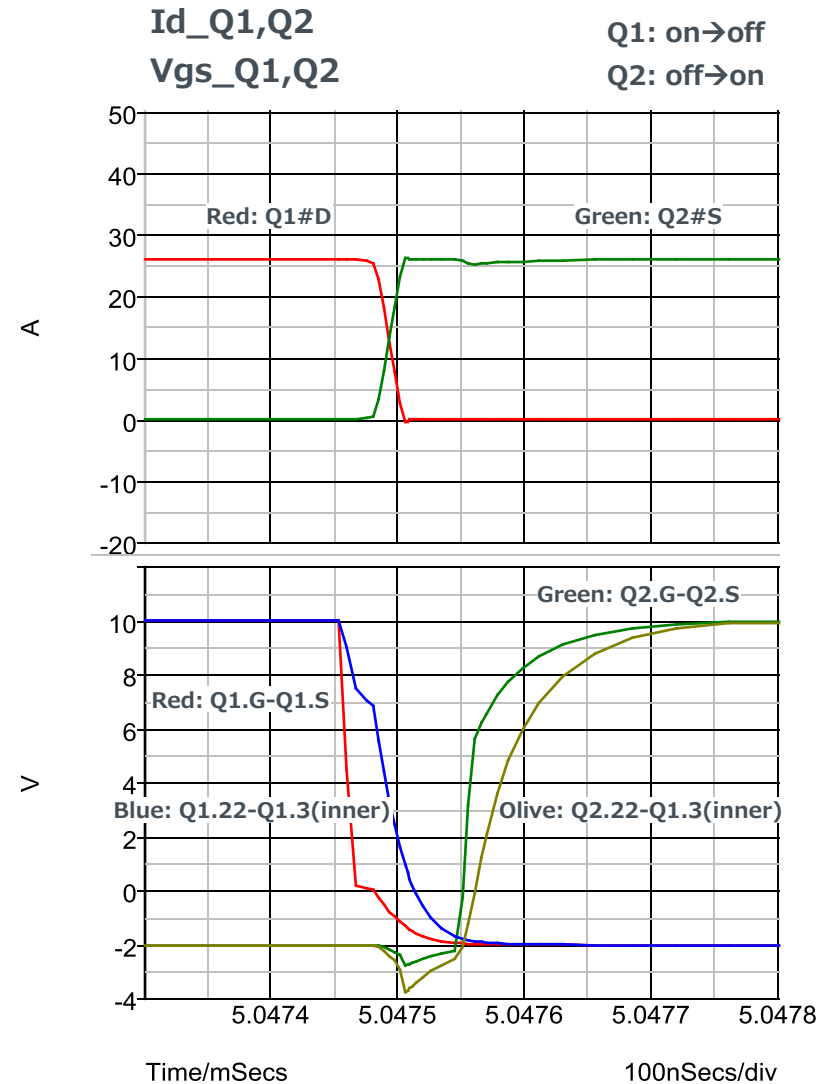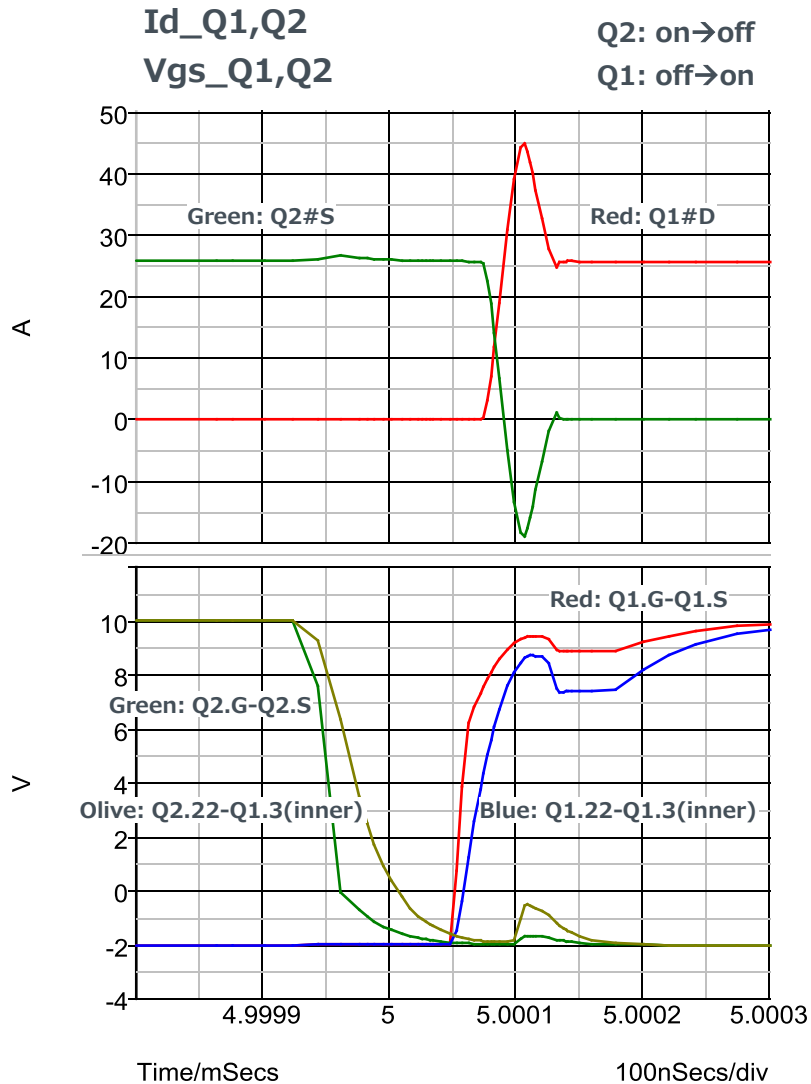

fsw=20kHz~100kHz

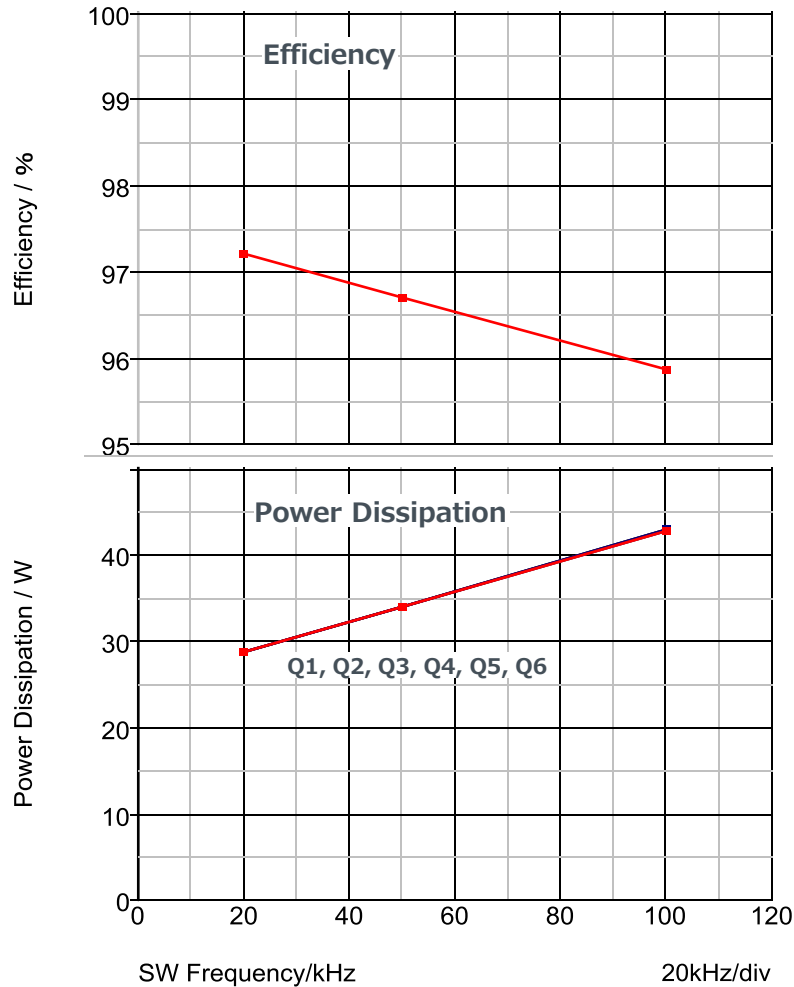

Junction Temperature=-25°C~125°C

