### **Featured Products**



Achieves class-leading\* low  $V_F$  performance in low voltage applications

\*ROHM Sept. 2025 study

Ultra-Low V<sub>F</sub>, Low I<sub>R</sub> Schottky Barrier Diode

RBE01VYM6AFH



### Overview: Ultra-Low $V_F$ , Low $I_R$ Schottky Barrier Diode (SBD)





The RBE01VYM6AFH is an SBD optimized for low-voltage operation, achieving both ultra-low  $V_F$  and low  $I_R$  - characteristics typically in a trade-off relationship. This makes it suitable for a broad spectrum of applications, from photovoltaic protection in automotive ADAS cameras to rectification in consumer electronics.

### **Features**

 Protects against photovoltaic voltage during power OFF, safeguarding high-resolution cameras from damage and degradation, improving reliability

AEC-Q101 qualified, delivering the stringent performance required for photovoltaic voltage countermeasures in ADAS\* cameras Market requirements: Forward voltage  $V_F$ <300mV @ Forward current  $I_F$ =7.5mA,  $T_a$ =-40°C Reverse current  $I_R$ <20mA @ Reverse voltage  $V_R$ =3V,  $T_a$ =125°C

• Specialized low-voltage, low-power operation ensures suitability for a broad range of applications, from automotive to consumer electronics

Absolute Max Rating:  $V_R$ =6V

Ultra-low V<sub>F</sub>: 175mV @ I<sub>F</sub>=7.5mA, T<sub>a</sub>=25°C


Low  $I_R$ : 15µA @  $V_R$ =3V,  $T_a$ =25°C

\*Advanced Driver Assistance Systems



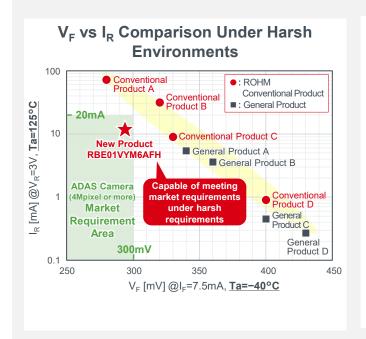
# Improves Reliability by Protecting High-Resolution Cameras from Damage due to Photovoltaic Voltage During Power OFF





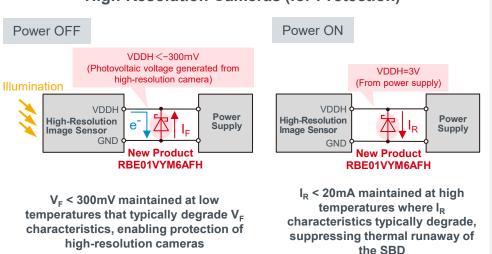
## Application Example of ROHM's New SBD in ADAS High-Resolution Cameras (for Protection)



Ultra-low  $V_F$  maintains protection voltage at low temperatures, while low  $I_R$  suppresses thermal runaway caused by reverse leakage current at high temperatures
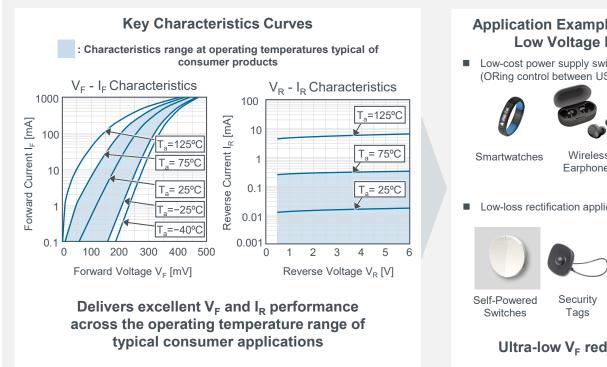
## Low-Voltage, Low-Power Design Ensures Suitability for Applications Ranging from Automotive to Consumer Electronics





Application Examples of ROHM's New SBD in the Low Voltage Range (for Rectification) Low-cost power supply switching applications (ORing control between USB and battery) New Product RBE01VYM6AFH **USB** Power Supply Wireless Li-lon Load Earphones Batterv Low-loss rectification applications (energy harvesting) **New Product** RBE01VYM6AFH **EM Induction** Power Regulator Generation...etc Load Ultra-low V<sub>F</sub> reduces application power loss

Provides superior performance in low-voltage rectification applications

# Ultra-Low $V_F$ , Low $I_R$ Schottky Barrier Diode [RBE01VYM6AFH]: Key Specifications



	Part No.	Absolute Max Ratings (T <sub>c</sub> =25°C, unless otherwise specified)					Electrical Characteristics (T <sub>j</sub> =25°C)		Automotive-	Package
	Part No.	V <sub>RM</sub> [V]	V <sub>R</sub> [V]	I <sub>o</sub> [A] 60Hz Tc=120°C	I <sub>FSM</sub> [A] 60Hz 1 Cycle	T <sub>j</sub> (Max) [°C]	V <sub>F</sub> (Max) [mV] @ I <sub>F</sub> =7.5mA	I <sub>R</sub> (Max) [μΑ] @V <sub>R</sub> =3V	Grade AEC-Q101	[mm]
New	RBE01VYM6AFH ∰ <mark>ख</mark>	6	6	0.1	1	125	200	30	YES	SOD-323HE (TUMD2M) 2.5×1.4×0.6

Click on the (a) icon to access the product page and the icon to view the datasheet on ROHM's website.

Package notation in parenthesis ( ) denotes the ROHM package type.

### **Application Examples**

#### [Protection]

- · Vehicle cameras
- · Surveillance cameras
- · Drones, etc.



### [Rectification]

- Smartwatches
- · Wireless earphones
- · Security tags, etc.



**Protects high-resolution cameras** 

**Contributes to lower loss** 

#### **Notice**

- The information contained in this document is intended to introduce ROHM Group (hereafter referred to as ROHM) products. When using ROHM products, please verify the latest specifications or datasheets before use.
- ROHM does not warrant that the information contained herein is error-free. ROHM shall not be in any way responsible or liable for any damages, expenses, or losses incurred by you or third parties resulting from errors contained in this document.
- The information and data described in this document, including typical application circuits, are examples only and are not intended to guarantee to be free from infringement of third parties intellectual property or other rights. ROHM does not grant any license, express or implied, to implement, use, or exploit any intellectual property or other rights owned or controlled by ROHM or any third parties with respect to the information and data contained herein.
- When exporting ROHM products or technologies described in this document to other countries, you must abide by the procedures and provisions stipulated in all applicable export laws and regulations, such as the Foreign Exchange and Foreign Trade Act and the US Export Administration Regulations, and follow the necessary procedures in accordance with these provisions.
- No part of this document may be reprinted or reproduced in any form by any means without the prior written consent of ROHM.
- The information contained in this document is current as of September 2025 and is subject to change without notice.



ROHM Co., Ltd.

21 Saiin Mizosaki-cho, Ukyo-ku Kyoto 615-8585 Japan

www.rohm.com