

# BD7682FJ-LB-EVK-402 Parts list

Item	Specifications	Parts name	Manufacture	
Capacitor	C1, C9	0.033 $\mu$ F, 650 Vac	PHE450RB5330J	KEMET
	C10	N.C.	-	-
	C12	2200 pF, 50 V	08055C222JAT2A	AVX
	C14	330 pF, 1 kV	225000111543	YAGEO
	C15	0.1 $\mu$ F, 50 V	UMK212BJ104KGHT	TAIYO YUDEN
	C2, C3, C4	100 $\mu$ F, 450 V	450BXW100MEFR18X30	RUBYCON
	C5	22 $\mu$ F, 35 V	UVR1V220MDD1TD	NICHICON
	C6	4.7 $\mu$ F, 35 V	UVR1V4R7MDD1TD	NICHICON
	C7	0.1 $\mu$ F, 35 V	GRM21BR71H104JA01L	MURATA
	C8, C11, C13	47 pF, 50 V	GQM2195C1H470JB01D	MURATA
CIN1, CIN2, CIN3, CIN4	2200 pF, X1:760 Vac, Y1:500 Vac	DE1E3RB222M4BR01F	MURATA	
Connector	CN1		691250910003	WURTH ELECTRONIK
	CN2		691250610003	WURTH ELECTRONIK
	CN3		69110171002	WURTH ELECTRONIK
Capacitor	Cout1, Cout2	470 $\mu$ F, 35 V	LER471M1VG16VR6	HERMETI Corp., LTD
	Cout3	220 $\mu$ F, 35 V	UPS1V221MPD	NICHICON
	Cout4	1 $\mu$ F, 50 V	UMK212B7105KG-T	TAIYO YUDEN
	Csubber1	2200 pF, 2 kV	202S41W222KV4E.	JOHANSON DIELECTRICS INC
	CY1, CY2, CY3	2200 pF, X1:760 Vac, Y1:500 Vac	DE1E3RB222M4BR01F	MURATA
Diode	D1, D2, D3, D4, D5, D6, D7, D8, D9, D10, D11, D12, D20, D21	1 A, 1 kV	1N4007	
	D13, D14	1 A, 1 kV	UF4007	
	D15, D16	5.5 A, 200 V	1.5KE200A	
	D17	1 A, 40 V	RB160L-40TE25	ROHM
	D18	0.5 A, 200 V	RF05VAM2S	ROHM
	D19	0.1 A, 90 V	1S535VM	ROHM
	DN1	SBD, 10 A x 2, 200 V	STPS20200CFP	ST-MICRO
Heat Sink	HS1	Heat Sink	MI-217-25	MEICON. Co., LTD.
	HS2	Heat Sink	MI-301G-25.4	MEICON. Co., LTD.
Inductor	L1, L2	1 mH	768772102	WURTH ELECTRONIK
	L3	2.2 $\mu$ H, 4.3 A	7447462022	WURTH ELECTRONIK
	L4	N.C.	-	-
LED	LED1	RED 1 mA	SML-P11UTT86RK	ROHM
FET	Q1	1700 V, 4 A	SCT2H12NZ	ROHM
Resistor	R1, R2, R3, R4, R5, R6, R7, R8, R9, R10, R13, R14	470 k $\Omega$	MCR18ERTF4703	ROHM
	R11, R12	1 M $\Omega$	KTR18EZPF1004	ROHM
	R15	33 k $\Omega$	MCR10ERTF3302	ROHM
	R16	10 $\Omega$	MCR10ERTF10R0	ROHM
	R17	150 $\Omega$	MCR10EZPF1500	ROHM
	R18, R28	10 k $\Omega$	MCR10ERTF1002	ROHM
	R19	1.5 $\Omega$	ERX2S1R5	PANASONIC
	R20	150 k $\Omega$	MCR10ERTF1503	ROHM
	R21	20 k $\Omega$	MCR10ERTF2002	ROHM
	R22, R24, R32	1 k $\Omega$	MCR10ERTF1001	ROHM
	R23	82 $\Omega$	MCR100JZHF82R0	ROHM
	R25	82 k $\Omega$	MCR10ERTF8202	ROHM
	R26	4.7 k $\Omega$	MCR10ERTF4701	ROHM
	R27	8.2 k $\Omega$	MCR10ERTF8201	ROHM
	R29	N.C.	-	-
	R30	30 k $\Omega$	MCR03ERTF3002	ROHM
	R31	10 $\Omega$	MCR100JZHF10R0	ROHM
	Rsnubber1	200 k $\Omega$	RSF3WS-200KRJT	MAX-QUALITY Co., LTD
	RT1, RT2, RT3	5.1 $\Omega$	FKN2W5R1J	MAX-QUALITY Co., LTD
	RVCC1	11 $\Omega$	MCR10ERTF11R0	ROHM
Trans	T1	EFD-30	GC-FED30-172K	G-CHAN Co., LTD
IC	U1		BD7682FJ-LB	ROHM
PhotoCoupler	U2		LTV-817-B	LITEON
IC	U3		TL431BQ	TI
varistor	VAR1, VAR2, VAR3	1080 V, 10 KA, $\phi$ 20 mm	TMOV20RP750E	LITTELFUSE

## Important Notes on the Use of Reference Designs

- 1) The contents of this document are subject to change without notice for the purpose of improvement.
- 2) ROHM provides reference designs (including, but not limited to, circuit diagrams, layout data, parts lists, reference boards and their evaluation results, etc.) and all materials related to evaluation boards (hereinafter collectively referred to as "Reference Designs, etc.") to customers for the purpose of referencing them in the development of devices, equipment, software, etc. incorporating ROHM products (hereinafter collectively referred to as "Customer Products"). The design, verification, etc. required for the development of the Customer's Product shall be done at the customer's responsibility and expense. In no event shall the customer use the Reference Designs, etc. for any purpose other than the purpose mentioned above.
- 3) Reference Designs, etc. are provided on an "as is" basis. ROHM disclaims all warranties, express or implied, including, but not limited to, warranties of usefulness, functionality, accuracy, merchantability, and fitness for a particular purpose. In no event shall ROHM be liable for any damages (including, but not limited to, lost profits or other incidental, consequential, or punitive damages) arising out of, related to or in connection with the use of or application of the Reference Designs, etc. whether in contract or tort. For the avoidance of doubt, ROHM does not warrant that the Reference Designs, etc. will work with the Customer's Product.
- 4) When using Reference Designs, etc. be sure to request and verify the latest specifications (including the specifications of the products that compose the Reference Design, etc.) separately.
- 5) The customer shall be responsible for implementing safety measures such as derating, redundant design, fire prevention, backup, and fail-safe measures, etc., to prevent personal injury, fire damage, etc., caused by the Customer's Product developed with Reference Designs, etc. ROHM assumes no liability whatsoever for any use in excess of the ratings or in case of failure to observe the instructions for use.
- 6) The application circuit examples, constants, and other information provided in Reference Designs, etc. are intended to illustrate standard operation and usage. Therefore, when designing for mass production, please take into account various external conditions.
- 7) Reference Designs, etc. are intended to show typical operations and examples of application circuits, etc., and do not constitute a license, express or implied, to implement or use any intellectual property rights or any other rights of ROHM or any other company. ROHM shall not be liable for any disputes arising from, related to or in connection with the use of the Reference Designs, etc.
- 8) Please make sure to contact ROHM and obtain ROHM's consent before using the Reference Designs, etc. for the following Customer's Product that requires particularly high reliability. Transportation equipment (in-vehicle, ship, railroad, etc.), trunk line communication equipment, traffic signal equipment, disaster and security equipment, safety equipment, medical equipment, servers, solar cells, power transmission systems, etc.
- 9) Do not use Reference Designs, etc. for the following Customer's Product that requires extremely high reliability. Aerospace equipment, nuclear power control equipment, submarine relay equipment, etc.
- 10) Do not use Reference Designs, etc. for military use, such as development of weapons of mass destruction, or for any other military purpose.
- 11) ROHM does not assume any liability for any accidents or damages caused by non-compliance with the descriptions in this document.
- 12) The information contained in this document has been carefully prepared to ensure accuracy. However, ROHM shall not be liable for any loss or damage incurred by customers due to errors or misprints in this document.
- 13) Do not reproduce or duplicate any part of this document in any form or by any means without ROHM's permission.



Thank you for your accessing to ROHM product informations.  
More detail product informations and catalogs are available, please contact us.

### ROHM Customer Support System

<http://www.rohm.com/contact/>