

## [Main Board]

No.	Device	Designator	Value	Description	Part Number	Manufacture	Quantity	DNP
1	Capacitor	C1,C19,	35V/1 $\mu$	CAP CER 1 $\mu$ F 35V X7R 0603	CGA3E1X7R1V105K080AC	TDK	2	
2	Capacitor	C2,C20,	10V/10 $\mu$	CAP CER 10 $\mu$ F 10V X7R 0805	C2012X7R1A106K125AC	TDK	2	
3	Capacitor	C3,C4,C5,C6,C7,C8,	50V/4700p	CAP CER 4700PF 50V C0G 0603	CGA3E2C0G1H472J080AA	TDK	6	
4	Capacitor	C9,C10,C11,C12, C15,C16,	630V/1 $\mu$	CAP STACKED 1 $\mu$ F 630V MLCC 2220	CAA572X7T2J105M640LH	TDK	6	
5	Capacitor	C13,	24V/1 $\mu$	CAP CER 1 $\mu$ F 25V X7R 0805	C2012X7R1E105K125AB	TDK	1	
6	Capacitor	C14,	50V/10n	CAP CER 10000PF 50V C0G 0805	C2012C0G1H103J060AA	TDK	1	
7	Capacitor	C17,	1.3KV/10 $\mu$	CAP FILM 10 $\mu$ F 1.3KVDC	B32776G1106K000	TDK	1	
8	Capacitor	C18,C21,C22,C23,C24,	50V/0.1 $\mu$	CAP CER 0.1 $\mu$ F 50V X7R 0402	CGA2B3X7R1H104K050BB	TDK	5	
9	LED	D1,D8,	GREEN	LED GREEN DIFFUSED 1608 SMD	SML-D12P8WT86	ROHM Semiconductor	2	
10	Diode	D2,D3,D4,D5,D6,D7,	60V/1A	DIODE SCHOTTKY 60V 1A TUMD2M	RB160VAM-60	ROHM Semiconductor	6	
11	SiC Power Module	HSDIP1,	1200V/70A	HSDIP20, 1200V, 70A, 3-Phase-bridge,	BST70T2P4K01-VC	ROHM Semiconductor	1	
12	Connector	I/F1,	B34B-PHDSS	CONN HEADER VERT 34POS 2MM	B34B-PHDSS	JST	1	
13	Connector	I/F2,	TSW-117-07-S-D	CONN HEADER VERT 34POS 2.54MM	TSW-117-07-S-D	SAMTEC	1	
14	Connector	Q1_Gate1,Q2_Gate1,Q3_Gate1,Q4_Gate1,Q5_Gate1,Q6_Gate1,	B12P-MQ	CONN RCPT 12POS 0.098 TIN PCB	B12P-MQ	JST	6	
15	Connector	Idc_ad1,Iu_ad1,Iw_ad1,Vdc_ad1,Vuv_ad1,	B8P-MQ-C	CONN RCPT 8POS 0.098 TIN PCB	B8P-MQ-C	JST	5	
16	Connector	J1,J15,J17,	B2B-XH-A	CONN HEADER VERT 2POS 2.5MM	B2B-XH-A	JST	3	
17	Connector	J2,J3,J4,J5,J6,J7,J8,J9,J10	73415-2061	CONN MMCX JACK STR 50 OHM SMD	73415-2061	Molex	9	

## [Main Board]

No.	Device	Designator	Value	Description	Part Number	Manufacture	Quantity	DNP
18	Terminal	J11,J12,J13,J14,J16,	7808	TERM SCREW M5 6PIN PCB	7808	Keystone Electronics	5	
19	IC	IC1,IC2,IC3,IC4,IC5,	LMR1802G-LBTR	IC CMOS 1 CIRCUIT 5SSOP	LMR1802G-LBTR	ROHM Semiconductor	5	
20	IC	PS1,PS2,	NME1205SC	DC DC CONVERTER 5V 1W	NME1205SC	Murata Electronics	2	
21	Resistor	R1,R15,	470	RES SMD 470 OHM 1% 1/8W 0805	MCR10EZPF4700	ROHM Semiconductor	2	
22	Resistor	R2,	10k	RES SMD 10K OHM 1% 1/8W 0805	MCR10ERTF1002	ROHM Semiconductor	1	
23	Resistor	R3,	56	RES SMD 56 OHM 1% 1/8W 0805	MCR10ERTF56R0	ROHM Semiconductor	1	
24	Resistor	R4,R5,R6,	1m	RES SMD 1m OHM 1% 8W 2512	PSR100KTQFH1L00	ROHM Semiconductor	3	
25	Resistor	R7,R8,R9,R10,R11,R22,R23,R24,R25,R26,	300k	RES SMD 300K OHM 1% 1/4W 1206	MCR18ERTF3003	ROHM Semiconductor	10	
26	Resistor	R12,R27,	360	RES SMD 360 OHM 1% 1/4W 1206	MCR18ERTF3600	ROHM Semiconductor	2	DNP
27	Resistor	R13,R17,R19,R21,R29,	0	RES SMD 0 OHM JUMPER 1/8W 0805	MCR10ERTJ000	ROHM Semiconductor	5	DNP
28	Resistor	R14,R16,R18,R20,R28,	0	RES SMD 0 OHM JUMPER 1/8W 0805	MCR10ERTJ000	ROHM Semiconductor	5	

## [Gate Driver Board]

No.	Device	Designator	Value	Description	Part Number	Manufacture	Quantity	DNP
1	Capacitor	C1,C11,	35V/1 $\mu$	CAP CER 1 $\mu$ F 35V X7R 0603	CGA3E1X7R1V105K080AC	TDK	2	
2	Capacitor	C2,C12,C13,C15,	50V/0.1 $\mu$	CAP CER 0.1 $\mu$ F 50V X7R 0402	CGA2B3X7R1H104K050BB	TDK	4	
3	Capacitor	C3,C5,C6,	35V/10 $\mu$	CAP CER 10 $\mu$ F 35V X7R 1206	CGA5L1X7R1V106M160AC	TDK	3	
4	Capacitor	C4,	25V/10 $\mu$	CAP CER 10 $\mu$ F 25V X7S 0805	CGA4J1X7S1E106K125AC	TDK	1	
5	Capacitor	C9,C10,	50V/1000p	CAP CER 1000PF 50V C0G 0603	CGA3E2C0G1H102J080AA	TDK	2	
6	Capacitor	C14,	50V/1000p	CAP CER 1000PF 50V C0G 0603	CGA3E2C0G1H102J080AA	TDK	1	DNP
7	LED	D1,	GREEN	LED GREEN DIFFUSED 1608 SMD	SML-D12P8W	ROHM Semiconductor	1	
8	Diode	D2,	40V/1A	DIODE SCHOTTKY 40V 1A PMDU	RB160MM-40TR	ROHM Semiconductor	1	
9	Diode	D3,D4,	60V/1A	DIODE SCHOTTKY 60V 1A TUMD2M	RB160VAM-60TR	ROHM Semiconductor	2	
10	Connector	J1,	12MQ-ST	CONN RCPT 12P 0.098 TIN PCB R/A	12MQ-ST	JST	1	
11	Resistor	JP1,	-	—	—	—	1	DNP
12	Filter	L1,	DLW21PH201XQ2L	CMC 500MA 2LN 200 OHM SMD AECQ200	DLW21PH201XQ2L	Murata Electronics	1	
13	Resistor	R1,R3,R4,	100	RES SMD 100 OHM 5% 1/8W 0805	MCR10EZPJ101	ROHM Semiconductor	3	
14	Resistor	R2,	470	RES SMD 470 OHM 1% 1/8W 0805	MCR10EZPF4700	ROHM Semiconductor	1	
15	Resistor	R6,	6.8	RES SMD 6.8 OHM 5% 3/4W 1206	ESR18EZPJ6R8	ROHM Semiconductor	1	
16	Resistor	R7,	6.8	RES SMD 6.8 OHM 5% 3/4W 1206	ESR18EZPJ6R8	ROHM Semiconductor	1	
17	Resistor	R8,	4.7k	RES SMD 4.7K OHM 5% 1/8W 0805	MCR10EZPJ472	ROHM Semiconductor	1	
18	Resistor	R9,	0	RES SMD 0 OHM JUMPER 1/8W 0805	MCR10ERTJ000	ROHM Semiconductor	1	DNP
19	IC	U1,	18V/-2.5V, 80mA/80mA DC DC CONVERTER 18V -2.5V 2W	MGJ2D121802SC	Murata Electronics	1		
20	IC	U2,	200mA/5.0V	IC REG LINEAR 5V 200MA 8HTSOP	BD450M2WEFJ-CE2	ROHM Semiconductor	1	
21	IC	U3,	BM61M41RFV-CE2	DGT ISO 3.75KV 1CH GT DVR 10SSOP	BM61M41RFV-CE2	ROHM Semiconductor	1	

Note : Gate Driver Board x 6

## Important Notes on the Use of Reference Designs

- 1) The contents of this document are subject to change without notice for the purpose of improvement.
- 2) ROHM provides reference designs (including, but not limited to, circuit diagrams, layout data, parts lists, reference boards and their evaluation results, etc.) and all materials related to evaluation boards (hereinafter collectively referred to as "Reference Designs, etc.") to customers for the purpose of referencing them in the development of devices, equipment, software, etc. incorporating ROHM products (hereinafter collectively referred to as "Customer Products"). The design, verification, etc. required for the development of the Customer's Product shall be done at the customer's responsibility and expense. In no event shall the customer use the Reference Designs, etc. for any purpose other than the purpose mentioned above.
- 3) Reference Designs, etc. are provided on an "as is" basis. ROHM disclaims all warranties, express or implied, including, but not limited to, warranties of usefulness, functionality, accuracy, merchantability, and fitness for a particular purpose. In no event shall ROHM be liable for any damages (including, but not limited to, lost profits or other incidental, consequential, or punitive damages) arising out of, related to or in connection with the use of or application of the Reference Designs, etc. whether in contract or tort. For the avoidance of doubt, ROHM does not warrant that the Reference Designs, etc. will work with the Customer's Product.
- 4) When using Reference Designs, etc. be sure to request and verify the latest specifications (including the specifications of the products that compose the Reference Design, etc.) separately.
- 5) The customer shall be responsible for implementing safety measures such as derating, redundant design, fire prevention, backup, and fail-safe measures, etc., to prevent personal injury, fire damage, etc., caused by the Customer's Product developed with Reference Designs, etc. ROHM assumes no liability whatsoever for any use in excess of the ratings or in case of failure to observe the instructions for use.
- 6) The application circuit examples, constants, and other information provided in Reference Designs, etc. are intended to illustrate standard operation and usage. Therefore, when designing for mass production, please take into account various external conditions.
- 7) Reference Designs, etc. are intended to show typical operations and examples of application circuits, etc., and do not constitute a license, express or implied, to implement or use any intellectual property rights or any other rights of ROHM or any other company. ROHM shall not be liable for any disputes arising from, related to or in connection with the use of the Reference Designs, etc.
- 8) Please make sure to contact ROHM and obtain ROHM's consent before using the Reference Designs, etc. for the following Customer's Product that requires particularly high reliability. Transportation equipment (in-vehicle, ship, railroad, etc.), trunk line communication equipment, traffic signal equipment, disaster and security equipment, safety equipment, medical equipment, servers, solar cells, power transmission systems, etc.
- 9) Do not use Reference Designs, etc. for the following Customer's Product that requires extremely high reliability. Aerospace equipment, nuclear power control equipment, submarine relay equipment, etc.
- 10) Do not use Reference Designs, etc. for military use, such as development of weapons of mass destruction, or for any other military purpose.
- 11) ROHM does not assume any liability for any accidents or damages caused by non-compliance with the descriptions in this document.
- 12) The information contained in this document has been carefully prepared to ensure accuracy. However, ROHM shall not be liable for any loss or damage incurred by customers due to errors or misprints in this document.
- 13) Do not reproduce or duplicate any part of this document in any form or by any means without ROHM's permission.



Thank you for your accessing to ROHM product informations.  
More detail product informations and catalogs are available, please contact us.

### ROHM Customer Support System

<http://www.rohm.com/contact/>